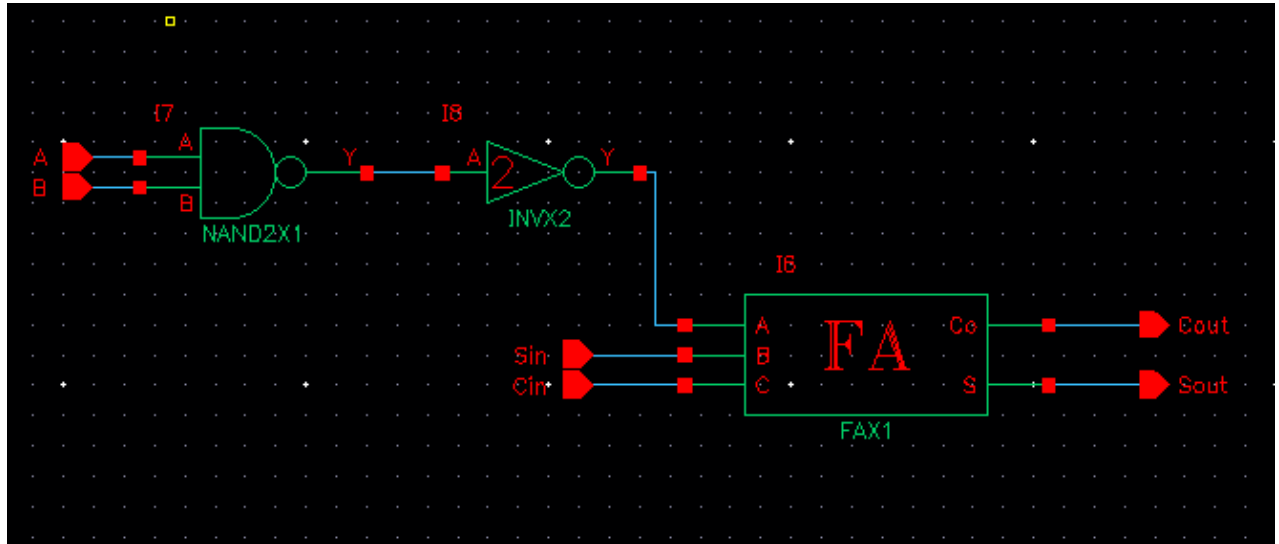



ECE520 Introduction to VLSI, Project 4

Name: Arijit Sengupta, ID: 001441748


Part A




SysF schematic

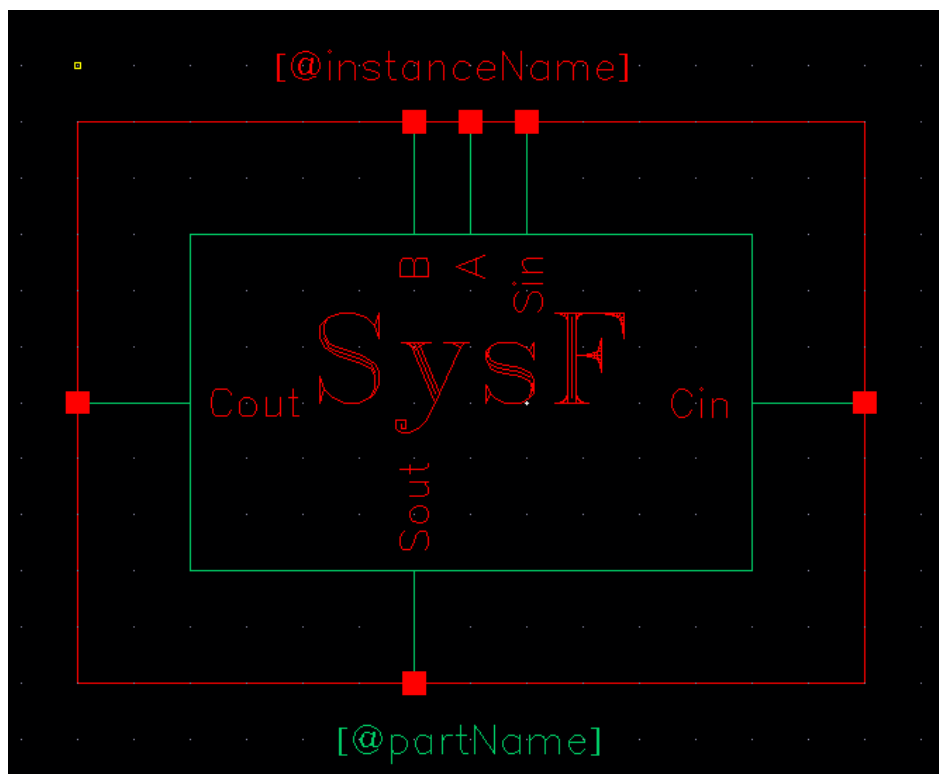

SysF symbol

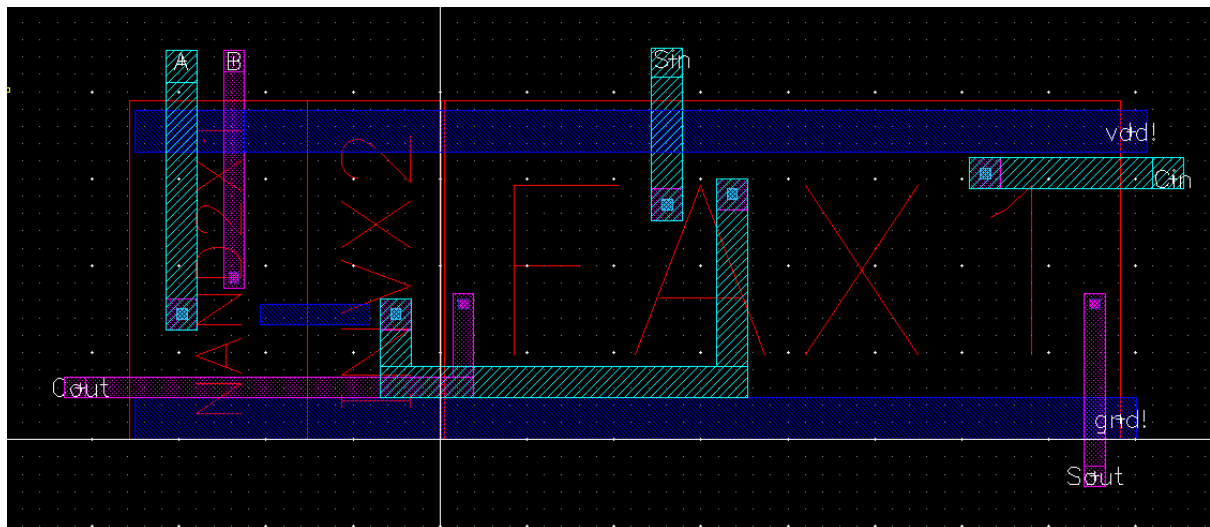

SysF layout (Top level)

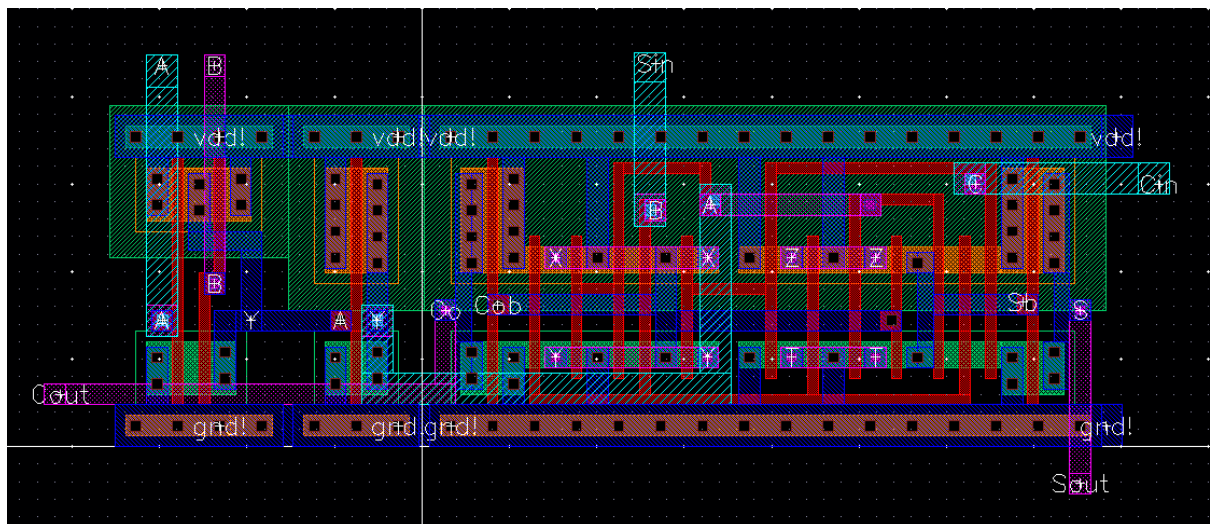

SysF layout (Lower level)

```
DRC started.....Sat Dec 14 17:51:17 2019
completed ....Sat Dec 14 17:51:17 2019
CPU TIME = 00:00:00 TOTAL TIME = 00:00:00
***** Summary of rule violations for cell "SysF layout" *****
Total errors found: 0
```


Artist LVS [X] [] [X]

Commands Help **cadence**

Run Directory: LVS [Browse]

Create Netlist: ☒ schematic ☒ extracted

Library: PROJ4 PROJ4

Cell: SysF SysF

View: schematic extracted

[Browse] [Sel by Cursor] [Browse] [Sel by Cursor]

Rules File: divaLVS.ru1 [Browse]

Rules Library: ☒ NCSU_TechLib_am106

LVS Options: ☒ Rewiring ☐ Device Fixing
☐ Create Cross Reference ☒ Terminals

Correspondence File: ☐ lvs_corr_file [Create]

Switch Names: []

Priority: 0 Run: background [v]

[Run] [Output] [Error Display] [Monitor] [Info]

[Backannotate] [Parasitic Probe] [Build Analog] [Build Mixed]

22

[X] [X]

The LVS job has completed. The net-lists match.

Run Directory: /network/rit/home/as447343/cadence/LVS

[Close]

Artist LVS [X] [] [X]

Commands Help **cadence**

Run Directory: LVS [Browse]

Create Netlist: ☒ schematic ☒ extracted

Library: PROJ4 PROJ4

Cell: SysF SysF

View: schematic analog_extracted

[Browse] [Sel by Cursor] [Browse] [Sel by Cursor]

Rules File: divaLVS.ru1 [Browse]

Rules Library: ☒ NCSU_TechLib_am106

LVS Options: ☒ Rewiring ☐ Device Fixing
☐ Create Cross Reference ☒ Terminals

Correspondence File: ☐ lvs_corr_file [Create]

Switch Names: []

Priority: 0 Run: background [v]

[Run] [Output] [Error Display] [Monitor] [Info]


[Backannotate] [Parasitic Probe] [Build Analog] [Build Mixed]

22

[X] Build Analog Extracted View [X]


Extracted Parasitics: ☒ Include All ☐ Set From Schematic ☐ None

[OK] [Cancel] [Defaults] [Apply] [Help]

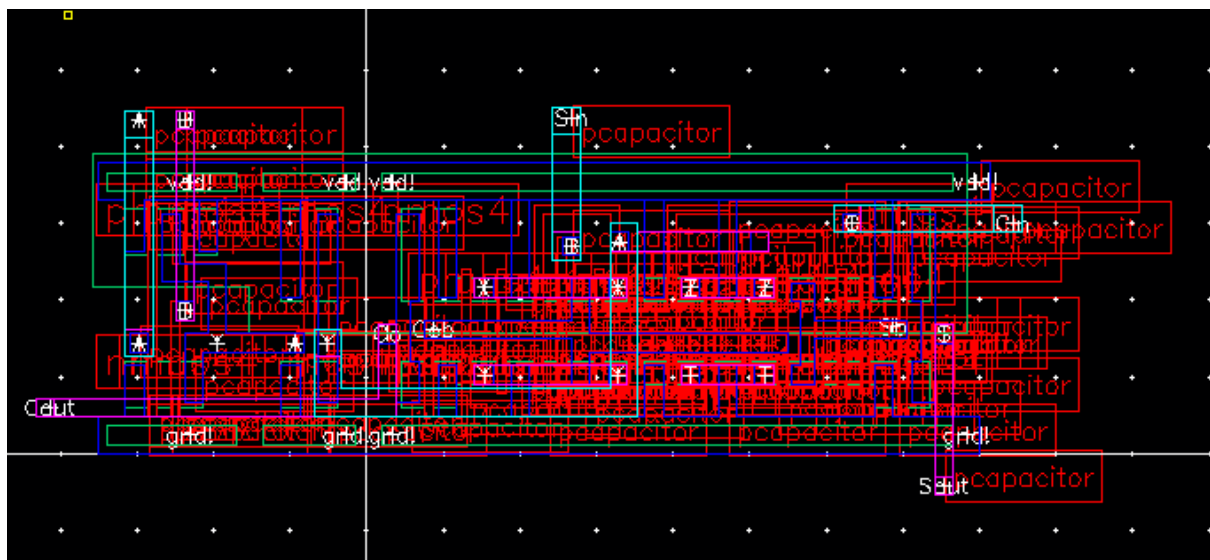


SysF analog extracted view


Part B

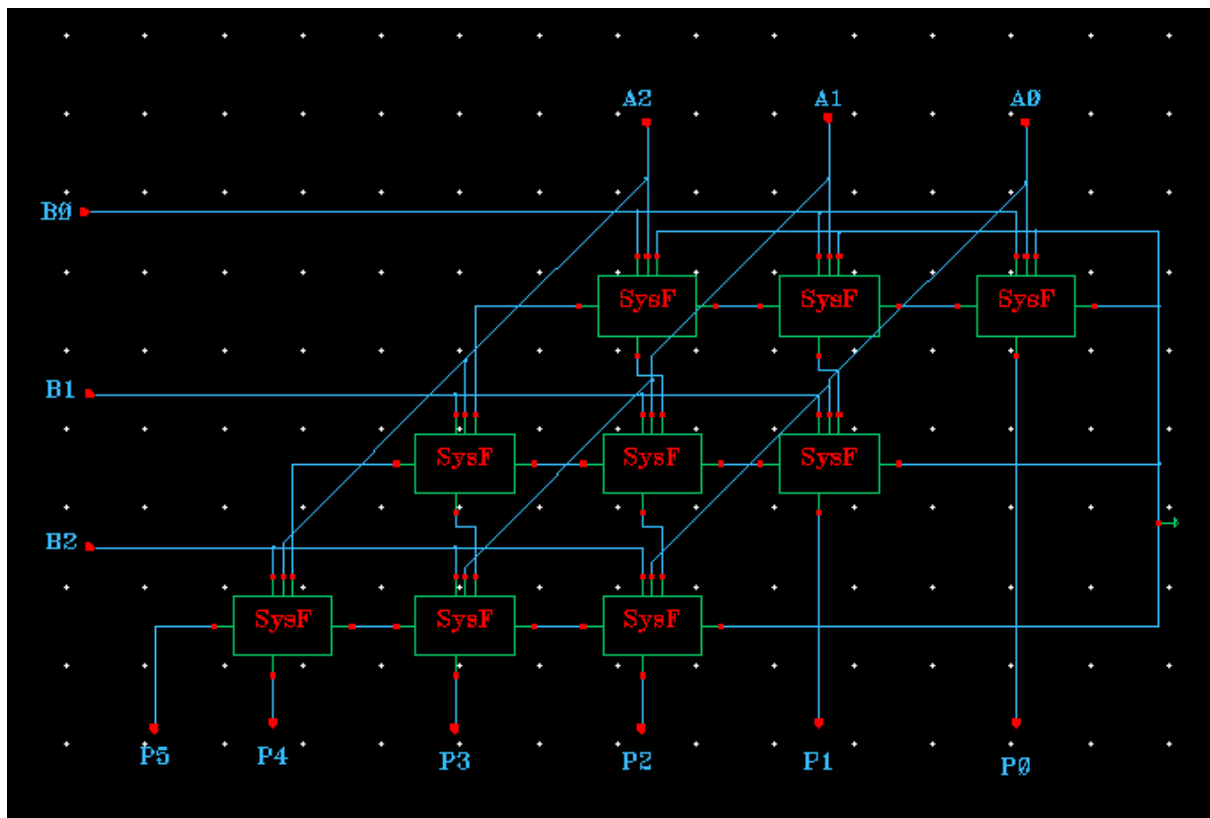


Mult3x3 schematic

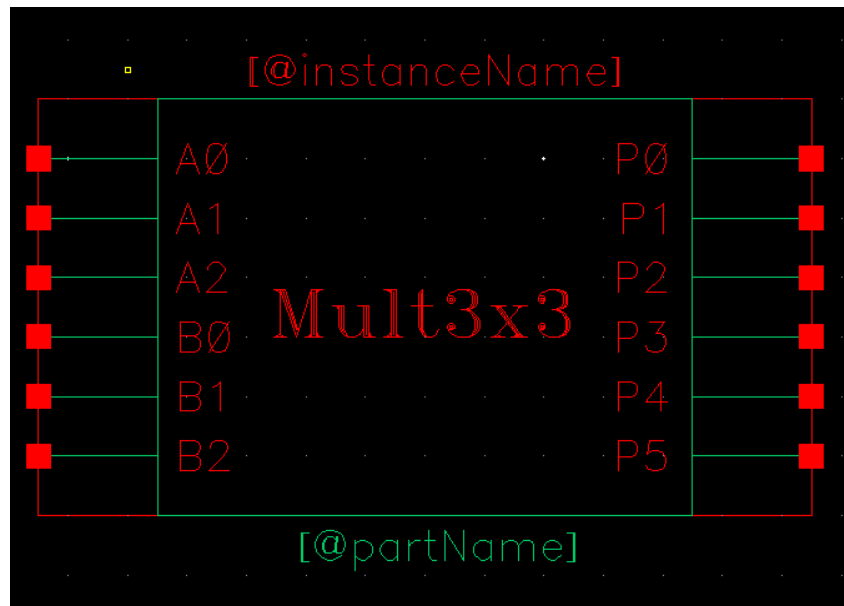


Mult3x3 symbol

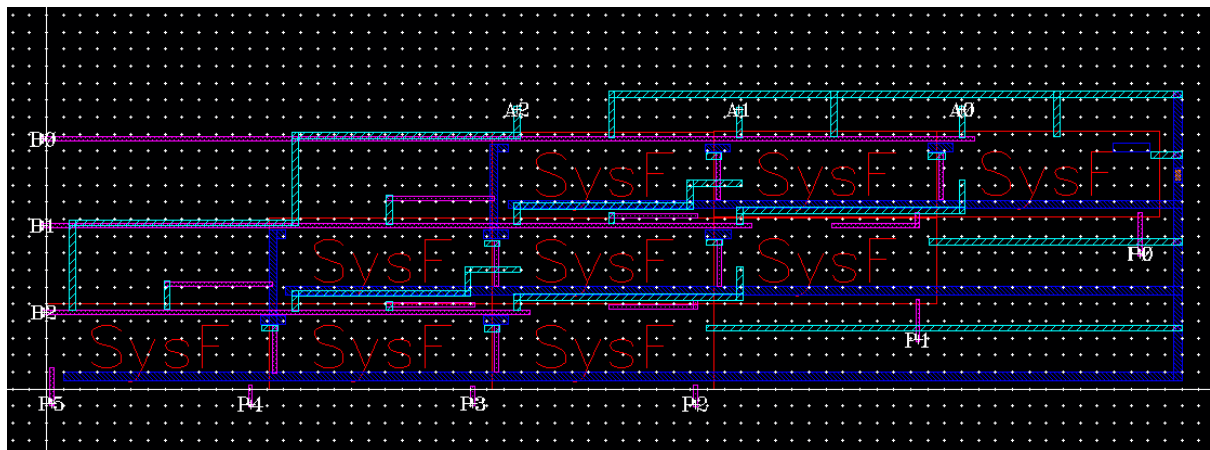

Mult3x3 Layout (Top Level)

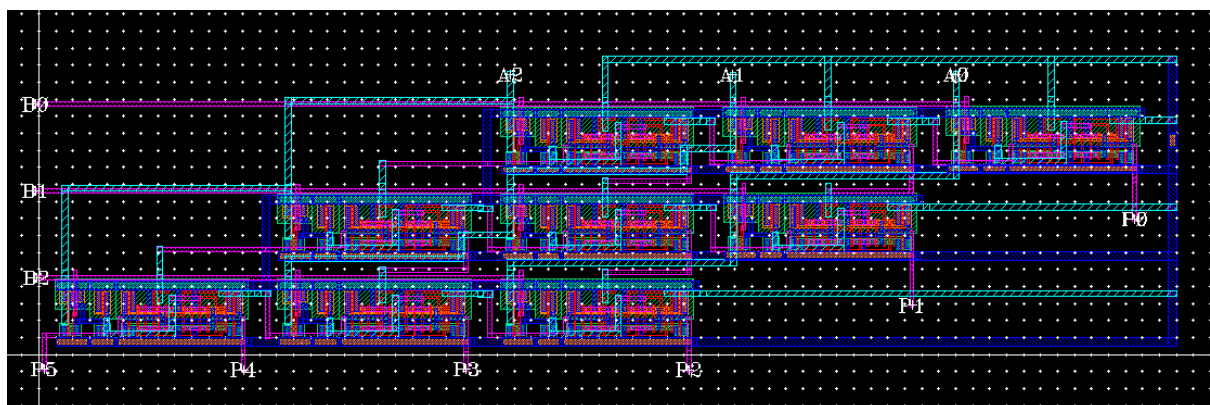



Mult3x3 Layout (Lower Level)

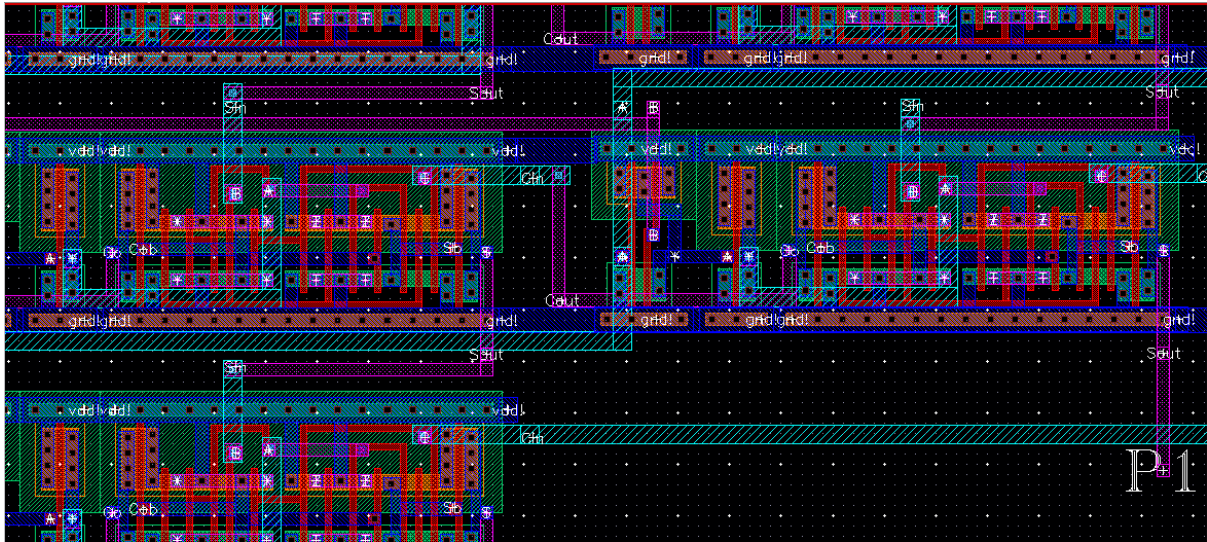


Mult3x3 Layout (zoomed in to individual SysF cells)
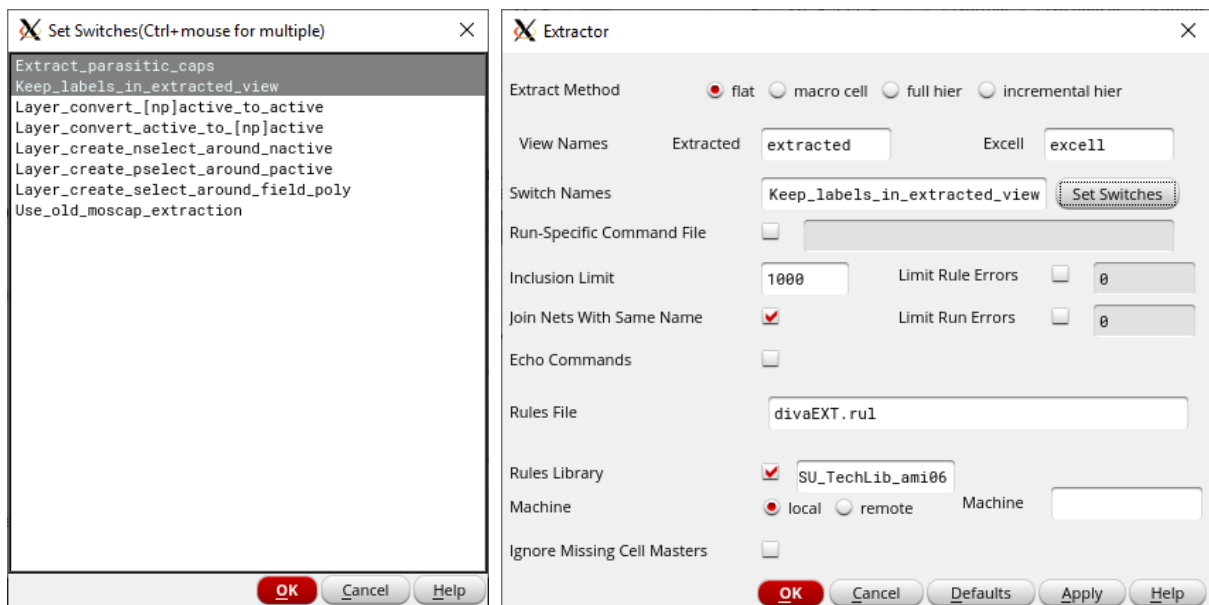
```
DRC started.....Sat Dec 14 18:03:08 2019
completed ....Sat Dec 14 18:03:08 2019
CPU TIME = 00:00:00 TOTAL TIME = 00:00:00
***** Summary of rule violations for cell "Mult3x3 layout" *****
Total errors found: 0
```



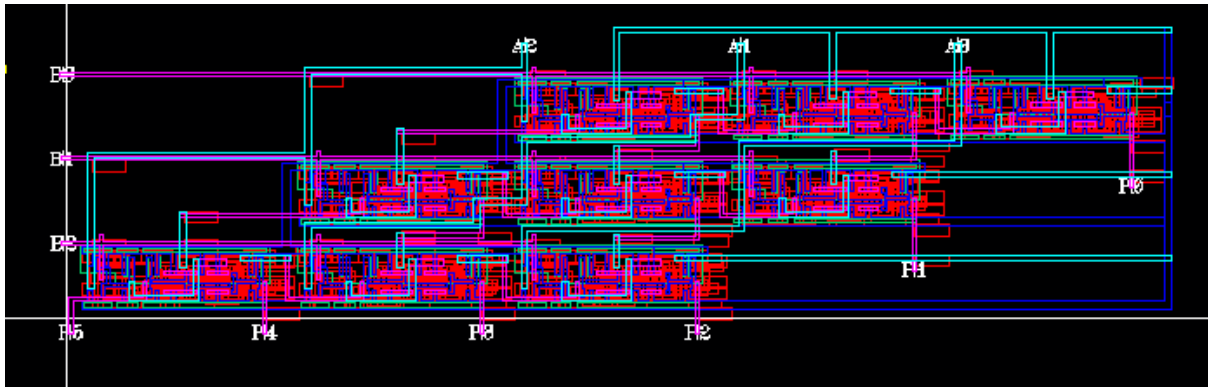

Mult3x3 extracted view (Top Level)

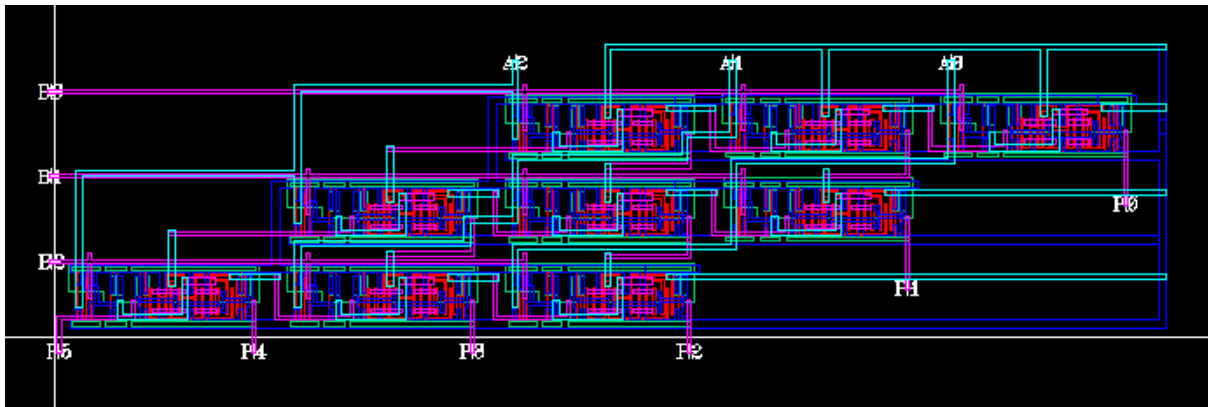

Mult3x3 extracted view (Lower Level)

Artist LVS

Commands Help

Run Directory: LVS [Browse]

Create Netlist: ☒ schematic ☒ extracted

Library: PROJ4 PROJ4

Cell: Mult3x3 Mult3x3

View: schematic extracted

[Browse] [Sel by Cursor] [Browse] [Sel by Cursor]

Rules File: divaLVS.rul [Browse]

Rules Library: ☒ NCSU_TechLib_am106

LVS Options: ☒ Rewiring ☐ Device Fixing

☐ Create Cross Reference ☒ Terminals

Correspondence File: ☐ lvs_corr_file [Create]


Switch Names: [Text Box]


Priority: 0 Run: background

[Run] [Output] [Error Display] [Monitor] [Info]

[Backannotate] [Parasitic Probe] [Build Analog] [Build Mixed]

26

 

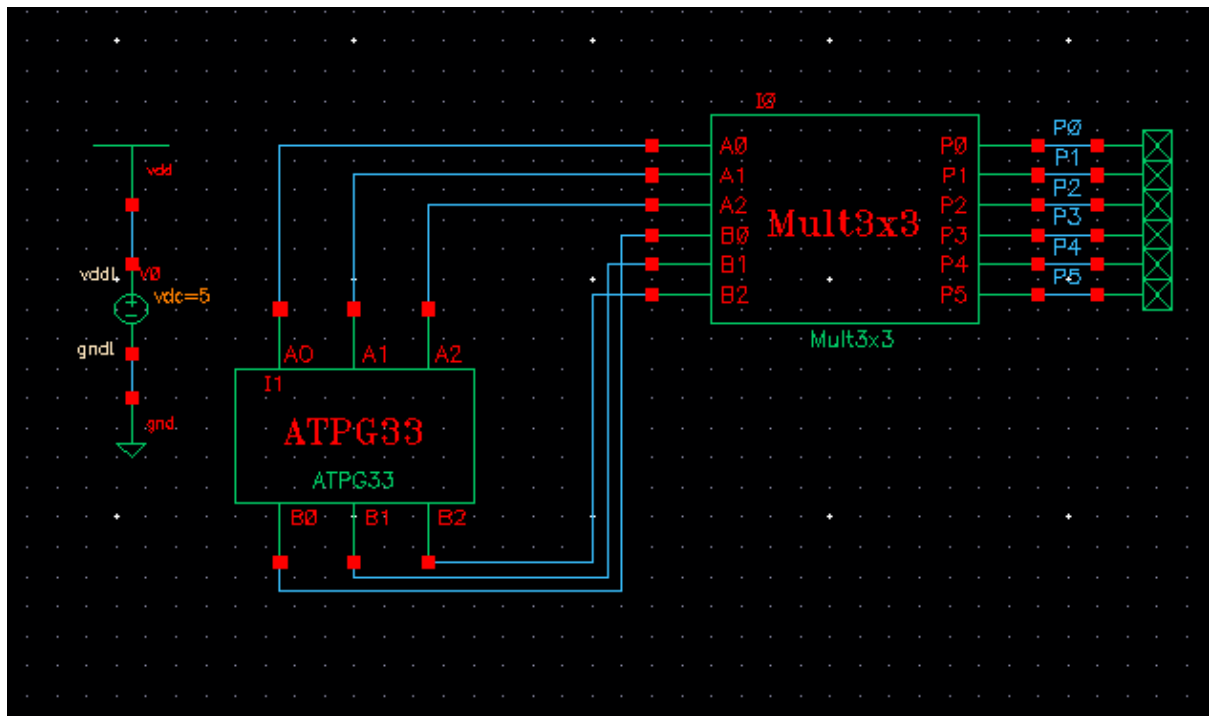

TBmul33 schematic

Part C


B2	B1	B0	A2	A1	A0	P5	P4	P3	P2	P1	P0
0	0	0	1	1	1	0	0	0	0	0	0
0	0	1	1	1	1	0	0	0	1	1	1
0	1	0	1	1	1	0	0	1	1	1	0
0	1	1	1	1	1	0	1	0	1	0	1
1	0	0	1	1	1	0	1	1	1	0	0
1	0	1	1	1	1	0	1	1	1	1	1
1	1	0	1	1	1	1	0	1	0	1	0
1	1	1	1	1	1	1	1	0	0	0	1

I chose the MSBs B2, B1 and B0 as 3 vpulse with the following values:


- B2: Period = 4T, Pulse width = 1.95T, Delay = 1ns, Rise time = Fall time = 0.05T
- B1: Period = 2T, Pulse width = 0.95T, Delay = 1ns, Rise time = Fall time = 0.05T
- B0: Period = T, Pulse width = 0.45T, Delay = 1ns, Rise time = Fall time = 0.05T

I added vdc to the LSBs A2, A1, A0 and gave the DC voltage as D (Don't care!). D can be set as 5V (for logic 1) and 0V (for logic 0) during simulation. For our results, since it's a multiplier D=5V will be much more beneficial to yield proper values because multiplying anything by 0 will only return 0.

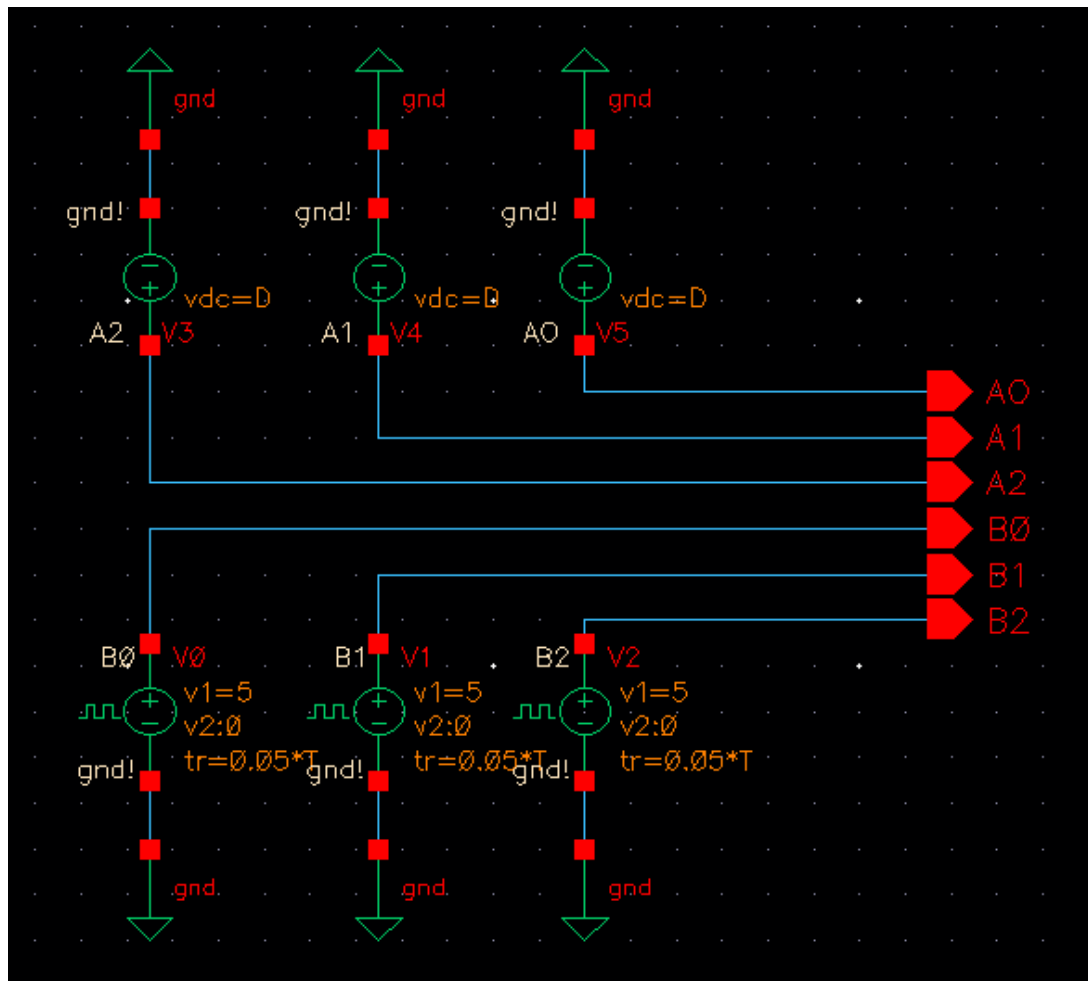
So, we obtain unique values for P5...P0 for these 8 input vectors from the ATPG33.




ATPG33 schematic

 


ATPG33 symbol

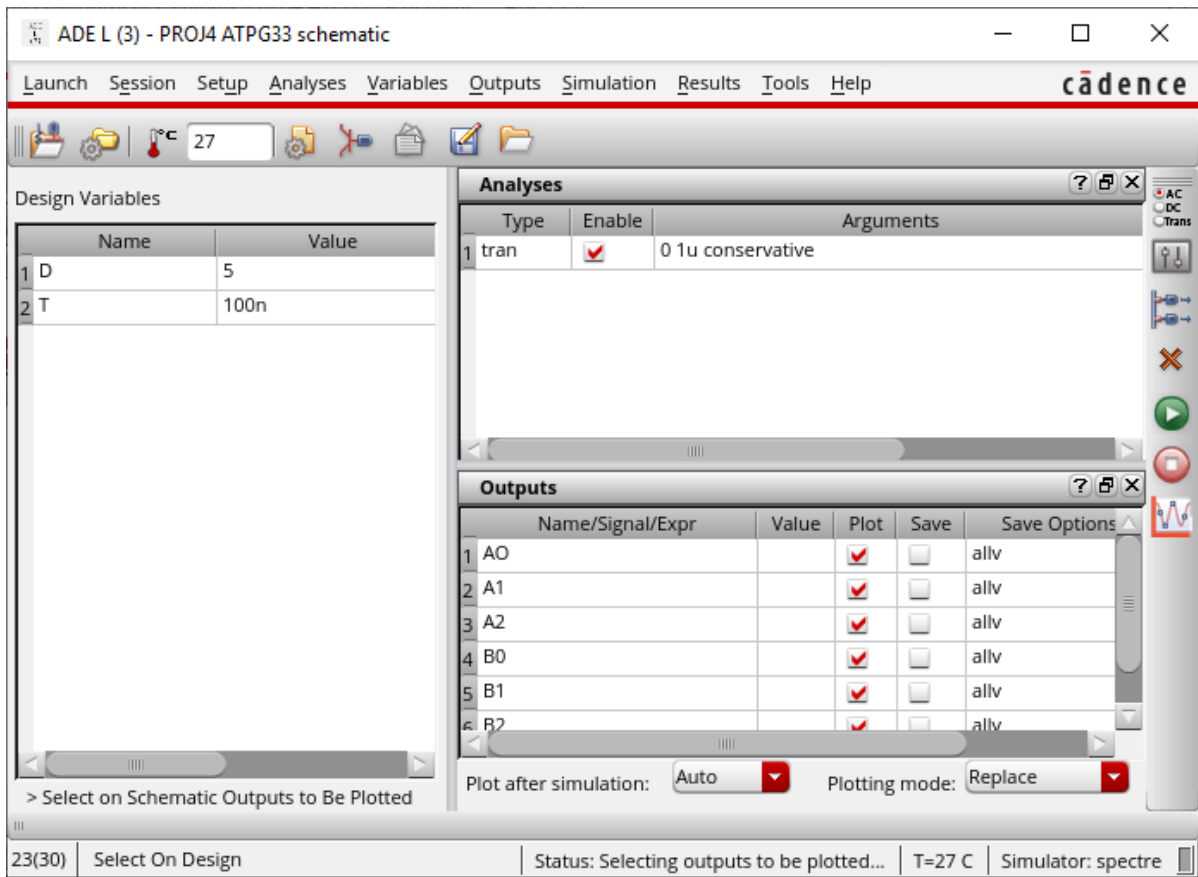


ATPG33 ADE L

 

ATPG33 output waveform

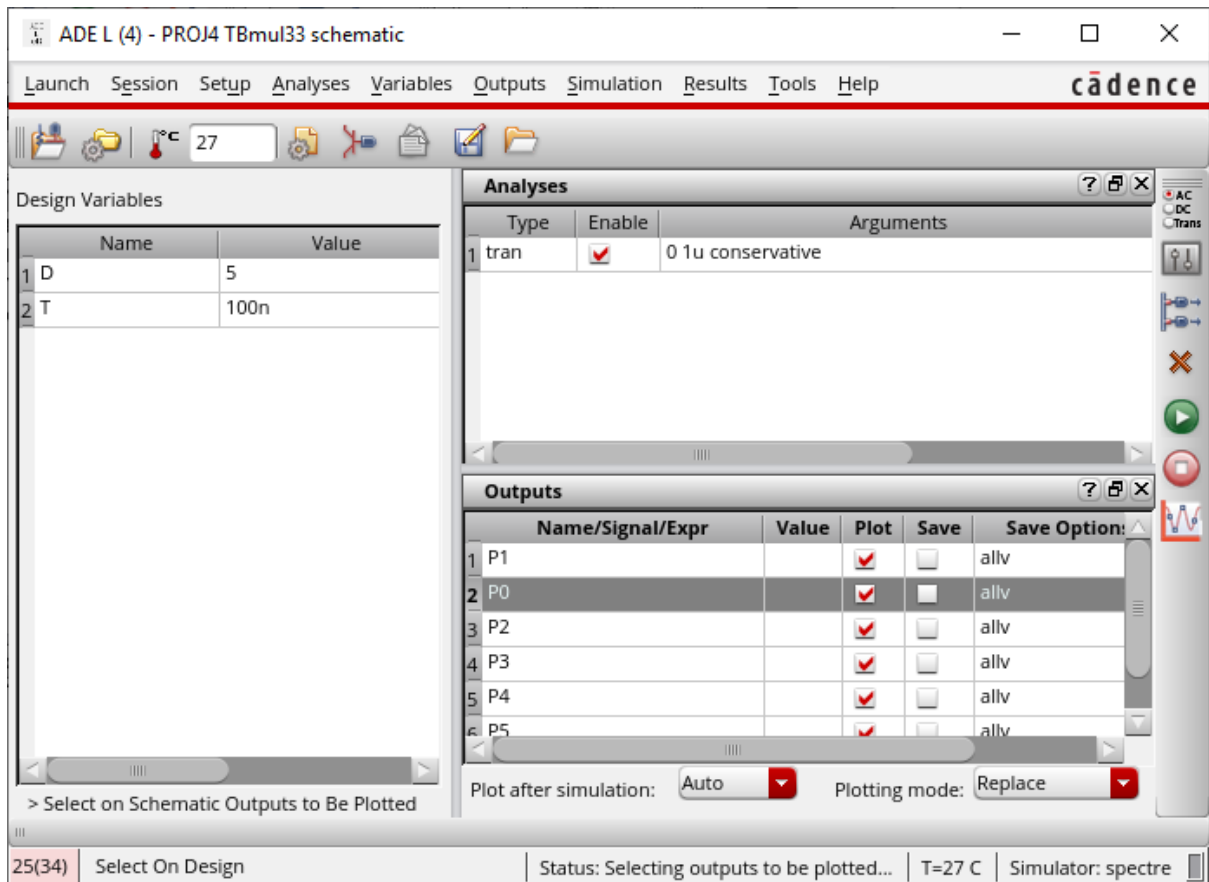

TBmul33 ADE L

 

TBmul33 output waveform

The values from the plot matches exactly with the calculated values in the table above. Hence, the circuit works fine.

Part D

B7	B6	B5	B4	B3	B2	B1	B0	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	D	D	D	D	D	D	D	D	D	D	D	D
0	0	0	1	D	D	D	D	D	D	D	D	D	D	D	D
0	0	1	0	D	D	D	D	D	D	D	D	D	D	D	D
0	0	1	1	D	D	D	D	D	D	D	D	D	D	D	D
0	1	0	0	D	D	D	D	D	D	D	D	D	D	D	D
0	1	0	1	D	D	D	D	D	D	D	D	D	D	D	D
0	1	1	0	D	D	D	D	D	D	D	D	D	D	D	D
0	1	1	1	D	D	D	D	D	D	D	D	D	D	D	D
1	0	0	0	D	D	D	D	D	D	D	D	D	D	D	D
1	0	0	1	D	D	D	D	D	D	D	D	D	D	D	D
1	0	1	0	D	D	D	D	D	D	D	D	D	D	D	D
1	0	1	1	D	D	D	D	D	D	D	D	D	D	D	D
1	1	0	0	D	D	D	D	D	D	D	D	D	D	D	D
1	1	0	1	D	D	D	D	D	D	D	D	D	D	D	D
1	1	1	0	D	D	D	D	D	D	D	D	D	D	D	D
1	1	1	1	D	D	D	D	D	D	D	D	D	D	D	D


I chose the MSBs B7, B6, B5 and B4 as 4 vpulse with the following values:

- B7: Period = 8T, Pulse width = 3.95T, Delay = 1ns, Rise time = Fall time = 0.05T
- B6: Period = 4T, Pulse width = 1.95T, Delay = 1ns, Rise time = Fall time = 0.05T
- B5: Period = 2T, Pulse width = 0.95T, Delay = 1ns, Rise time = Fall time = 0.05T
- B4: Period = T, Pulse width = 0.45T, Delay = 1ns, Rise time = Fall time = 0.05T


I added vdc to the other bits B3...B0, A7...A0 and gave the DC voltage as D (Don't care!). D can be set as 5V (for logic 1) and 0V (for logic 0) during simulation. For our results, since it's a multiplier **D=5V (logic 1)** will be much more beneficial to yield proper values because multiplying anything by 0 will only return 0.

These 16 values will basically cover about 90% of the 65536 test cases as we can replace any 4-bits with any other 4-bits (say B7...B4 with A7...A4 and obtain similar results). So basically, what we do here is create $2^4 = 16$ combinations from 4 input bits, which in turn can be fed to any 4 of the 16 bits and give about the same results as testing all $2^{16} = 65536$ combinations.

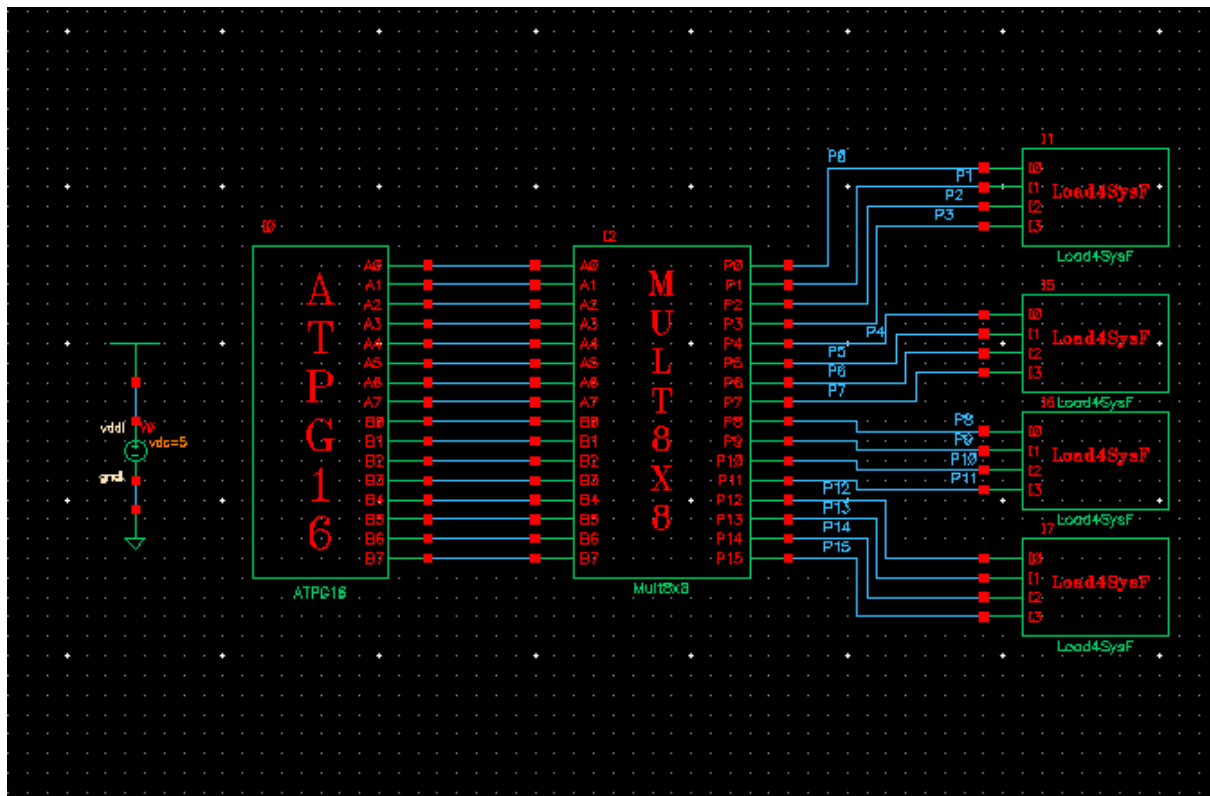
So, we obtain unique values for P15...P0 for these 16 input vectors from the ATPG16.




TBmul88 schematic

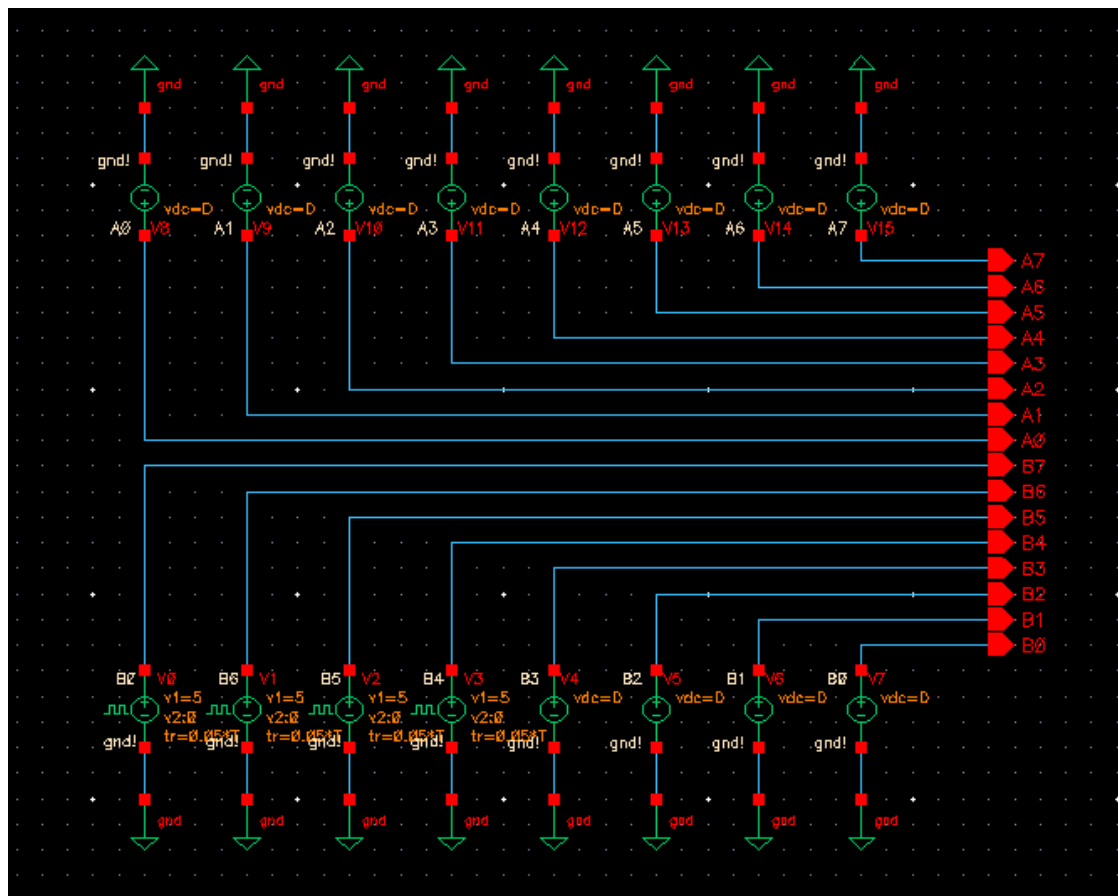

ATPG16 schematic

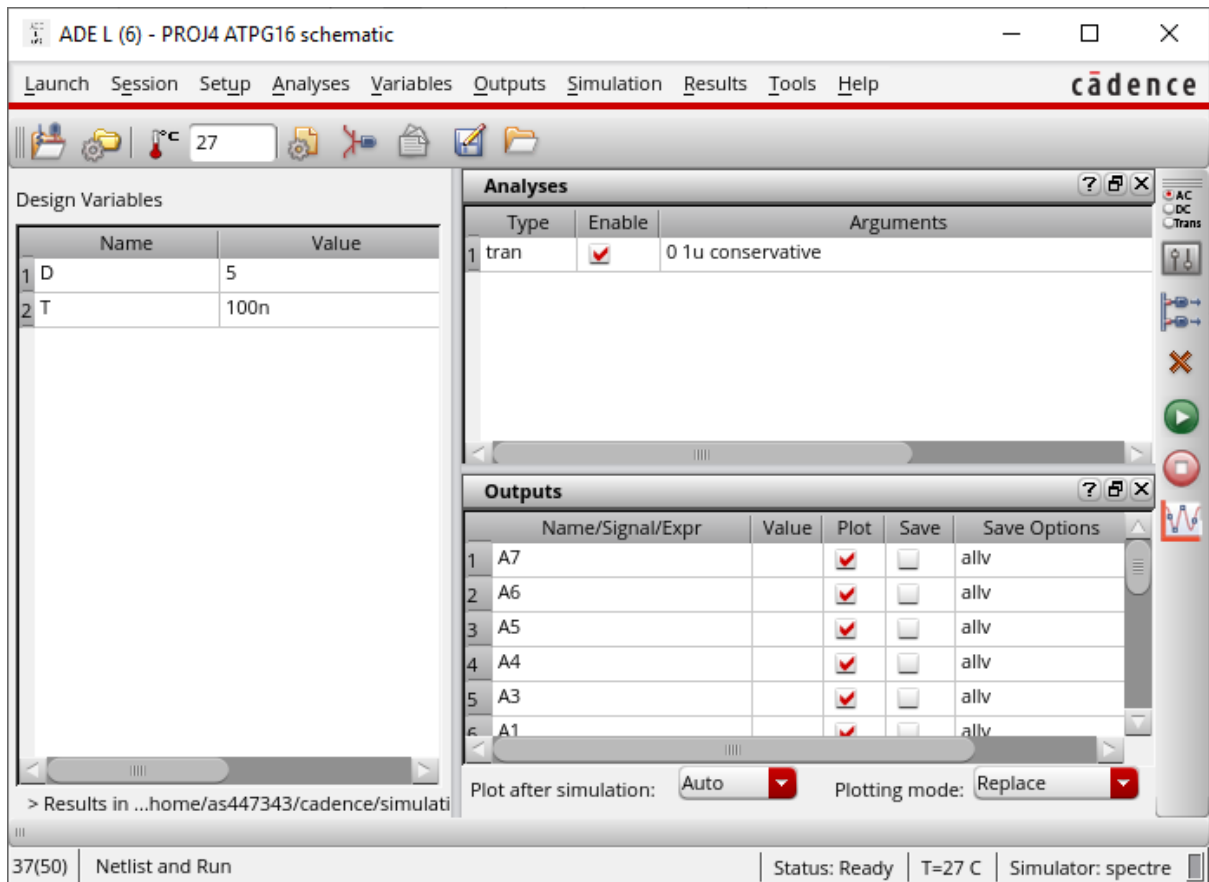


ATPG16 schematic ADE L

 


ATPG16 output waveform

The values from the plot matches exactly with the calculated values from the table hence it confirms the circuit will work fine.


Part E

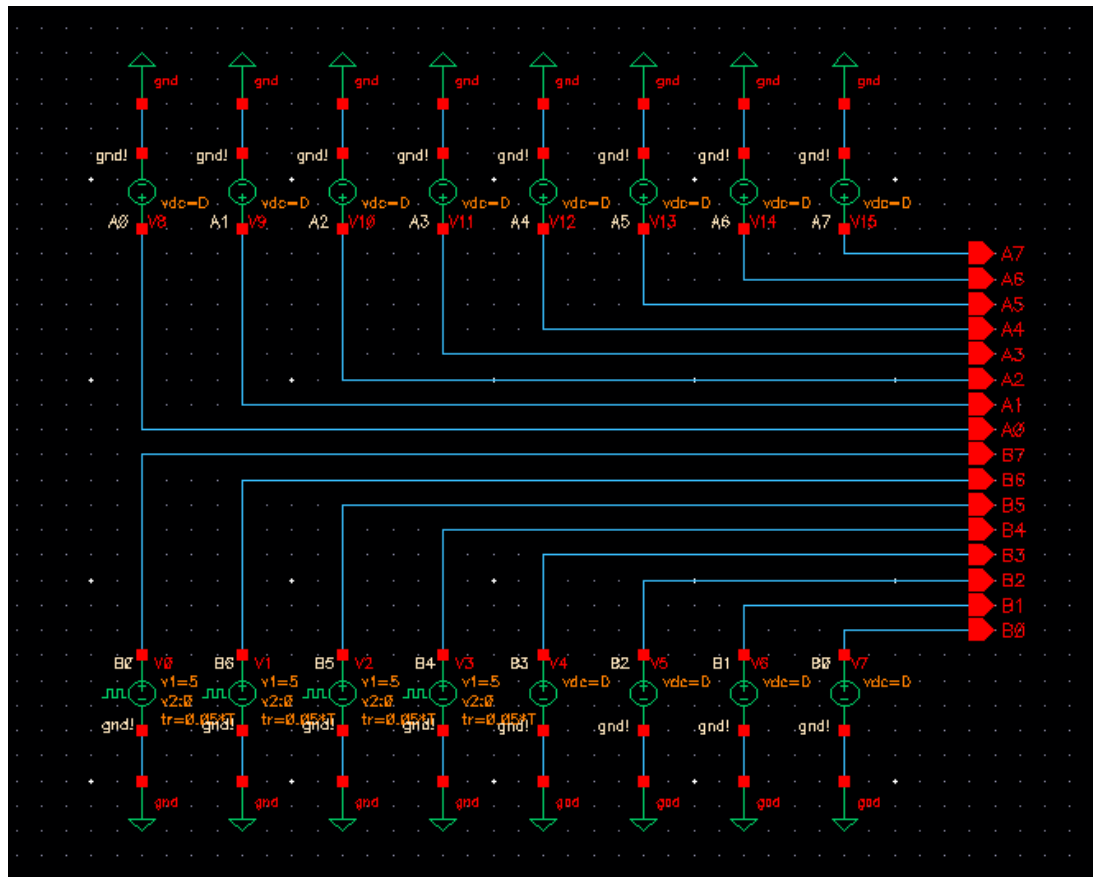


ATPG16 schematic

 


ATPG16 symbol

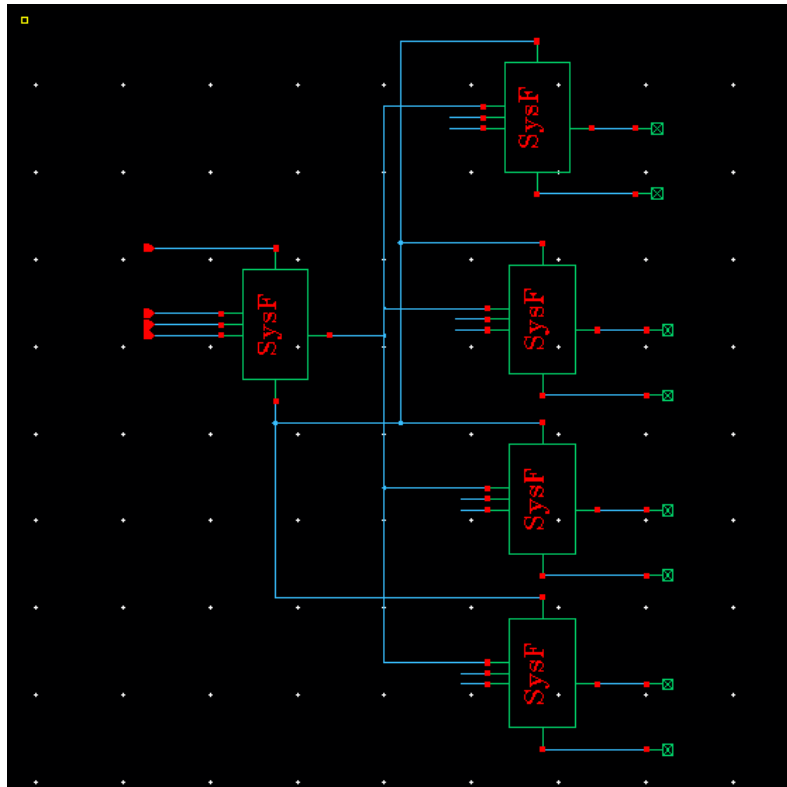


Load4SysF schematic

 


Load4SysF symbol

 


Mult8x8 schematic

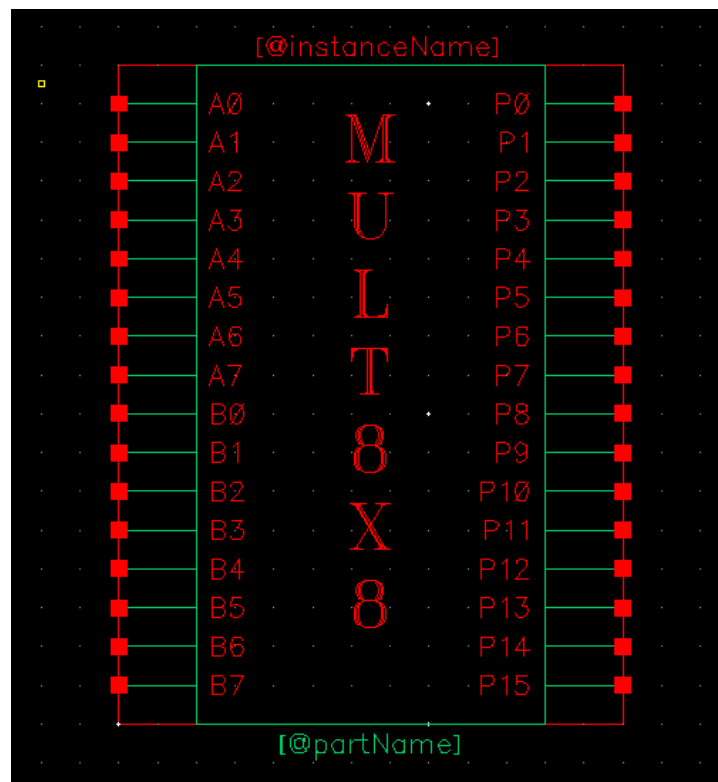




Mult8x8 symbol

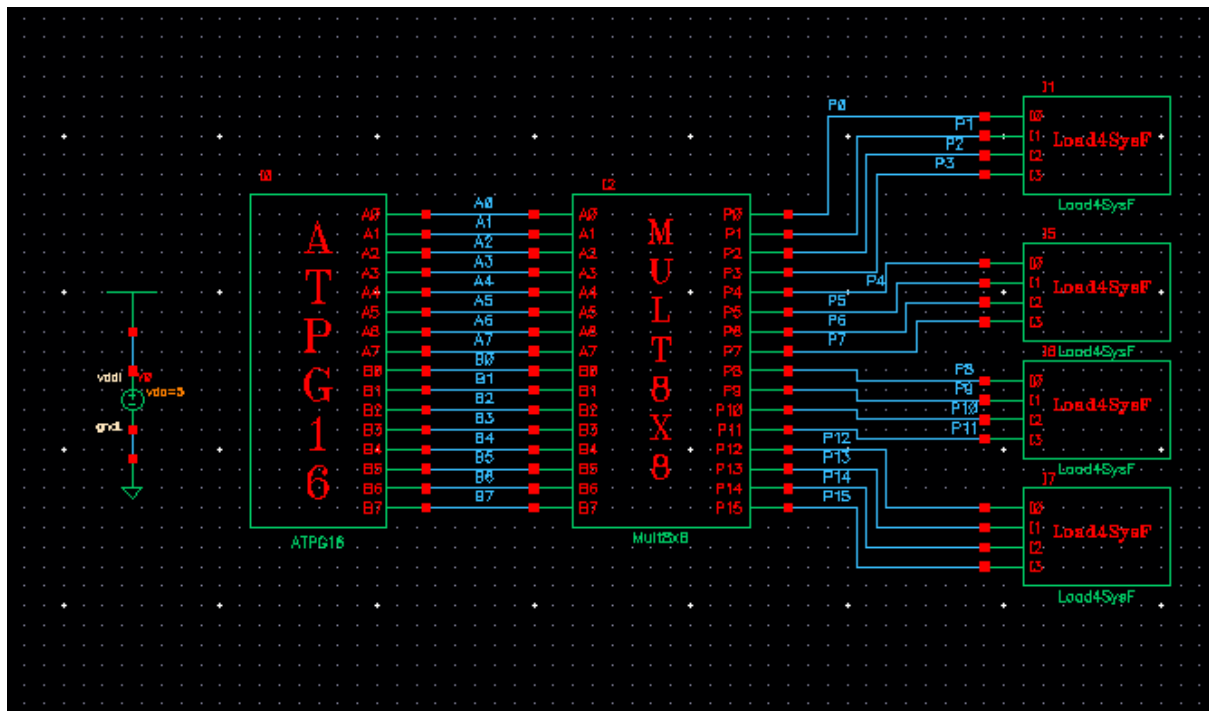

TBmul88 schematic

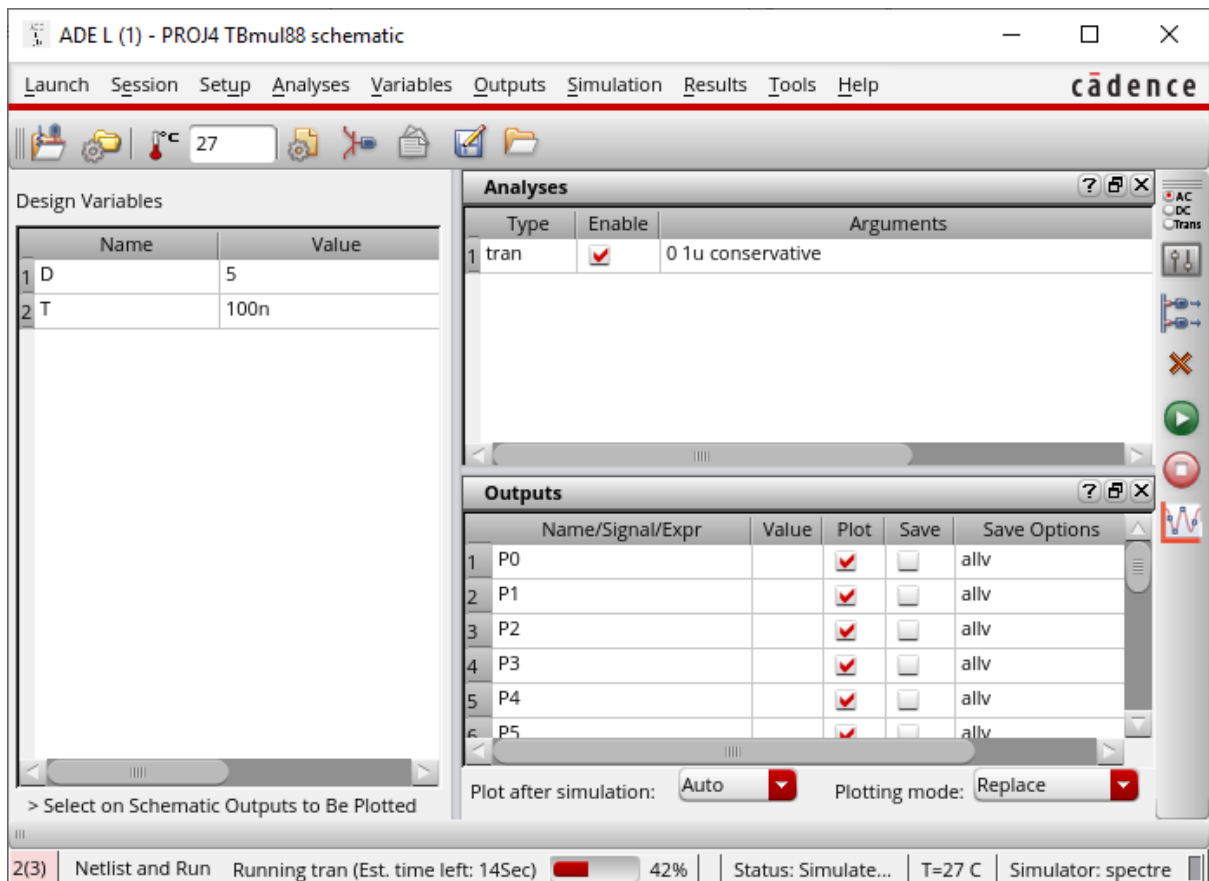



TBmul88 schematic ADE L

   

TBmul88 output waveform (schematic only, 10MHz)

The values from the plot matches exactly with the calculated values hence it confirms the circuit works fine.

  
Now we push it hard and decrease T to 10ns from 100ns. (i.e. we increase the frequency becomes 100MHz from 10MHz!)



TBmul88 output waveform (schematic only, 100MHz)

Propagation delays (schematic only):


F04 Delay	Expression/Remarks	Value
$t_{pd} (P0)$	P0 is constant	N/A
$t_{pd} (P1)$	P1 is constant	N/A
$t_{pd} (P2)$	P2 is constant	N/A
$t_{pd} (P3)$	P3 is constant	N/A
$t_{pd} (P4)$	1.79E-9	1.79ns
$t_{pd} (P5)$	1.795E-9	1.795ns
$t_{pd} (P6)$	568.9E-12	568.9ps
$t_{pd} (P7)$	1.781E-9	1.781ns
$t_{pd} (P8)$	793.8E-12	793.8ps
$t_{pd} (P9)$	1.419E-9	1.419ns
$t_{pd} (P10)$	1.423E-9	1.423ns
$t_{pd} (P11)$	1.42E-9	1.42ns
$t_{pd} (P12)$	1.42E-9	1.42ns
$t_{pd} (P13)$	1.435E-9	1.435ns
$t_{pd} (P14)$	1.413E-9	1.413ns
$t_{pd} (P15)$	1.336E-9	1.336ns

 


Therefore, the worst-case input-output 50%-50% propagation delay for schematic-only simulation came to be **1.795ns**.

Since we kept the value of D as 1 (5V), hence the lowermost bits remain constant which depends only on the values of A0, B0...A3, B3 and hence the summed values are either constant at 1 or at 0, as evident from the waveform.


Part F

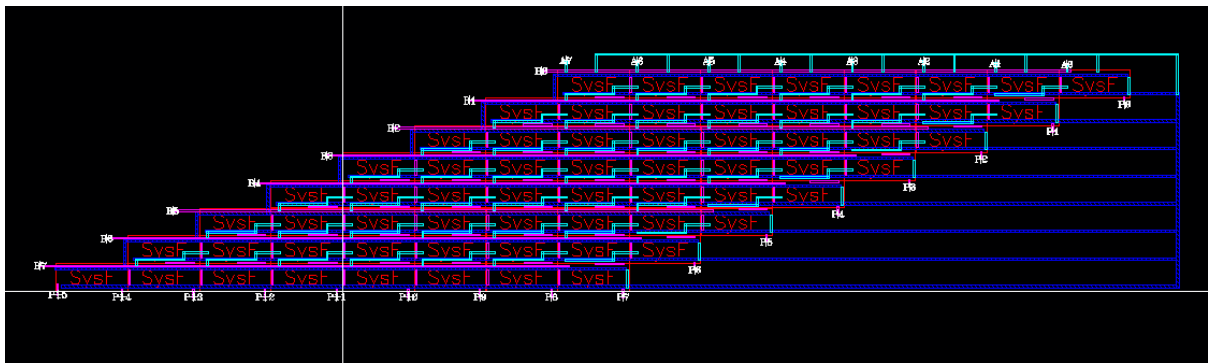


Mult8x8 layout (Top Level)

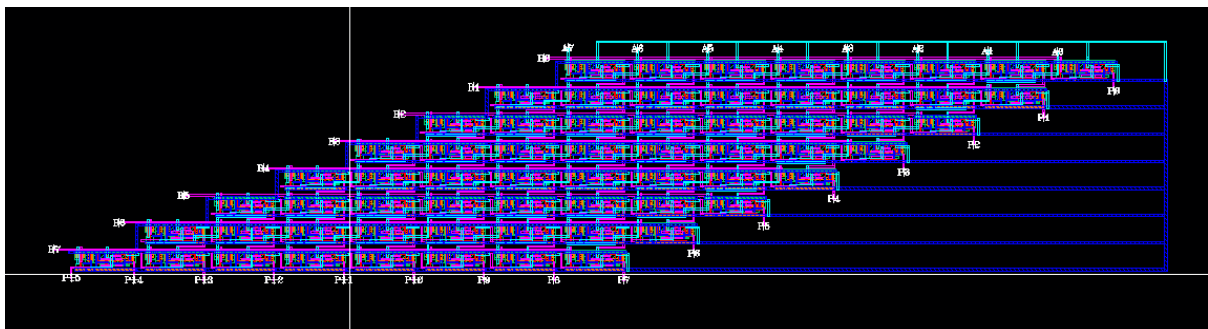

Mult8x8 layout (Lower Level)

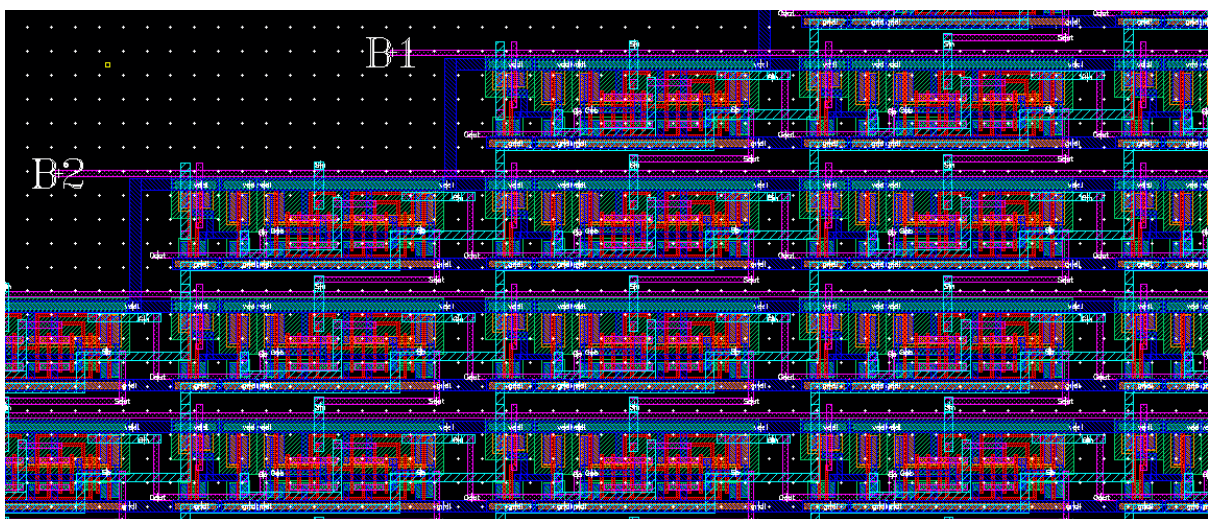

Mult8x8 layout (zoomed in)

 

Mult8x8 layout (further zoomed in)

DRC
✕

Checking Method
☒ flat
☐ hierarchical
☐ hier w/o optimization

Checking Limit
☒ full
☐ incremental
☐ by area

Coordinate
Sel by Cursor

Switch Names
Set Switches

Run-Specific Command File
☐

Inclusion Limit
Limit Rule Errors
☐

Join Nets With Same Name
☒
Limit Run Errors
☐

Echo Commands
☐

Rules File

Rules Library
☒



Machine
☒ local
☐ remote
Machine



Ignore Missing Cell Masters
☐

OK
Cancel
Defaults
Apply
Help


```

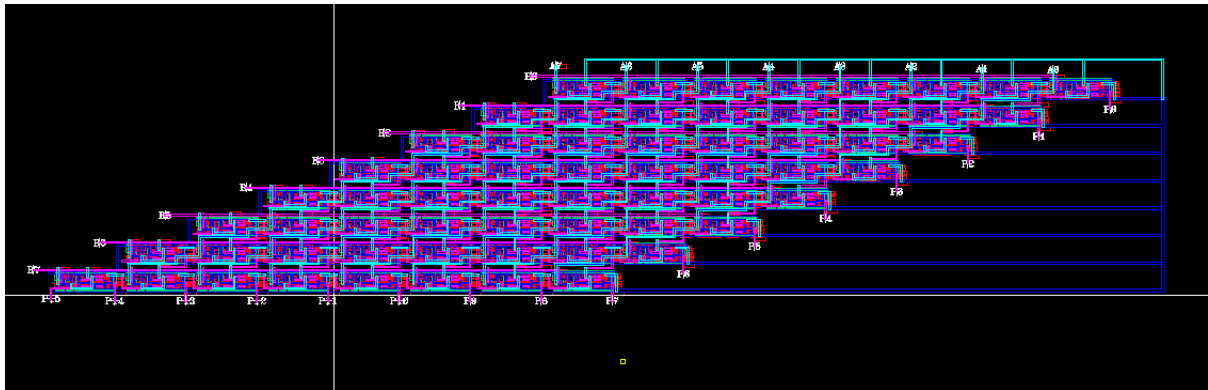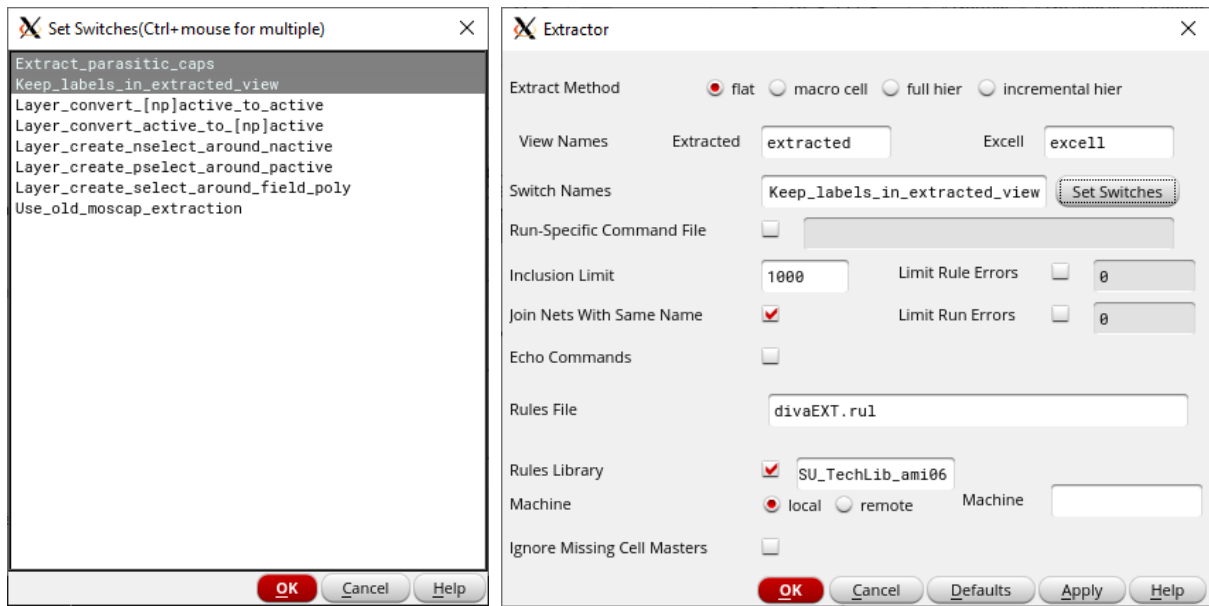DRC started.....Sat Dec 14 21:10:05 2019
completed ....Sat Dec 14 21:10:06 2019
CPU TIME = 00:00:00 TOTAL TIME = 00:00:01
***** Summary of rule violations for cell "Mult8x8 layout" *****
Total errors found: 0
  
```



 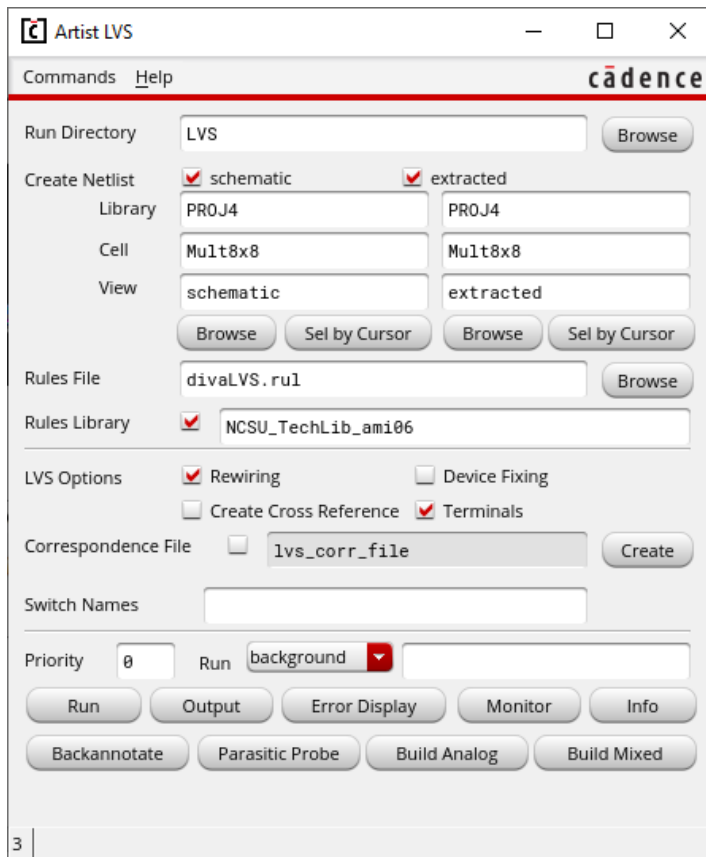

The net-lists match for Mult8x8!

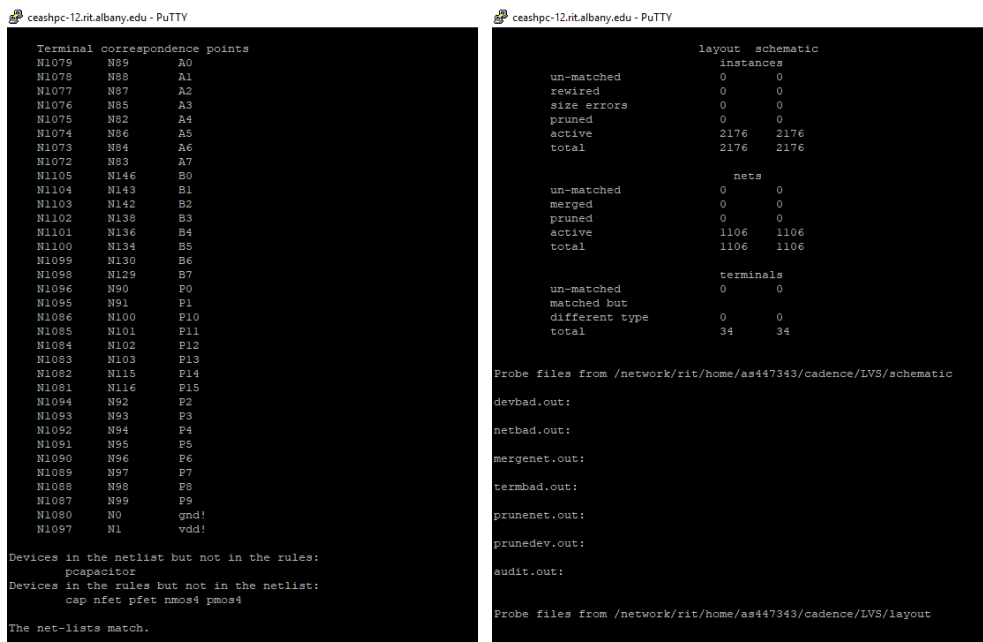

We do **cat si.out** to check the LVS file from the terminal.

Artist LVS [X] [] [X]

Commands Help **cadence**

Run Directory: LVS [Browse]

Create Netlist: ☒ schematic ☒ extracted

Library: PROJ4 PROJ4

Cell: SysF SysF

View: schematic extracted

[Browse] [Sel by Cursor] [Browse] [Sel by Cursor]

Rules File: divaLVS.ru1 [Browse]

Rules Library: ☒ NCSU_TechLib_am106

LVS Options: ☒ Rewiring ☐ Device Fixing
☐ Create Cross Reference ☒ Terminals

Correspondence File: ☐ lvs_corr_file [Create]

Switch Names: []

Priority: 0 Run: background [v]

[Run] [Output] [Error Display] [Monitor] [Info]

[Backannotate] [Parasitic Probe] [Build Analog] [Build Mixed]

22

[X] [X]

The LVS job has completed. The net-lists match.

Run Directory: /network/rit/home/as447343/cadence/LVS

[Close]

Artist LVS [X] [] [X]

Commands Help **cadence**

Run Directory: LVS [Browse]

Create Netlist: ☒ schematic ☒ extracted

Library: PROJ4 PROJ4

Cell: SysF SysF

View: schematic analog_extracted

[Browse] [Sel by Cursor] [Browse] [Sel by Cursor]

Rules File: divaLVS.ru1 [Browse]

Rules Library: ☒ NCSU_TechLib_am106

LVS Options: ☒ Rewiring ☐ Device Fixing
☐ Create Cross Reference ☒ Terminals

Correspondence File: ☐ lvs_corr_file [Create]

Switch Names: []

Priority: 0 Run: background [v]

[Run] [Output] [Error Display] [Monitor] [Info]


[Backannotate] [Parasitic Probe] [Build Analog] [Build Mixed]

22

[X] Build Analog Extracted View [X]

Extracted Parasitics: ☒ Include All ☐ Set From Schematic ☐ None

[OK] [Cancel] [Defaults] [Apply] [Help]

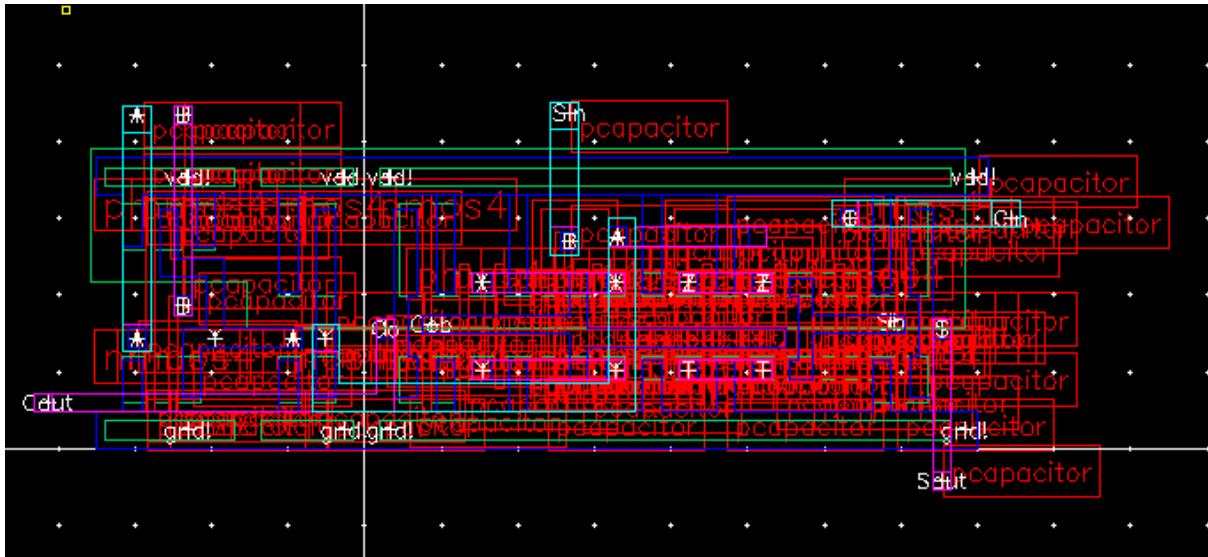

SysF analog extracted view

So now, we will simulate the TBmul88 using config view under the same parameters (i.e. $T = 10\text{ns}$ and $D = 5\text{V}$) and check the delay.

New Configuration

×

Top Cell

Library: PROJ4

Cell: TBmul88

View: schematic

Global Bindings

Library List: myLib

View List: :ctre cmos_sch cmos.sch schematic veriloga ahdl pspice dspf

Stop List: spectre

Constraint List:

Description

Default template for spectre

Note:


Please remember to replace Top Cell Library, Cell, and View fields with the actual names used by your design.

OK

Cancel


Use Template

Help

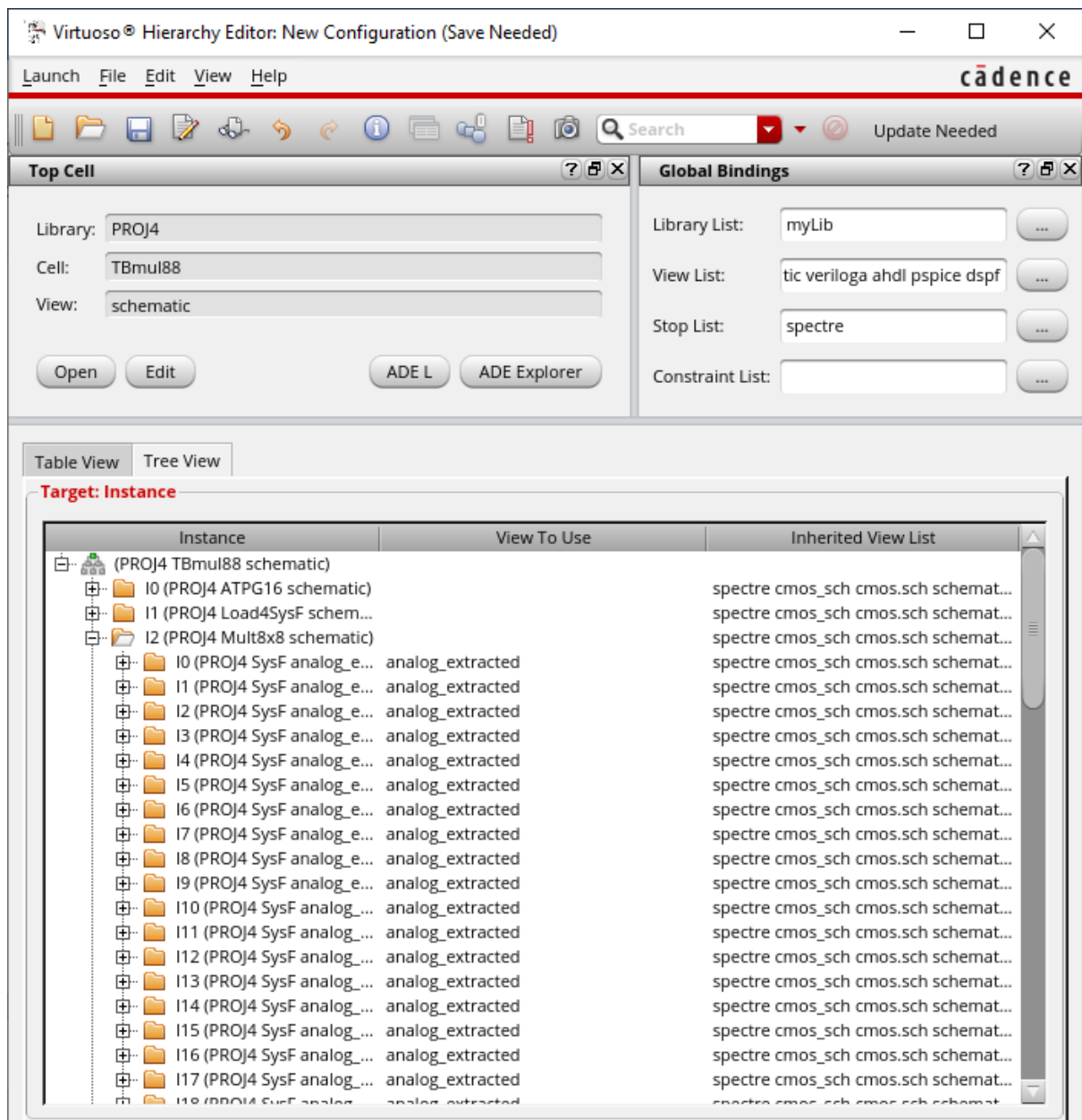

TBmul88 tree view

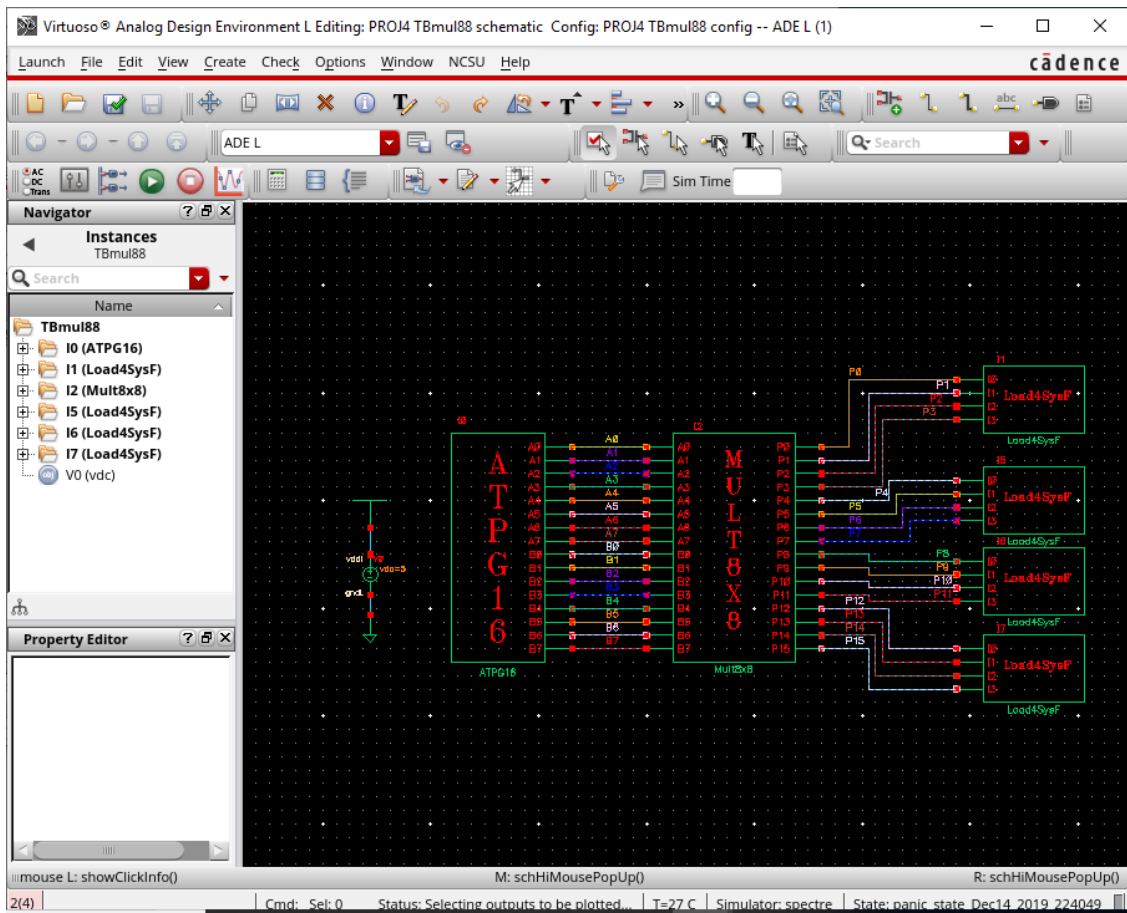We set the view for all the SysF to use as analog_extracted and simulate the circuit.



ADE L (1) - PROJ4 TBmul88 config

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Help

Navigation icons: 27, Plot, Save, Print, etc.

Design Variables

Name	Value
1 D	5
2 T	10n

> Select on Schematic Outputs to Be Plotted

Analyses

Type	Enable	Arguments
1 tran	<input checked="" type="checkbox"/>	0 100n conservative

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Option
12 A4		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
13 A3		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
14 A2		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
15 A1		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
16 A0		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
17 P15		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv


Plot after simulation: Auto Plotting mode: Replace

3(5) Netlis (Est. time left: 0Sec) 2% Status: Simulate... T=27 C Simulator: spectre State: panic_state_Dec14

TBmul88 config ADE L

Propagation delays (including parasitics):

F04 Delay	Expression/Remarks	Value
t_{pd} (P0)	P0 is constant	N/A
t_{pd} (P1)	P1 is constant	N/A
t_{pd} (P2)	P2 is constant	N/A
t_{pd} (P3)	P3 is constant	N/A
t_{pd} (P4)	1.706E-9	1.706ns
t_{pd} (P5)	1.709E-9	1.709ns
t_{pd} (P6)	1.689E-9	1.689ns
t_{pd} (P7)	1.698E-9	1.698ns
t_{pd} (P8)	723.5E-12	723.5ps
t_{pd} (P9)	1.151E-9	1.151ns
t_{pd} (P10)	1.117E-9	1.117ns
t_{pd} (P11)	1.12E-9	1.12ns
t_{pd} (P12)	1.134E-9	1.134ns
t_{pd} (P13)	1.154E-9	1.154ns
t_{pd} (P14)	1.764E-9	1.764ns
t_{pd} (P15)	1.966E-9	1.966ns

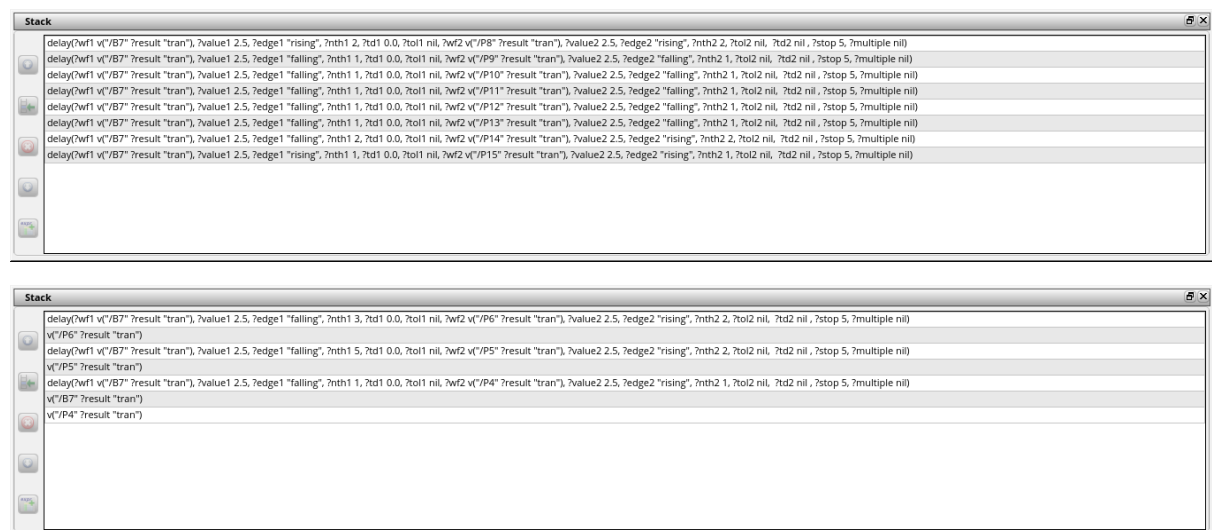

Therefore, the worst-case input-output 50%-50% propagation delay for schematic-only simulation came to be **1.966ns** which is worse than the schematic-only output. Though all the individual delays are not higher, but the worst-case delay is more compared to the previous value. It is very normal that layout parasitics, that too in a huge circuit like this will increase the propagation delay.

Since we kept the value of D as 1 (5V), hence the lowermost bits remain constant which depends only on the values of A0, B0...A3, B3 and hence the summed values are either constant at 1 or at 0, as evident from the waveform.