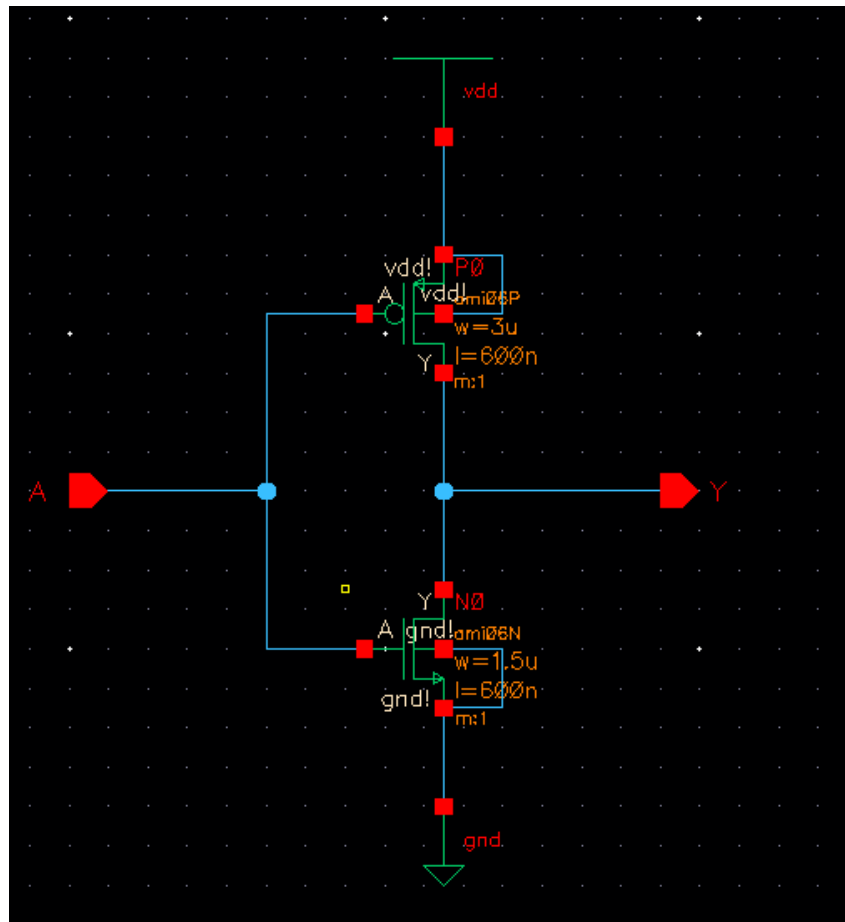


ECE520 Introduction to VLSI, Project 3


Name: Arijit Sengupta, ID: 001441748

PART A


INVX1:



INVX1 Schematic

 


INVX1 Symbol

 


INVX1 Layout


INVX2:

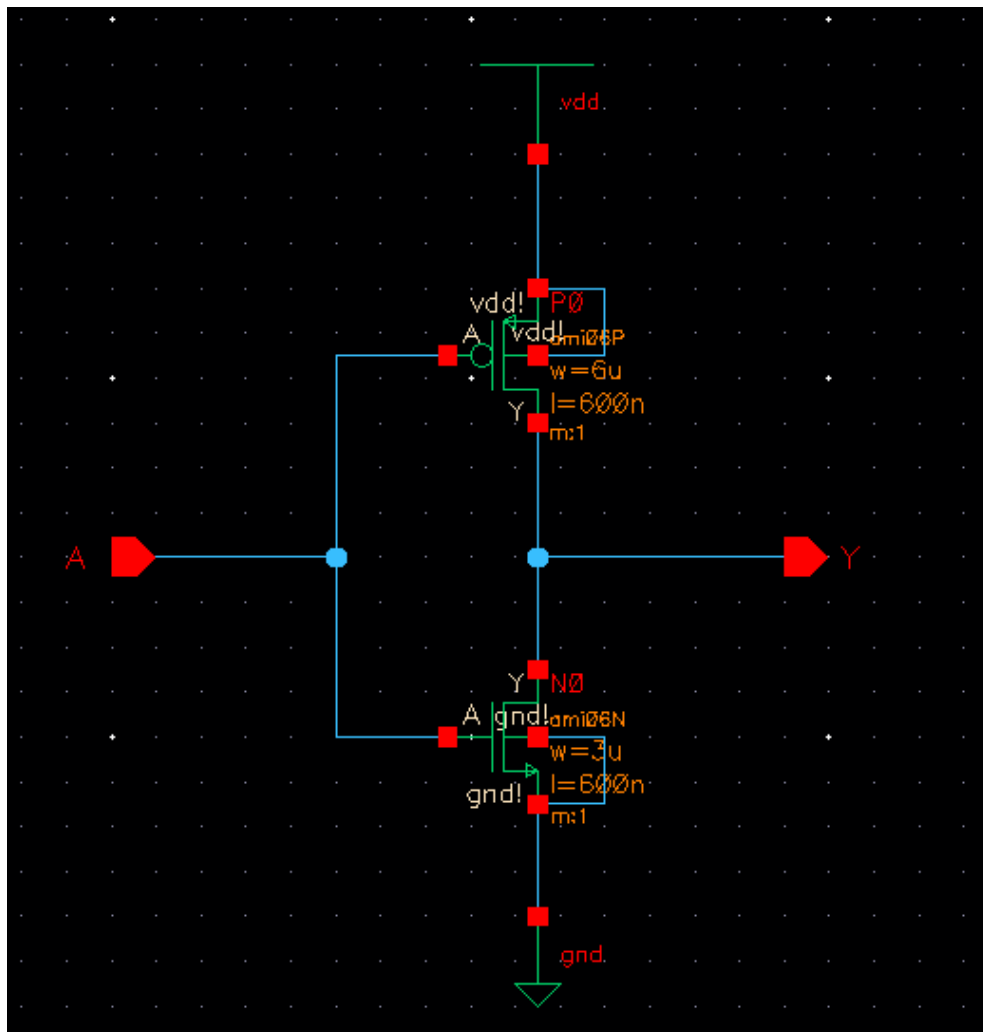

INVX2 Schematic

 


INVX2 Symbol

 


INVX2 Layout


INVX4:

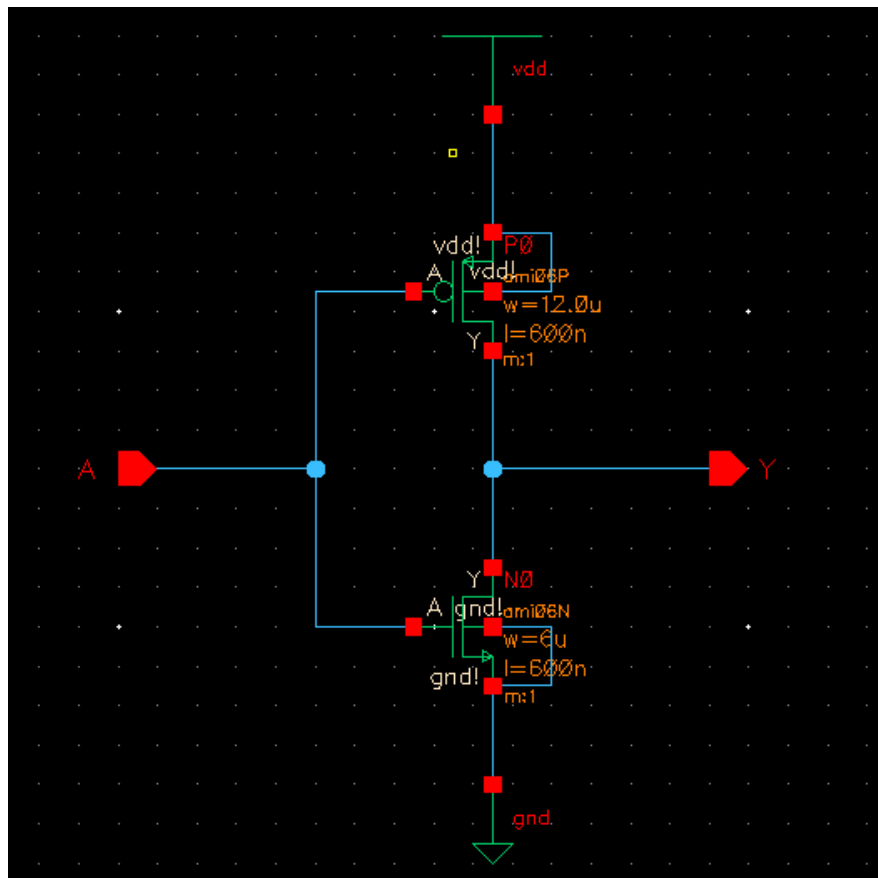

INVX4 Schematic

 


INVX4 Symbol

 


INVX4 Layout

PART B


TBinV1:

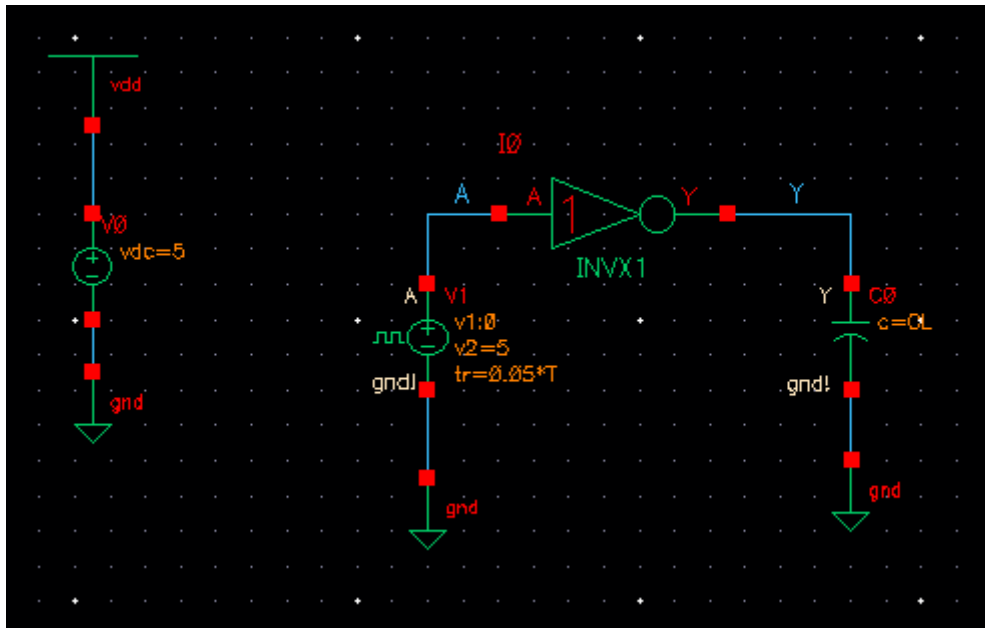

TBinV1 schematic

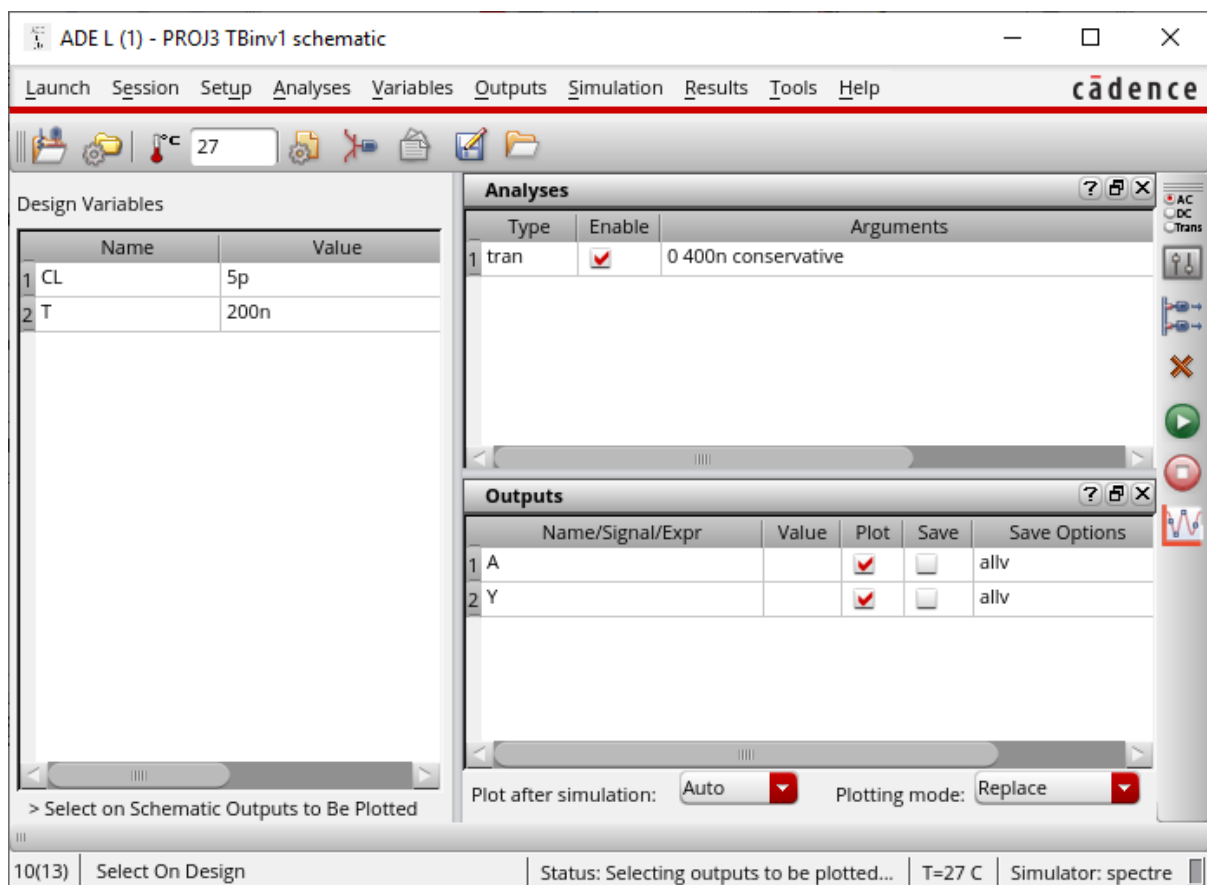

TBinV1 ADE L

 

TBinV1 output


Propagation delays:

$$t_{\text{pdr}} (A \rightarrow Y) = 28.7\text{E-}9 = \mathbf{28.7\text{ns}}$$


$$t_{\text{pdf}} (A \rightarrow Y) = 19.94\text{E-}9 = \mathbf{19.94\text{ns}}$$

Stack	
	delay(wf1 v("A") ?result "tran"), ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("Y") ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
	delay(wf1 v("A") ?result "tran"), ?value1 2.5, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("Y") ?result "tran"), ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
	v("A") ?result "tran")
	v("Y") ?result "tran")


TBinV2:

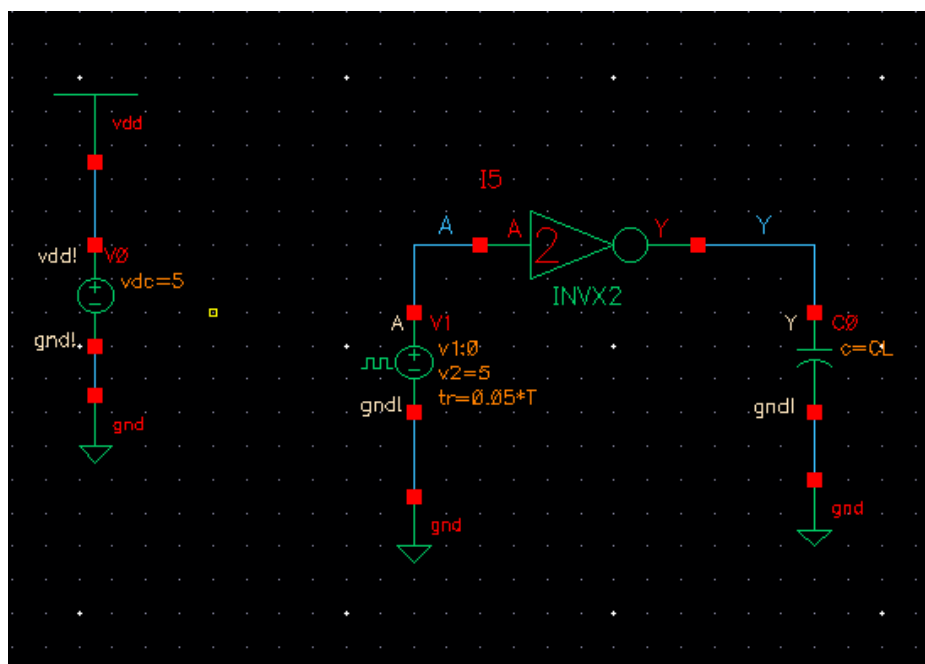

TBinV2 schematic

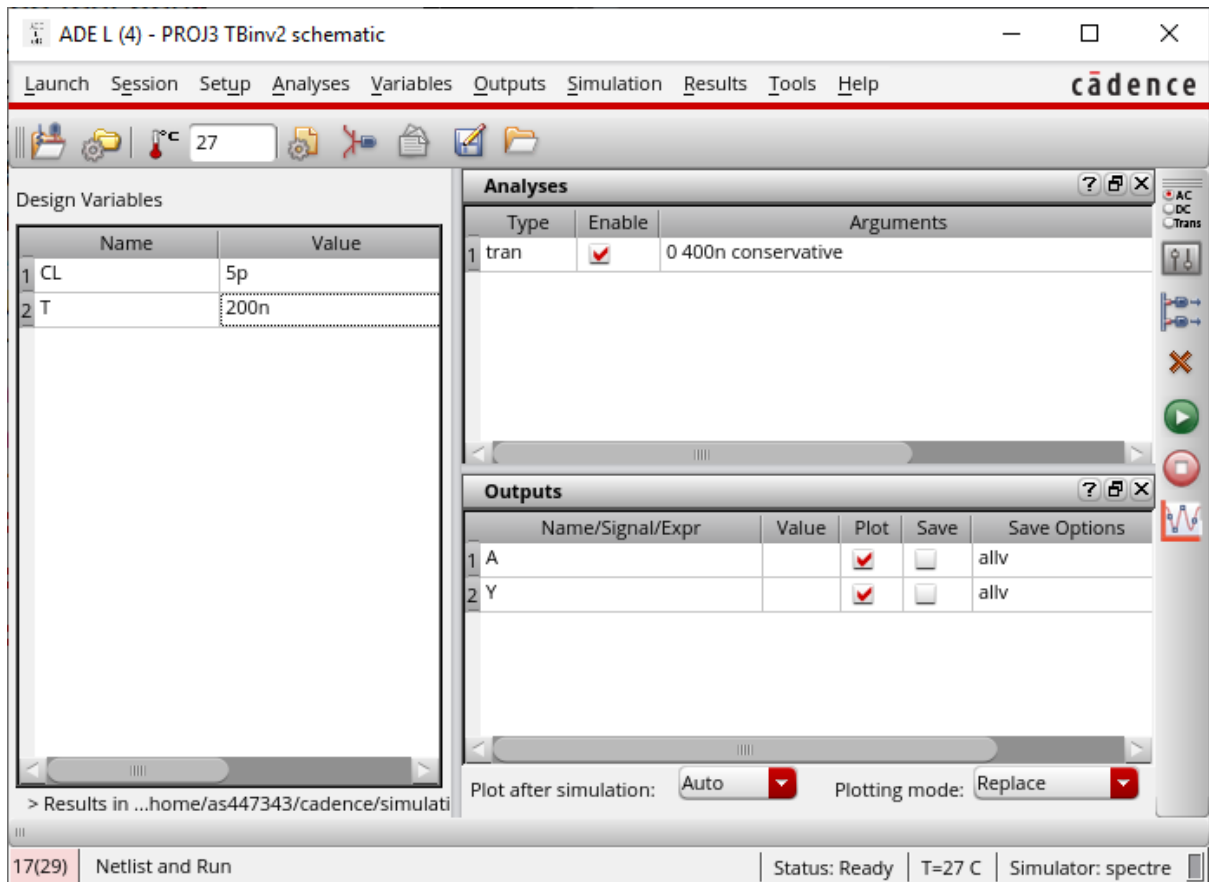

TBinV2 ADE L

 





TBinV2 output


Propagation delays:

$$t_{\text{pdr}}(A \rightarrow Y) = 12.34\text{E-}9 = \mathbf{12.34\text{ns}}$$


$$t_{\text{pdf}}(A \rightarrow Y) = 10.22\text{E-}9 = \mathbf{10.22\text{ns}}$$

 Stack	
	delay(?wf1 v("/A" ?result "tran"), ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/Y" ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
	delay(?wf1 v("/A" ?result "tran"), ?value1 2.5, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/Y" ?result "tran"), ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
	v("/Y" ?result "tran")
	v("/A" ?result "tran")


TBinV4:

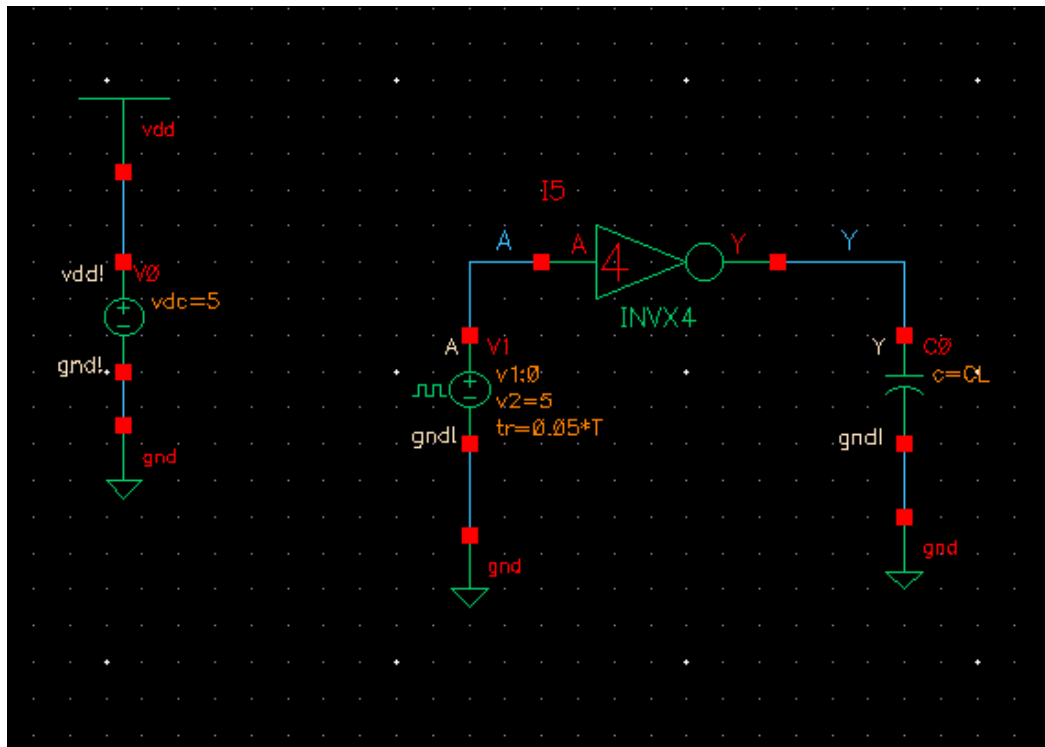

TBinV4 schematic

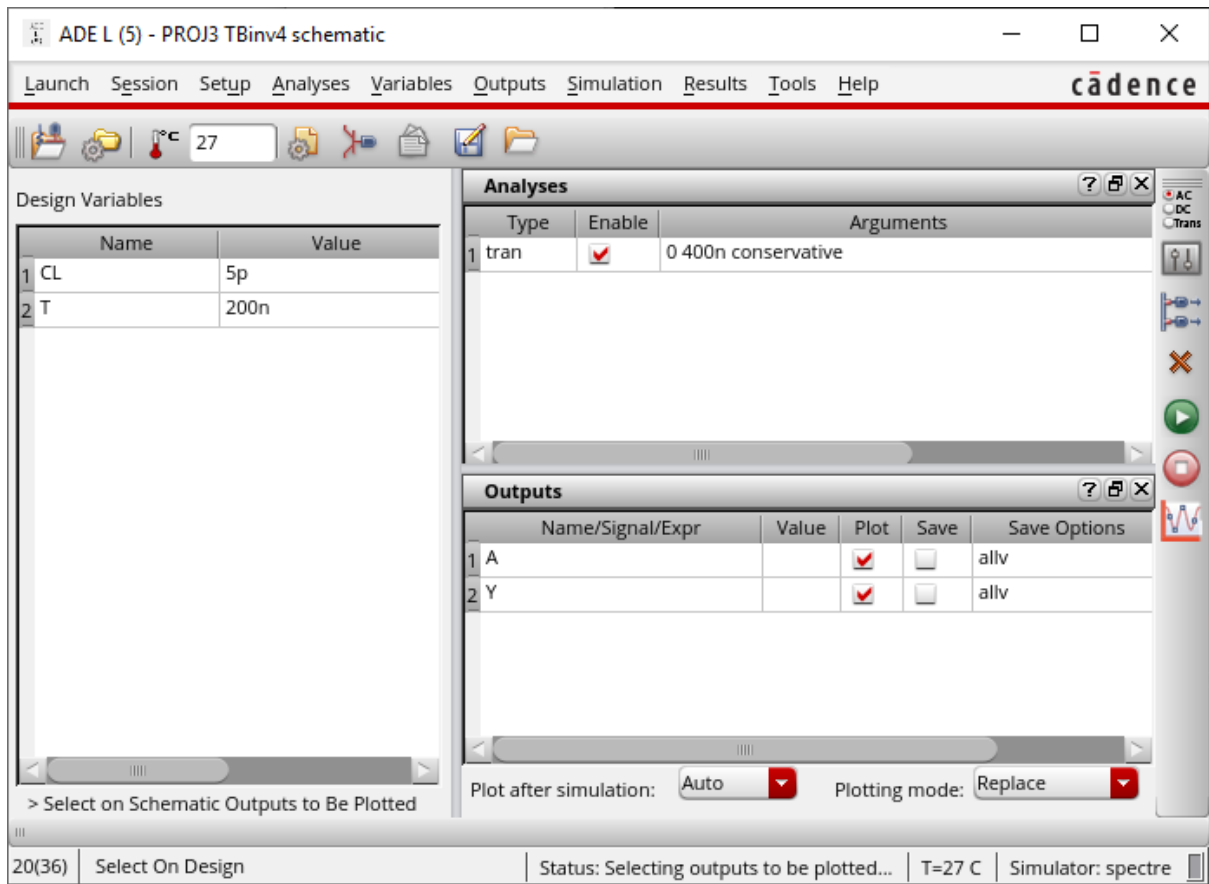

TBin4 ADE L

 





TBin4 output


Propagation delays:

$$t_{\text{pdr}}(A \rightarrow Y) = 6.296\text{E-}9 = \mathbf{6.296\text{ns}}$$


$$t_{\text{pdf}}(A \rightarrow Y) = 5.795\text{E-}9 = \mathbf{5.795\text{ns}}$$

Stack	
	delay(?wf1 v("/A" ?result "tran"), ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/Y" ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
	delay(?wf1 v("/A" ?result "tran"), ?value1 2.5, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/Y" ?result "tran"), ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
	v("/A" ?result "tran")
	v("/Y" ?result "tran")


PART C

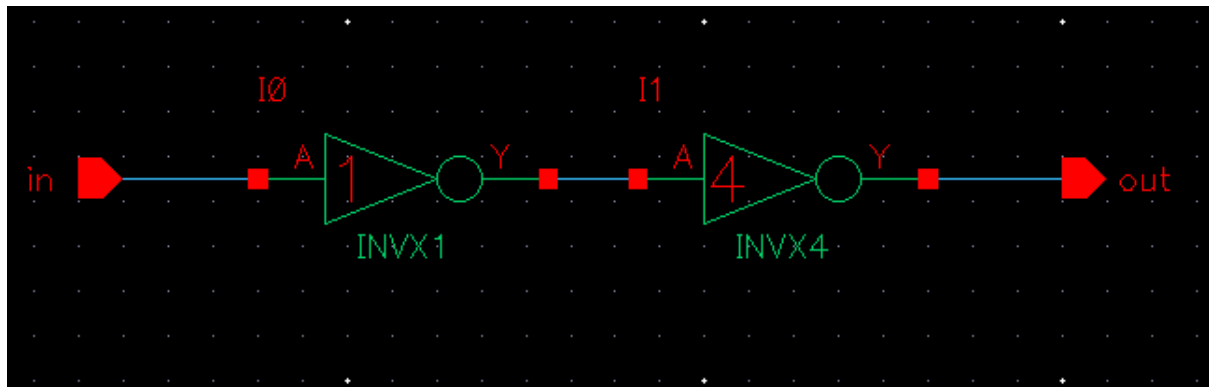


bufX14 schematic

 


bufX14 symbol

 

bufX14 Layout (Top Level)

 

bufX14 layout (Lower Level)

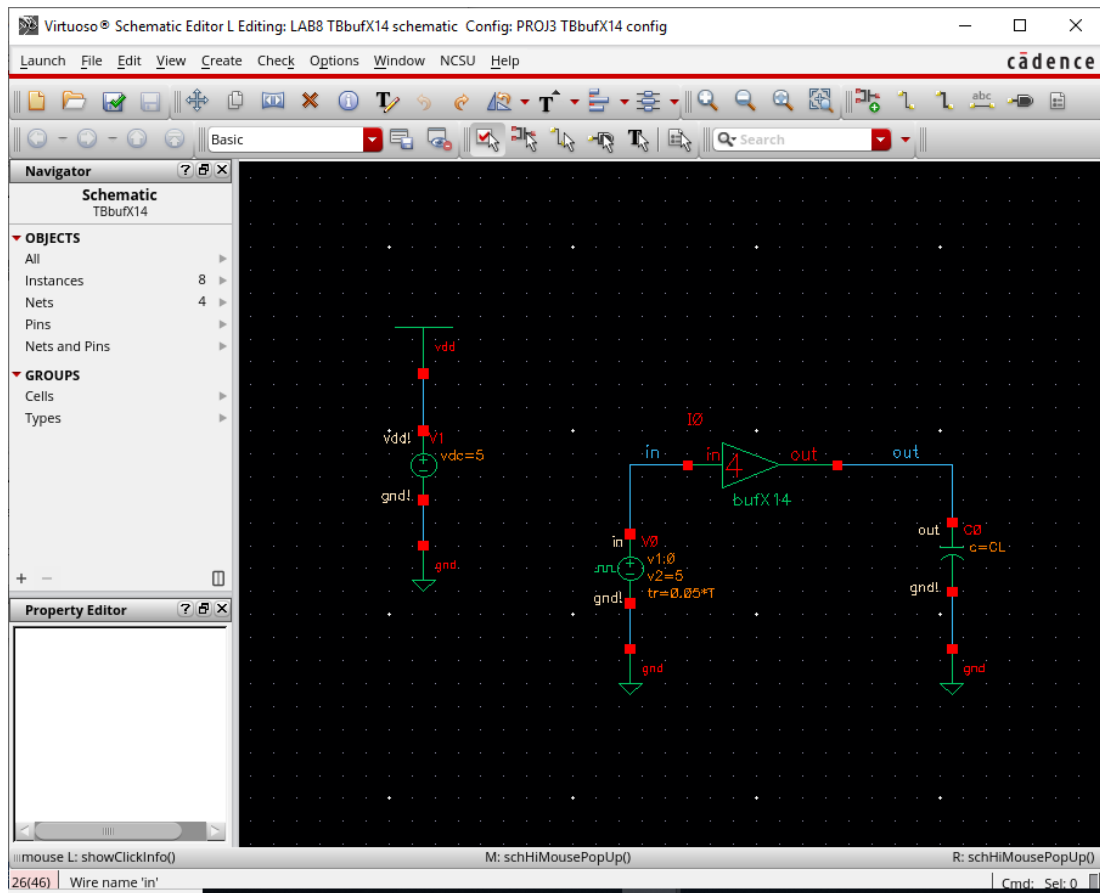

TBbufX14 schematic view (config)

ADE L (6) - PROJ3 TBbufX14 config

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Help

Design Variables

Name	Value
1 CL	5p
2 T	200n

Analyses

Type	Enable	Arguments
1 tran	<input checked="" type="checkbox"/>	0 400n conservative


Outputs

Name/Signal/Expr	Value	Plot	Save	Save Options
1 in		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2 out		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv

Plot after simulation: Auto Plotting mode: Replace

27(47) Select On Design Status: Selecting outputs to be plotted... T=27 C Simulator: spectre

TBbufX14 ADE L

 


TBbufX14 output


Propagation delays:

$$t_{\text{pdr}} (\text{in} \rightarrow \text{out}) = 5.803\text{E-}9 = \mathbf{5.803\text{ns}}$$


$$t_{\text{pdf}} (\text{in} \rightarrow \text{out}) = 6.183\text{E-}9 = \mathbf{6.183\text{ns}}$$

Stack	
	delay(?wf1 v("/in" ?result "tran"), ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/out" ?result "tran"), ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
	delay(?wf1 v("/in" ?result "tran"), ?value1 2.5, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/out" ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
	v("/in" ?result "tran")
	v("/out" ?result "tran")

 
INVX8:

 


INVX8 Layout

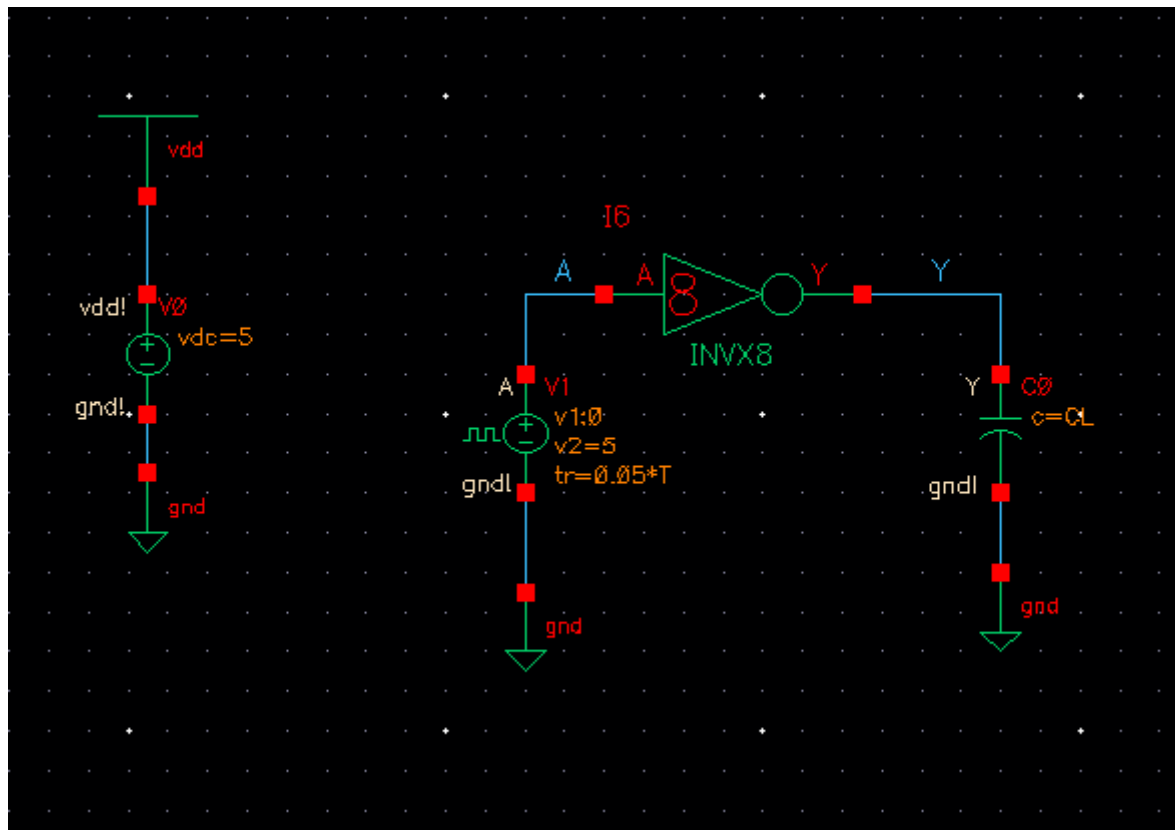

TBinV8 schematic

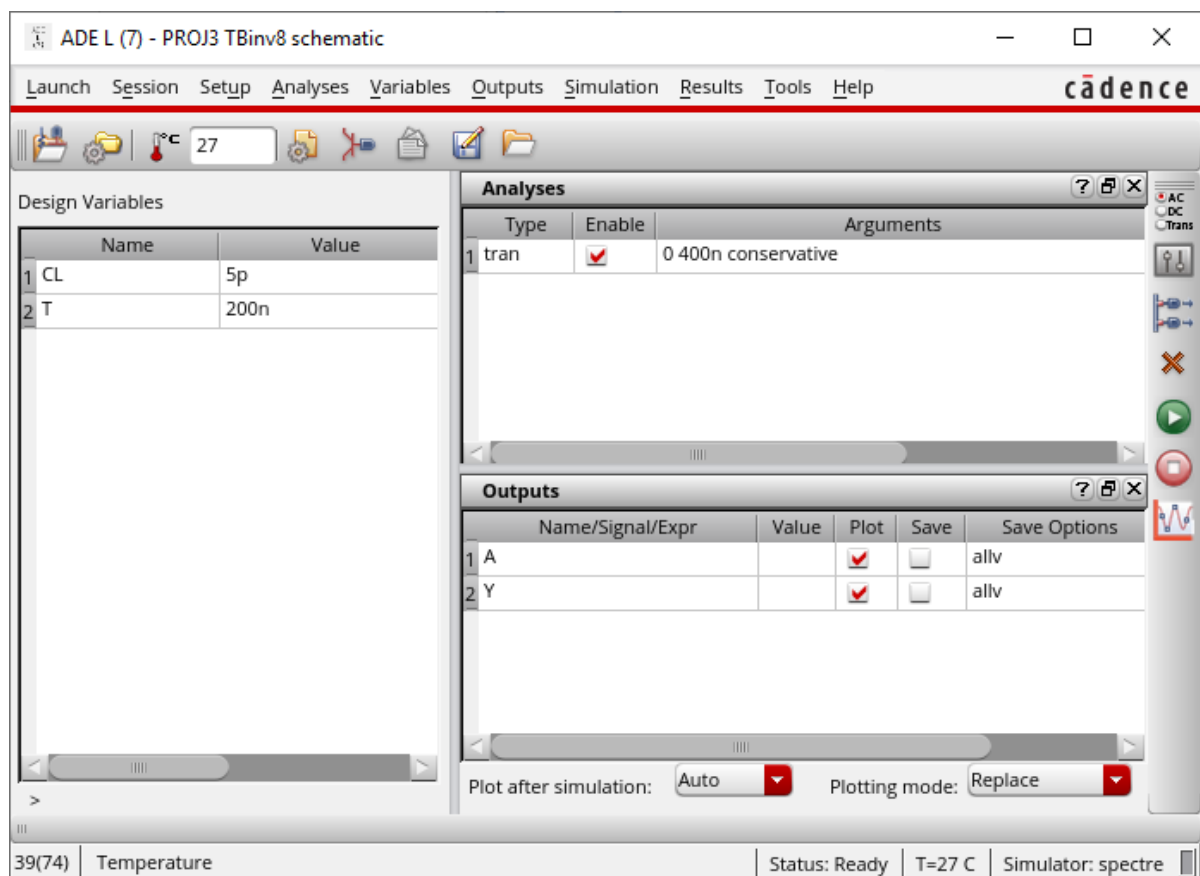

TBinV8 ADE L

 


TBinV8 output

Propagation delays:


$$t_{\text{pdr}} (A \rightarrow Y) = 3.725\text{E-}9 = \mathbf{3.725\text{ns}}$$

$$t_{\text{pdf}} (A \rightarrow Y) = 3.681\text{E-}9 = \mathbf{3.681\text{ns}}$$


PART E

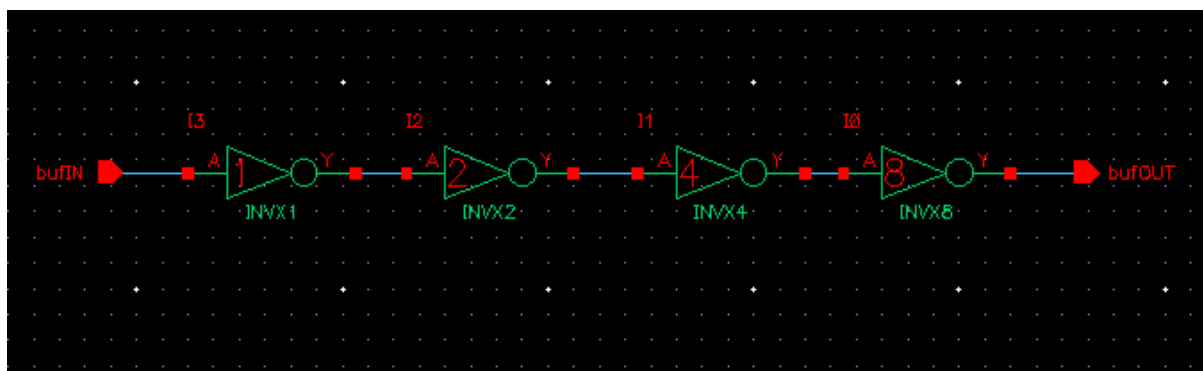


bufX1248 schematic

 


bufX1248 symbol

 


bufX1248 layout (Top Level)

 


bufX1248 layout (Lower Level)

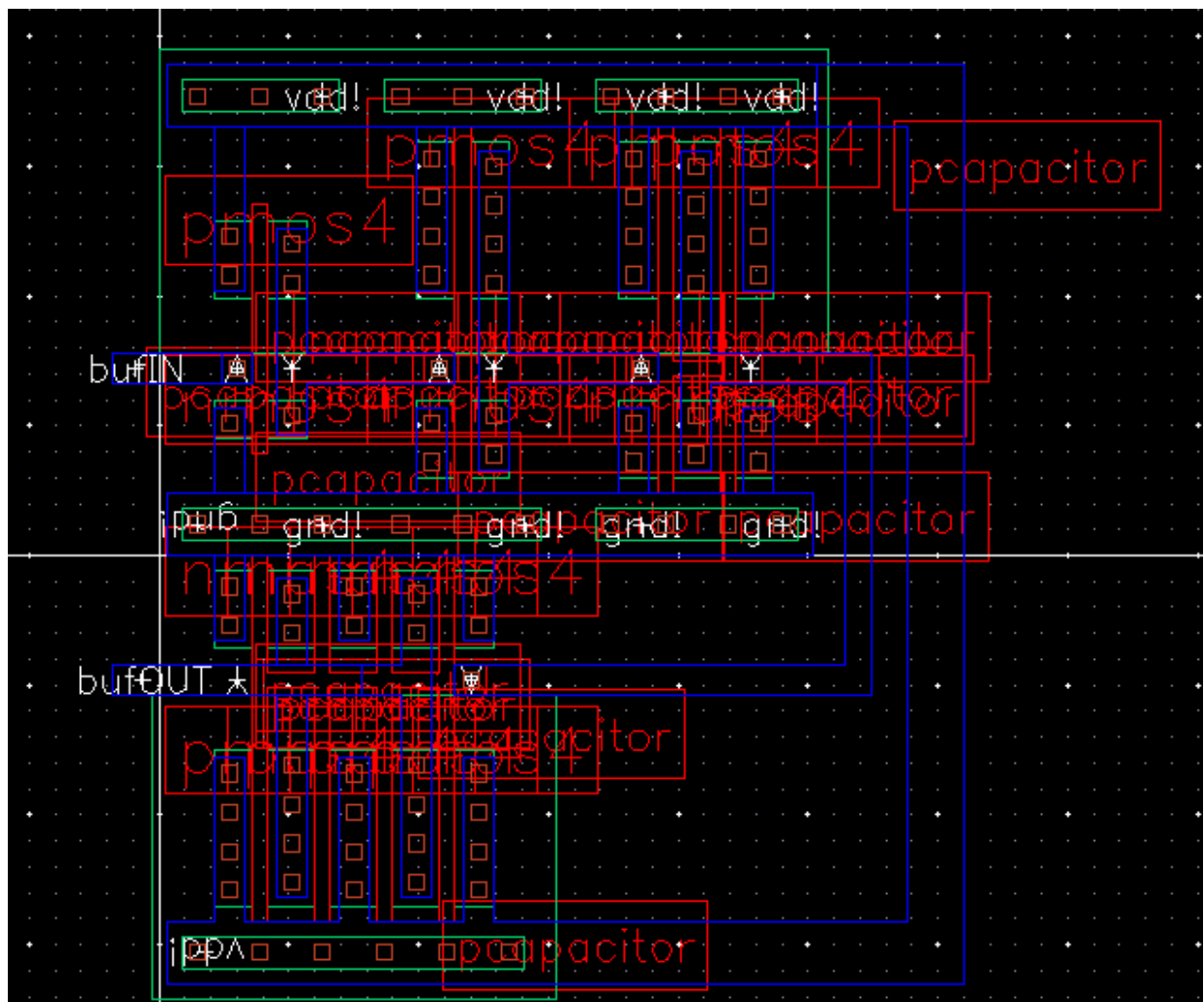


bufX1248 extracted (Top Level)

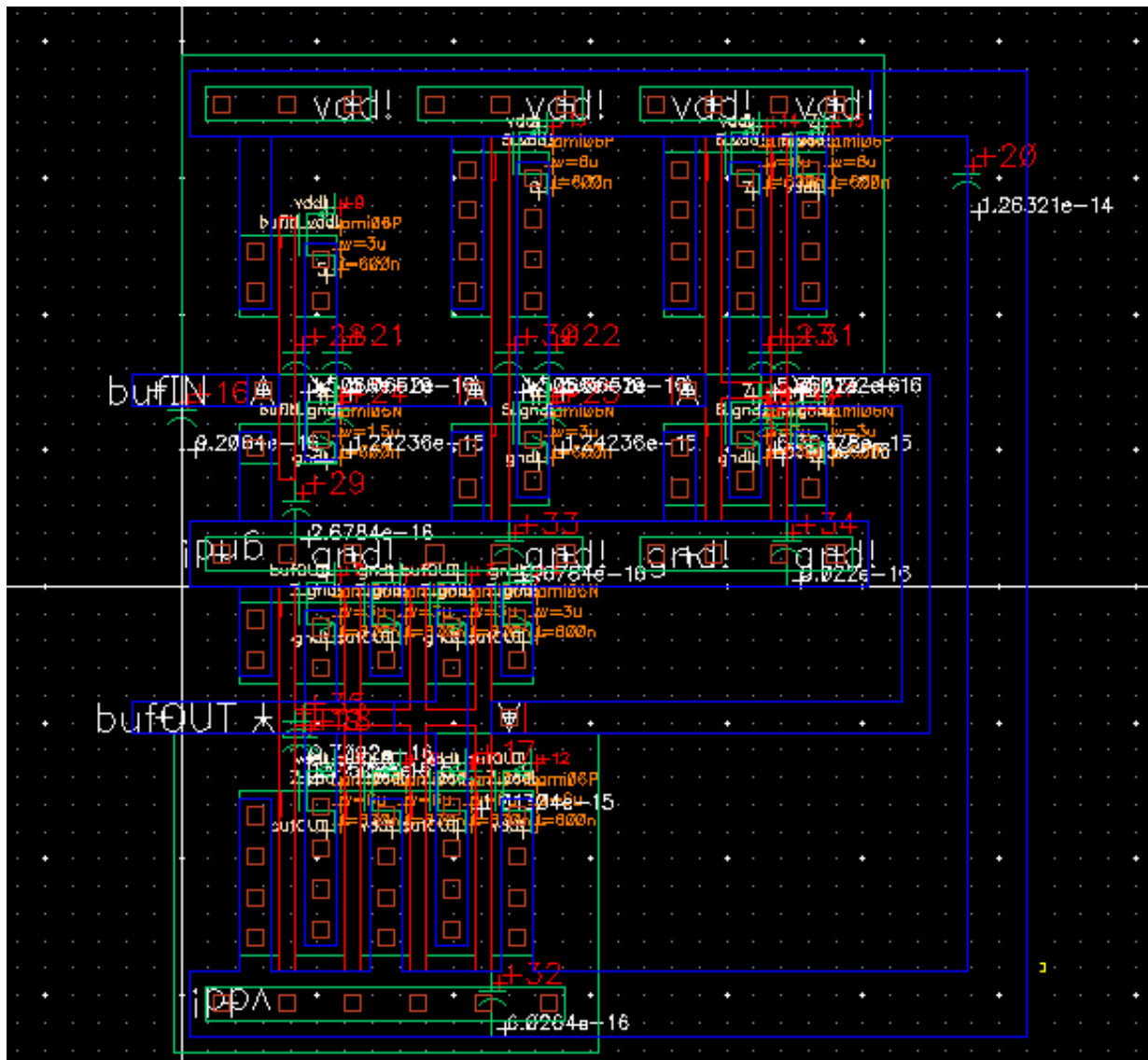

bufX1248 extracted (Lower Level)

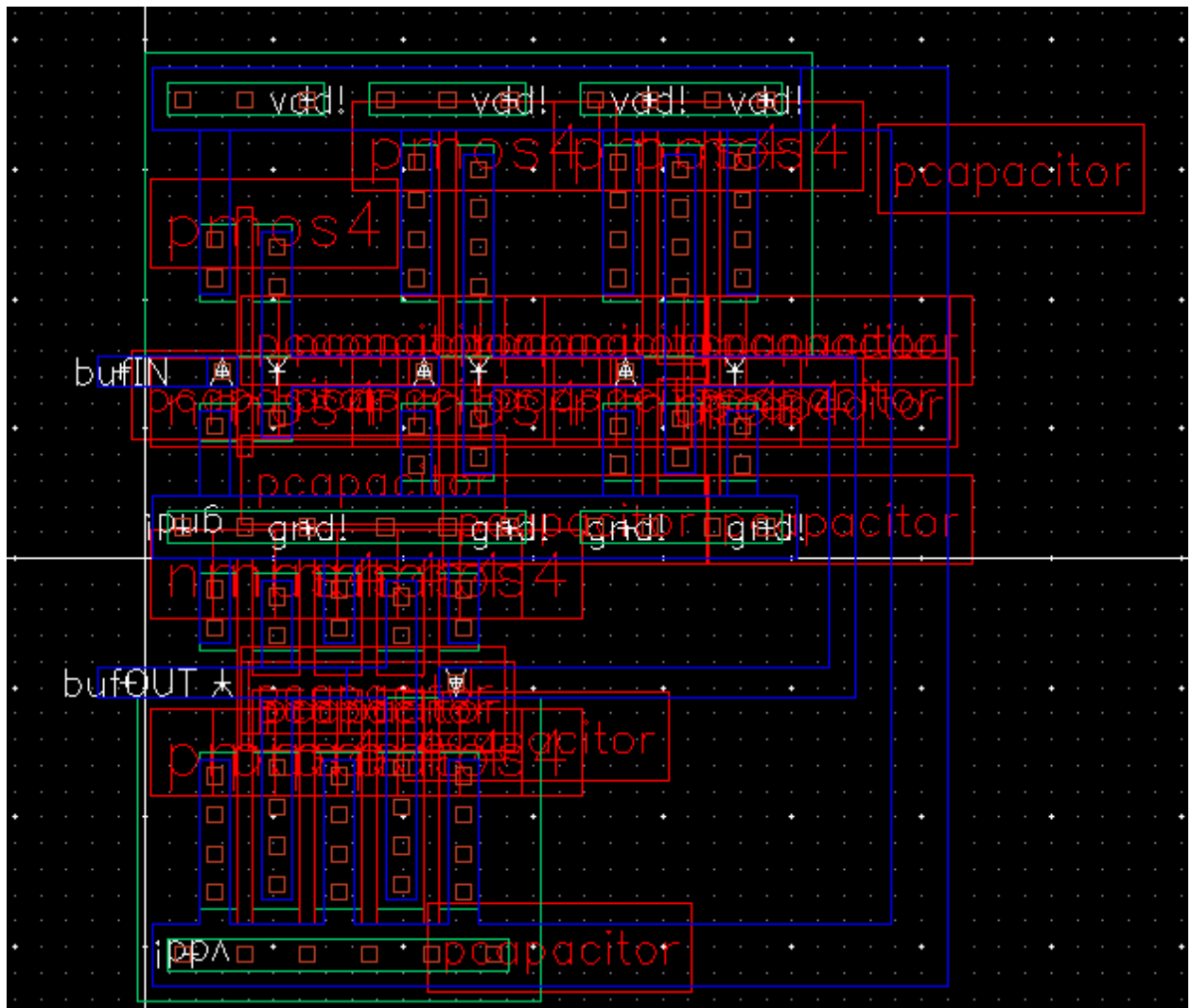

bufX1248 analog extracted (Top Level)

 

bufX1248 analog extracted (Lower Level)

Parasitic capacitor values:

```

ceashpc-12.rit.albany.edu - PuTTY
; pcapacitor Instance /+35 = auLvs device C7
d pcapacitor PLUS MINUS (p PLUS MINUS)
i 7 pcapacitor 3 0 " c 970.92e-18 "

; pcapacitor Instance /+34 = auLvs device C8
i 8 pcapacitor 3 1 " c 502.2e-18 "

; pcapacitor Instance /+33 = auLvs device C9
i 9 pcapacitor 3 2 " c 267.84e-18 "

; pcapacitor Instance /+32 = auLvs device C10
i 10 pcapacitor 4 0 " c 602.64e-18 "

; pcapacitor Instance /+31 = auLvs device C11
i 11 pcapacitor 4 1 " c 301.32e-18 "

; pcapacitor Instance /+30 = auLvs device C12
i 12 pcapacitor 4 2 " c 150.66e-18 "

; pcapacitor Instance /+29 = auLvs device C13
i 13 pcapacitor 6 3 " c 267.84e-18 "

; pcapacitor Instance /+28 = auLvs device C14
i 14 pcapacitor 6 4 " c 150.66e-18 "

; pcapacitor Instance /+27 = auLvs device C15
i 15 pcapacitor 1 0 " c 511.5e-18 "

; pcapacitor Instance /+26 = auLvs device C16
i 16 pcapacitor 3 0 " c 6.39378e-15 "

; pcapacitor Instance /+25 = auLvs device C17
i 17 pcapacitor 3 1 " c 1.24236e-15 "

; pcapacitor Instance /+24 = auLvs device C18
i 18 pcapacitor 3 2 " c 1.24236e-15 "

; pcapacitor Instance /+23 = auLvs device C19
i 19 pcapacitor 4 0 " c 506.52e-18 "

; pcapacitor Instance /+22 = auLvs device C20
i 20 pcapacitor 4 1 " c 506.52e-18 "

; pcapacitor Instance /+21 = auLvs device C21
i 21 pcapacitor 4 2 " c 506.52e-18 "

; pcapacitor Instance /+20 = auLvs device C22
i 22 pcapacitor 4 3 " c 12.6321e-15 "

; pcapacitor Instance /+19 = auLvs device C23
i 23 pcapacitor 5 0 " c 1.4775e-15 "

; pcapacitor Instance /+18 = auLvs device C24
i 24 pcapacitor 5 3 " c 2.15088e-15 "

; pcapacitor Instance /+17 = auLvs device C25
i 25 pcapacitor 5 4 " c 1.01304e-15 "

; pcapacitor Instance /+16 = auLvs device C26
i 26 pcapacitor 6 3 " c 920.64e-18 "

; nmos4 Instance /+7 = auLvs device Q27
d nmos D G S B (p D S)
i 27 nmos 3 1 0 3 " m 1 1 600e-9 w 3e-6 "

; nmos4 Instance /+6 = auLvs device Q28
i 28 nmos 0 1 3 3 " m 1 1 600e-9 w 3e-6 "

; nmos4 Instance /+5 = auLvs device Q29
i 29 nmos 1 2 3 3 " m 1 1 600e-9 w 3e-6 "

; nmos4 Instance /+4 = auLvs device Q30
i 30 nmos 3 0 5 3 " m 1 1 600e-9 w 3e-6 "

; nmos4 Instance /+3 = auLvs device Q31
i 31 nmos 5 0 3 3 " m 1 1 600e-9 w 3e-6 "

; nmos4 Instance /+2 = auLvs device Q32
i 32 nmos 3 0 5 3 " m 1 1 600e-9 w 3e-6 "


; nmos4 Instance /+0 = auLvs device Q33
i 33 nmos 5 0 3 3 " m 1 1 600e-9 w 3e-6 "

; nmos4 Instance /+1 = auLvs device Q34
i 34 nmos 2 6 3 3 " m 1 1 600e-9 w 1.5e-6 "


```

Capacitor Instance ID	Value (F)	From net name	To net name
16	920.64aF	bufIN	A (INVX1)
17	1.01304fF	metal1 connection (Y, INVX4)	A (INVX8)
18	2.15088fF	A (INVX8)	nmos4 (INVX8)
19	1.4775fF	pmos4 (INVX8)	Y (INVX8)
20	12.6321fF	vdd! (top)	vdd! (bottom)
21	506.52aF	pmos4 (INVX1)	Y (INVX1)
22	506.52aF	pmos4 (INVX2)	Y (INVX2)
23	506.52aF	pmos4 (INVX4)	Y (INVX4)
24	1.24236fF	Y (INVX1)	A (INVX2)
25	1.24236fF	Y (INVX2)	A (INVX4)
26	6.39378fF	Y (INVX4)	metal1 connection (A, INVX8)
27	511.5aF	A (INVX4)	nmos4 (INVX4)
28	150.66aF	pmos4 (INVX1)	Y (INVX1)
29	267.84aF	nmos4 (INVX1)	gnd!
30	150.66aF	pmos4 (INVX2)	Y (INVX2)
31	301.32aF	pmos4 (INVX4)	Y (INVX4)
32	602.64aF	vdd! (bottom)	pmos4 (INVX8)
33	267.84aF	nmos4 (INVX2)	gnd!
34	502.2aF	nmos4 (INVX4)	gnd!
35	970.92aF	Y (INVX8)	bufOUT



TBbufX1248:

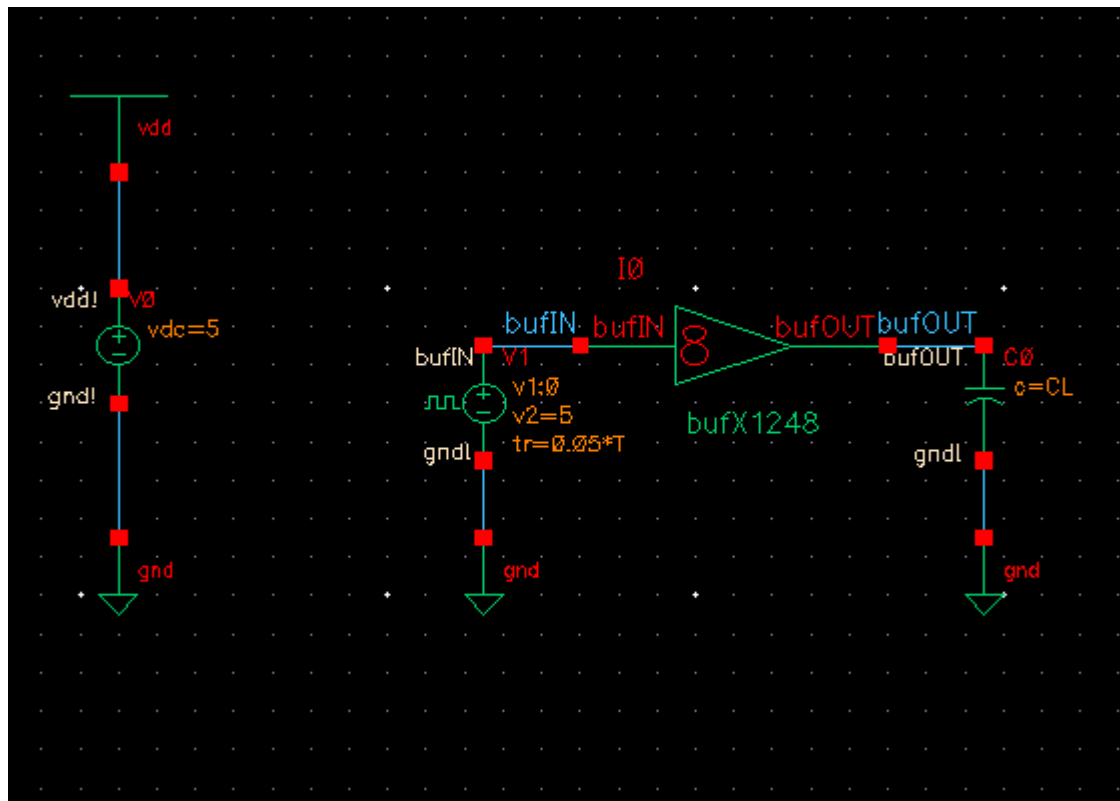

TBbufX1248 schematic

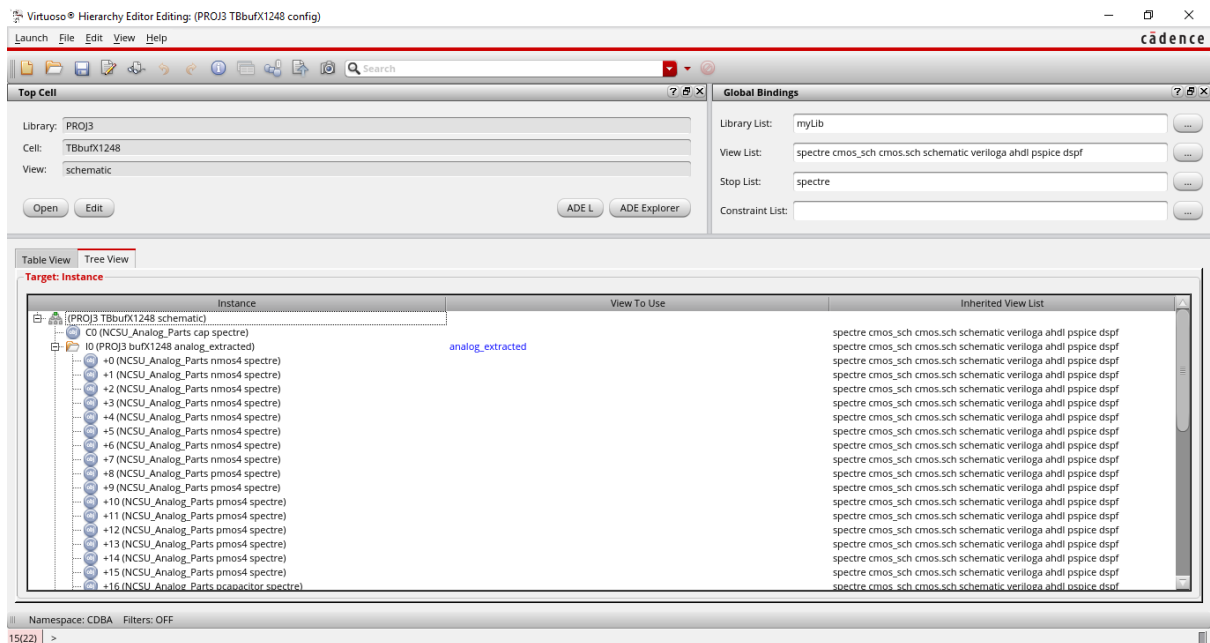


TBbufX1248 config (tree view)

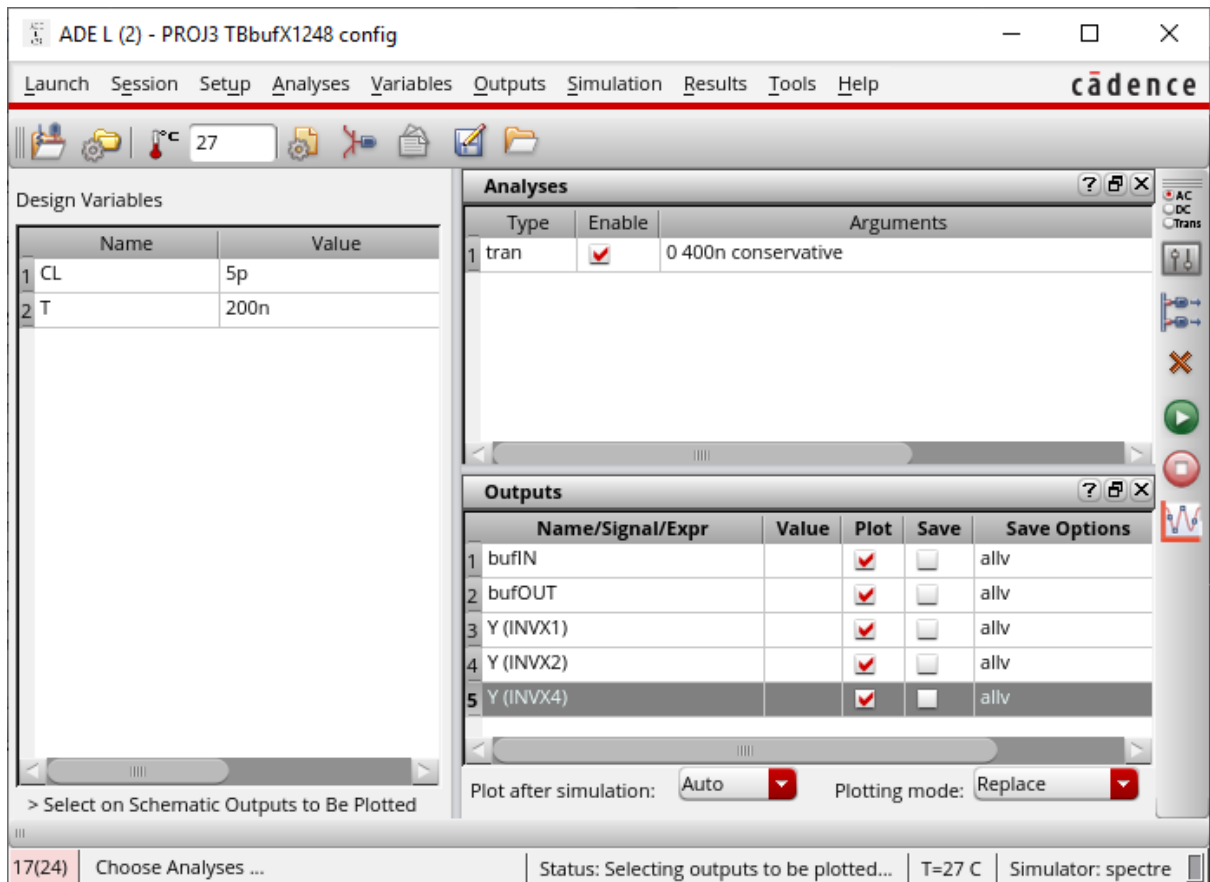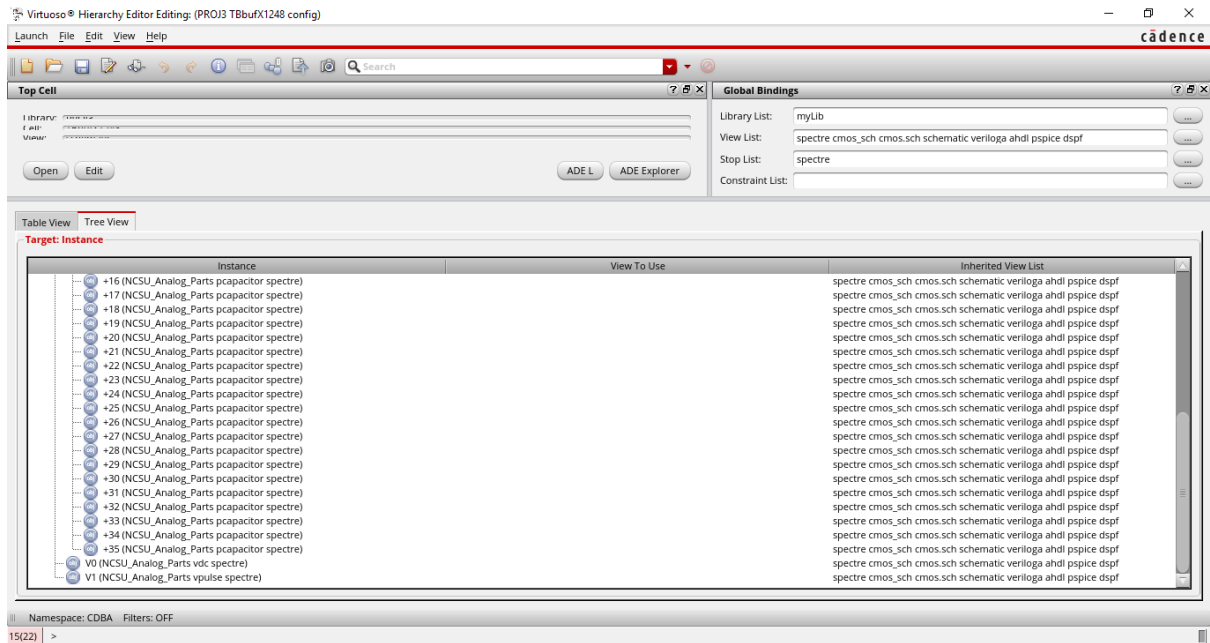

TBbufX1248 ADE L

 For the buffer bufX1248, bufIN \equiv A (INVX1), Y (INVX1) \equiv A (INVX2), Y (INVX2) \equiv A (INVX4), Y (INVX4) \equiv A (INVX8) and Y (INVX8) \equiv bufOUT since they are fed directly and hence not re-plotted. In the output below, net7 represents Y (INVX1), net 6 represents Y (INVX2) and net 5 represents Y (INVX4) respectively. The propagation delays are calculated accordingly.



TBbufX1248 output

Device Name	Expression	Value	Delay (s)
INVX1	$t_{pdr} (A \rightarrow Y)$	1.336E-9	1.336ns
	$t_{pdf} (A \rightarrow Y)$	632.5E-12	632.5ps
INVX2	$t_{pdr} (A \rightarrow Y)$	140.9E-12	140.9ps
	$t_{pdf} (A \rightarrow Y)$	161.0E-12	161.0ps
INVX4	$t_{pdr} (A \rightarrow Y)$	229.2E-12	229.2ps
	$t_{pdf} (A \rightarrow Y)$	268.0E-12	268.0ps
INVX8	$t_{pdr} (A \rightarrow Y)$	3.219E-9	3.219ns
	$t_{pdf} (A \rightarrow Y)$	2.646E-9	2.646ns
bufX1248	$t_{pdr} (bufIN \rightarrow bufOUT)$	3.592E-9	3.592ns
	$t_{pdf} (bufIN \rightarrow bufOUT)$	3.443E-9	3.443ns

Stack
delay(wf1 v"/IO/6" ?result "tran", ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v"/IO/5" ?result "tran", ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(wf1 v"/IO/6" ?result "tran", ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v"/IO/5" ?result "tran", ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(wf1 v"/IO/7" ?result "tran", ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v"/IO/6" ?result "tran", ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(wf1 v"/IO/7" ?result "tran", ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v"/IO/6" ?result "tran", ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(wf1 v"/bufIN" ?result "tran", ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v"/IO/7" ?result "tran", ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(wf1 v"/bufIN" ?result "tran", ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v"/bufOUT" ?result "tran", ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(wf1 v"/bufIN" ?result "tran", ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v"/bufOUT" ?result "tran", ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
Stack
delay(wf1 v"/IO/5" ?result "tran", ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v"/bufOUT" ?result "tran", ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(wf1 v"/IO/5" ?result "tran", ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v"/bufOUT" ?result "tran", ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
v"/IO/6" ?result "tran"
v"/IO/6" ?result "tran"
v"/IO/5" ?result "tran"
v"/bufOUT" ?result "tran"
v"/bufIN" ?result "tran"