 


ECE520: Lab 7 Inverter Analysis

Name: Arijit Sengupta, ID: 001441748


1) Analysing/correcting DRC errors

First, we delete the metal1 layer of input A. Next, we will get the nmos too close to above.




When we verify the design by Verify -> DRC, it shows 5 errors.
 
```
***** Summary of rule violations for cell "badinv layout" *****
# errors  Violated Rules
1  (SCMOS Rule 7.2) metal1 spacing: 0.90 um
1  (SCMOS Rule 7.3) metal1 enclosure of contact: 0.30 um
2  (SCMOS_SUBM Rule 2.3) source/drain active to well edge: 1.80 um
1  cp contact does not connect to two layers
5  Total errors found
```



 The polygon will change its colour to purple, which will highlight which error we are currently analysing.




The following “explanation” will print in the CIW windows:

```
(GE-1013): The highlighted marker belongs to cellview LAB7/badinv/layout and its reason is: (SCMOS_SUBM Rule 2.3)
source/drain active to well edge: 1.80 um
(GE-1013): The highlighted marker belongs to cellview LAB7/badinv/layout and its reason is: (SCMOS_SUBM Rule 2.3)
source/drain active to well edge: 1.80 um
```

We violated MOSIS Sub-micron SCMOS technology (SCMOS_SUBM) DRC Rule Number 2.3, which states:

- nactive layer should be at least 1.8 μ m (6 λ) far from the closest nwell.
- By bringing the nmos too close above, the nactive region of the nmos got too close to the nwell of the pmos.

 Looking at the other 4 errors, we single-click on the bottom polygon; it will turn purple and will give this explanation in CIW:



This violates DRC Rule Number 7.2, which states that metal1 spacing must be at least $0.9\mu\text{m}$ (3λ).

It can be checked in the divaDRC.rul file from the terminal by:


cat divaDRC.rul | grep "Rule7.2"

```
-bash-4.2$ cat divaDRC.rul | grep "Rule 7.2"
    sprintf( errMsg "(SCMOS Rule 7.2) metal1 spacing: %.2f um" (lambda*3.0))
    sprintf( errMsg "(SCMOS Rule 7.2) metal1 spacing: %.2f um" (lambda*2.0))
```

The other three errors are all bunched up in the area where we have the A input.

```
(GE-1013): The highlighted marker belongs to cellview LAB7/badinv/layout and its reason is: (SCMOS Rule 7.3) metal1
enclosure of contact: 0.30 um
(GE-1013): The highlighted marker belongs to cellview LAB7/badinv/layout and its reason is: cp contact does not
connect to two layers
(GE-1013): The highlighted marker belongs to cellview LAB7/badinv/layout and its reason is: (SCMOS_SUBM Rule 2.3)
source/drain active to well edge: 1.80 um
```

 It is telling to put a **metal1** around the **cp** (poly contact) that at least surrounds the **cp** by 1λ on every side, so we do that and rerun the DRC.



Doing that, we end up with 4 errors instead of 5.

```

***** Summary of rule violations for cell "badinv layout" *****
# errors  Violated Rules
      2  (SCMOS Rule 7.2) metal1 spacing: 0.90 um
      2  (SCMOS_SUBM Rule 2.3) source/drain active to well edge: 1.80 um
      4  Total errors found



```

Now, we hit s (stretch) and stretch the nmos below by $\lambda/2$ and run DRC again. We get 1 error.

```

***** Summary of rule violations for cell "badinv layout" *****
# errors  Violated Rules
      1  (SCMOS Rule 7.3) metal1 enclosure of contact: 0.30 um
      1  Total errors found

```

  

2) Extracting the inverter layout

We add the line **export CDS_Netlisting_Mode=Analog** to the ~/.bash_profile

```


export CDK_DIR="$HOME/cadence/Techlibs/ncsu-cdk-1.6.0.beta"
cd cadence
module load cadence
export CDS_Netlisting_Mode=Analog

```


We draw pins for vdd!, gnd!, A, Y, setting A to input, Y to output. vdd! and gnd! both to input/output.

Our goal is to determine whether the schematic of the inverter represents the same circuit as the layout of the same inverter cell, we just drew.

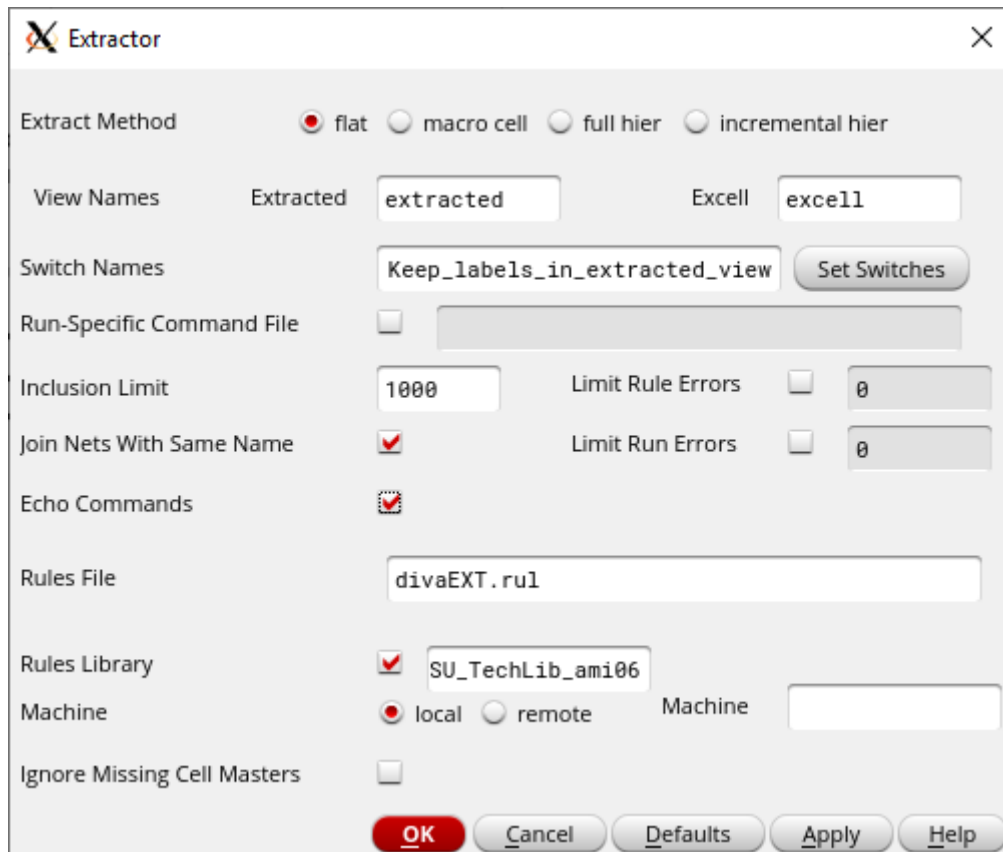- The first step in doing so is to extract the layout. Go to Verify -> Extract
- Click Set Switches and choose Extract_parasitic_caps Keep_labels_in_extracted_view
- Set Rules file to divaEXT.rul



 With these options, the extracted layout will be saved in the extracted view.




The values of the parasitic capacitors are:

- pcapacitor (instance "+2", library "NCSU_Analog_...") – **506.52aF**
- pcapacitor (instance "+3", library "NCSU_Analog_...") – **447.36aF**
- pcapacitor (instance "+4", library "NCSU_Analog_...") – **150.66aF**
- pcapacitor (instance "+5", library "NCSU_Analog_...") – **267.84aF**

According to the extractor, this layout represents 6 parts, all from the same NCSU_Analog_Parts library.

- pmos4: which is our pmos transistor on top
- nmos4: which is our nmos transistor on the bottom
- pcapacitor: which is a cell that exists in the NCSU_Analog_Parts library, with the sole intention to be able to model the parasitic capacitors in a circuit (layout).

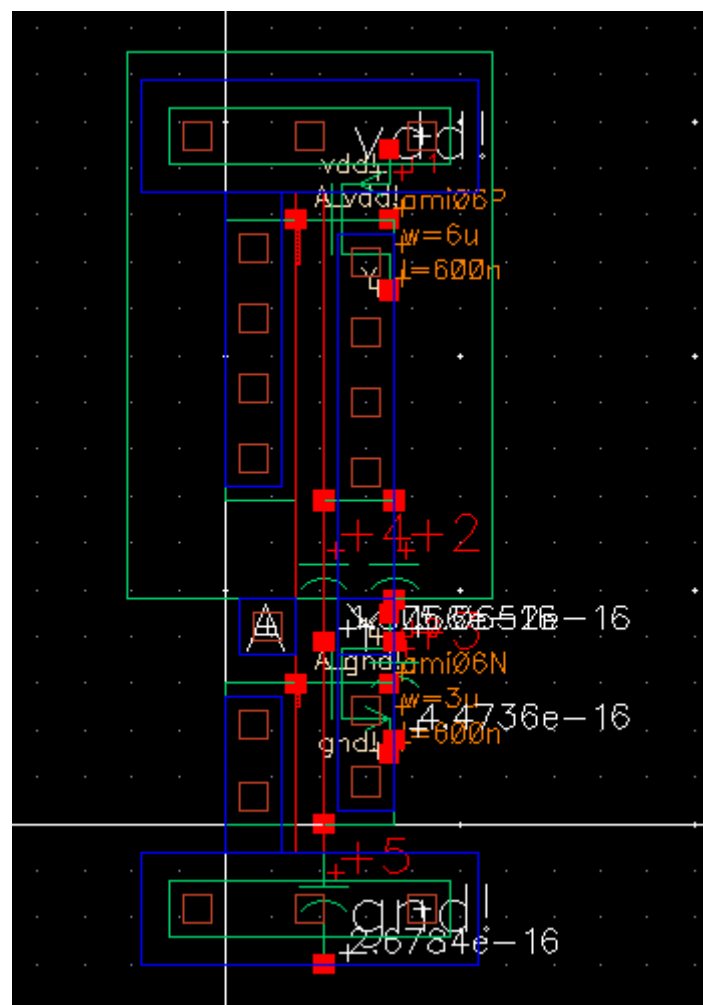Hitting SHIFT+F we switch to this detailed view:



3) LVS: Layout vs. Schematic


The tool that facilitates this comparison is called LVS (Layout vs. Schematic).



When Run, it returns the following success message:

```
LVS job is now started...  
The LVS job has completed. The net-lists match.
```
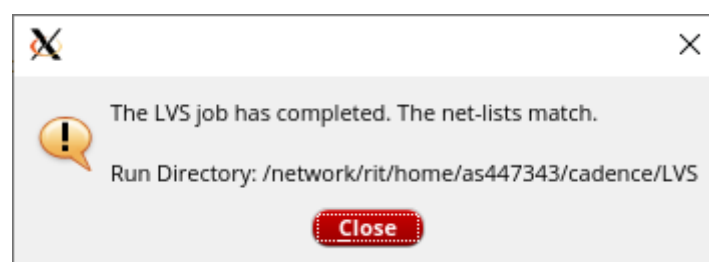
```
Run Directory: /network/rit/home/as447343/cadence/LVS
```



We go to the ~/cadence/LVS directory and look at the si.out file.

➤ `cd ~/cadence/LVScat si.out | less`

```
ceashpc-12.nt.albany.edu - PUTTY
8($#)SCDS: LVS version 6.1.8-64b 10/01/2018 19:50 (ip-172-18-22-57) $

Command line: /network/rit/lab/ceashpc/software/cadence/IC618/tools.lnx64/dfII/bin/64bit/LVS -dir /network/rit/home/as447343/cadence/LVS -l -s -t /network/rit/home/as447343/cadence/LVS/layout /network/rit/home/as447343/cadence/LVS/schematic
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /network/rit/home/as447343/cadence/LVS/layout/netlist
count
4      nets
4      terminals
1      pmos
1      nmos

Net-list summary for /network/rit/home/as447343/cadence/LVS/schematic/netlist
count
4      nets
4      terminals
1      pmos
1      nmos

Terminal correspondence points
N2      N2      A
N1      N5      Y
N0      N1      gnd!
N3      N0      vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.

          layout  schematic
          instances
un-matched      0      0
rewired          0      0
size errors      0      0
```

This is the report from LVS.

Now, we look at the extracted netlist.

➤ `cd ~/cadence/LVS/layout`
➤ `cat extNetlist | more`

```
-bash-4.2$ cat extNetlist | less
-bash-4.2$ cat extNetlist | more
t 2 A input
t 1 Y output
t 0 gnd! inputOutput
t 3 vdd! inputOutput

n 0 /gnd!
n 1 /Y
n 2 /A
n 3 /vdd!

; pmos4 Instance /+1 = auLvs device Q0
d pmos D G S B (p D S)
i 0 pmos 1 2 3 3 " m 1 1 600e-9 w 6e-6 "

; pcapacitor Instance /+5 = auLvs device C1
d pcapacitor PLUS MINUS (p PLUS MINUS)
i 1 pcapacitor 2 0 " c 267.84e-18 "

; pcapacitor Instance /+4 = auLvs device C2
i 2 pcapacitor 3 2 " c 150.66e-18 "

; pcapacitor Instance /+3 = auLvs device C3
i 3 pcapacitor 1 0 " c 447.36e-18 "

; pcapacitor Instance /+2 = auLvs device C4
i 4 pcapacitor 3 1 " c 506.52e-18 "

; nmos4 Instance /+0 = auLvs device Q5
d nmos D G S B (p D S)
i 5 nmos 1 2 0 0 " m 1 1 600e-9 w 3e-6 "

-bash-4.2$
```

Similarly, we look at the netlist of the schematic using these commands:

- cd ~/cadence/LVS/schematic
- cat extNetlist | less

```
t 2 A input
t 5 Y output

n 1 gnd!
n 0 vdd!
n 2 /A
n 5 /Y


; pmos4 Instance /P0 = auLvs device Q0
d pmos D G S B (p D S)
i 0 pmos 5 2 0 0 " m 1 "

; nmos4 Instance /N0 = auLvs device Q1
d nmos D G S B (p D S)
i 1 nmos 5 2 1 1 " m 1 "
t 0 vdd! global
t 1 gnd! global

(END)
```

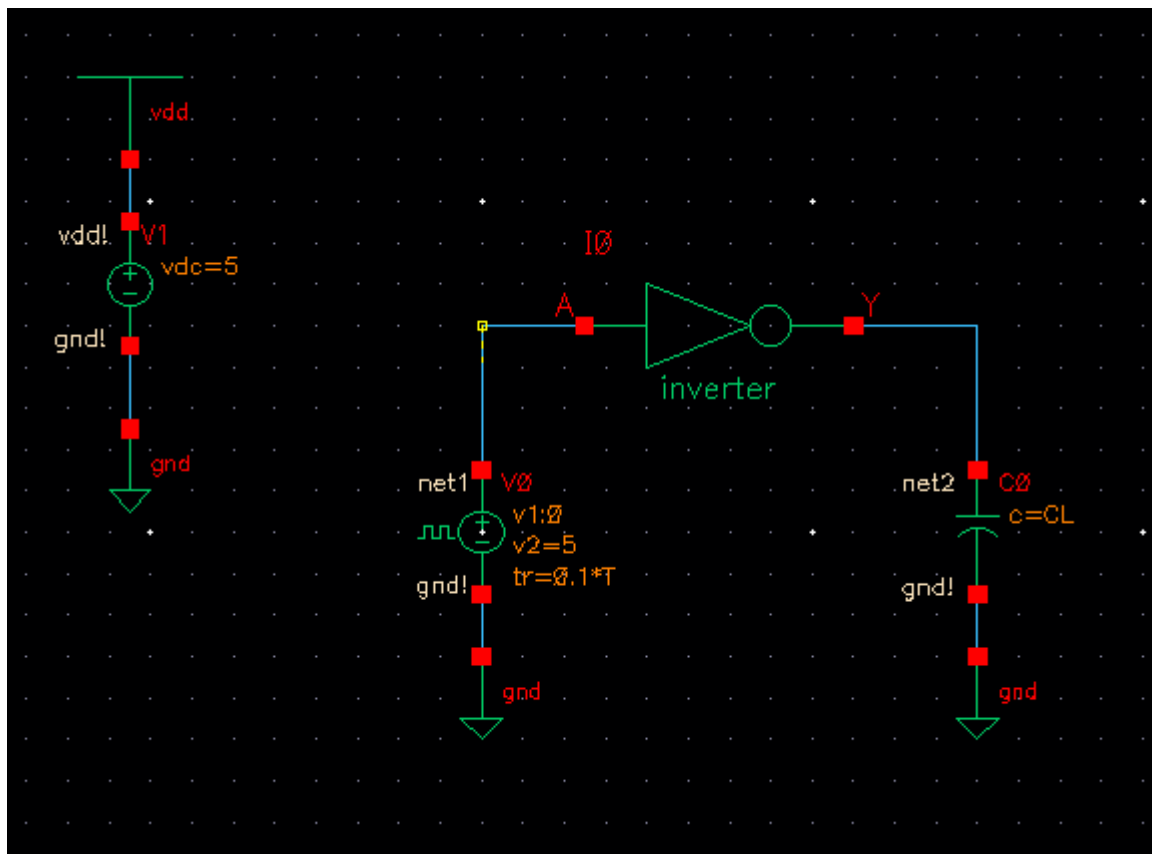4) Analyzing the inverter using ADE L

The TBinverter is the schematic view (called cmos_sch) of the test bench that includes other schematics and symbols.




- Parameterize cap to CL.
- Set vdc to 5V DC.
- Set vpulse Period=T.
- Delay = 1ps, Rise time = $0.1 \cdot T$, Fall time = $0.1 \cdot T$, Pulse width = $0.4 \cdot T$.
- Voltage 1 = 0V, Voltage 2 = 5V.

Rise and fall times are 10% of the total period; 80% is the upper and lower part of the wave, each 40% of the period.


Double-clicking the layout view of the inverter cell, we open it and go to Verify -> LVS again. Entering the parameters: Left side will still be the schematic view, but we will set the right side to analog_extracted. This time, we will click Build Analog.



We select Include All for parasitics

 


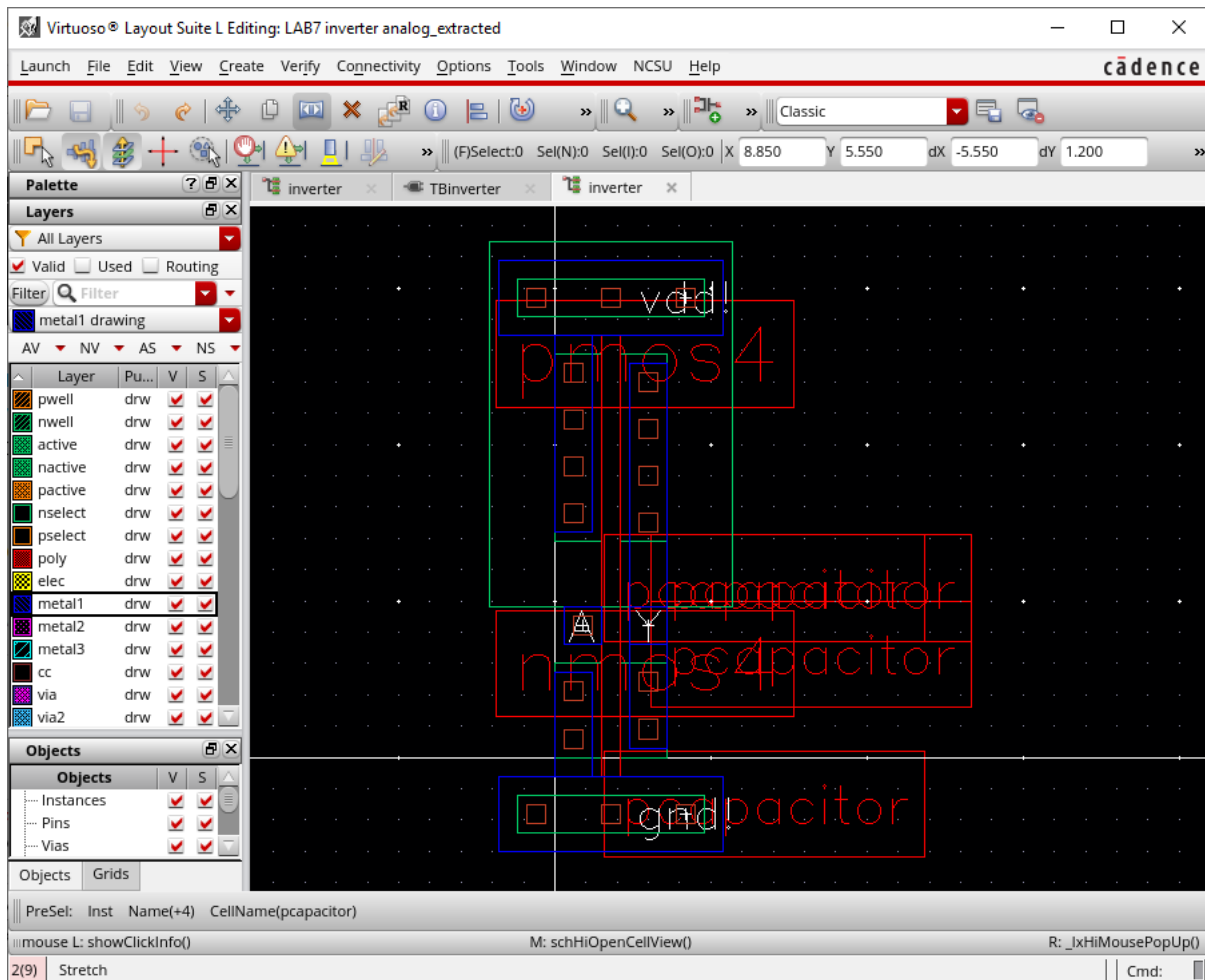Analog_extracted view is very similar to the extracted view.




The inverter now has 5 different views: analog_extracted, extracted, layout, schematic, and symbol. Close out of the layout view and analog_extracted view.

 In Library Manager, TBinverter cell is selected and we create new config view by File -> New -> Cell View. Choose config for View. It will open the config view of TBinverter with the Hierarchy Editor.



When in Hierarchy Editor, we click Use Template. In the Use Template window, Name = spectre is chosen.

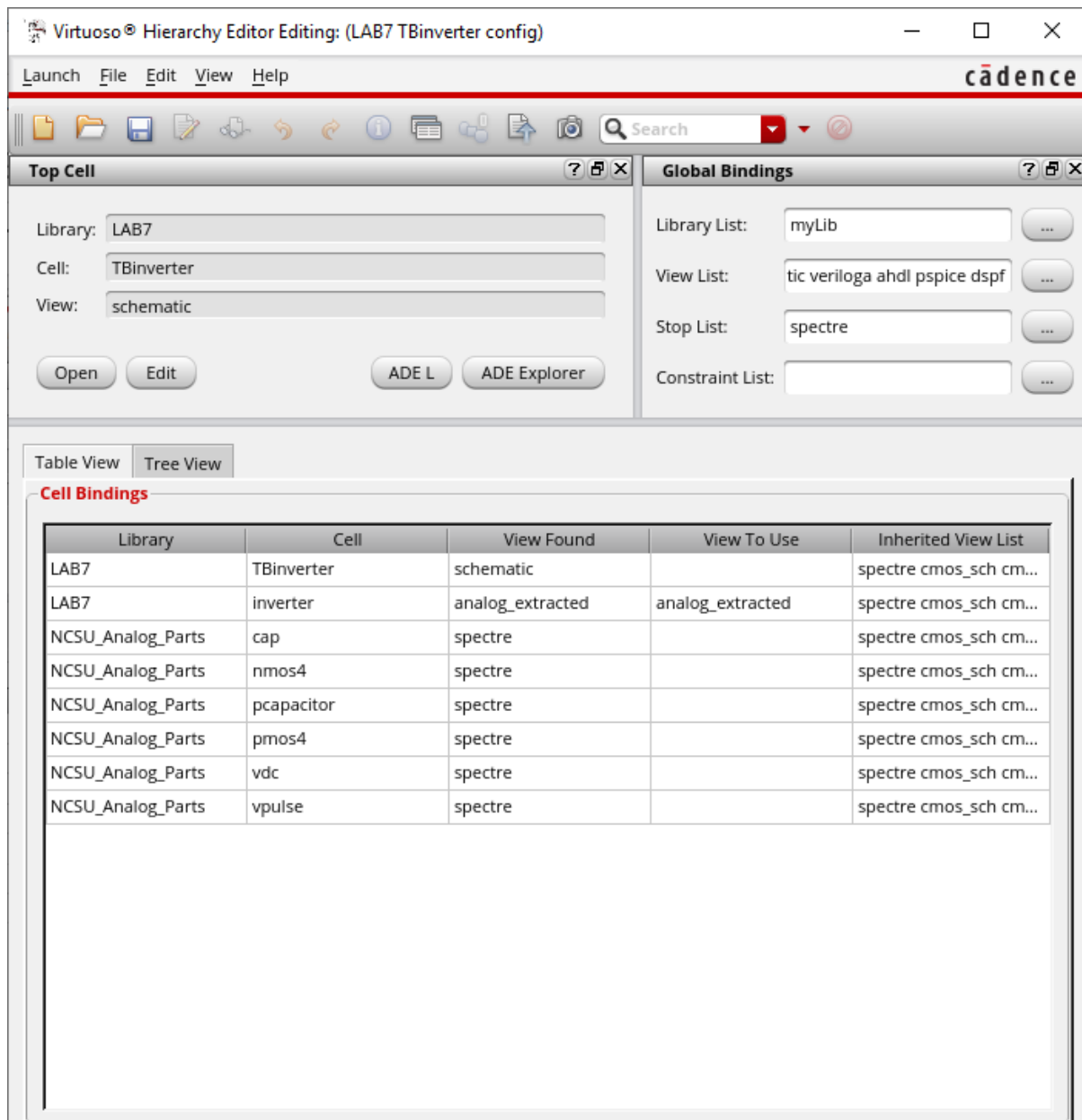In the New Configuration window, View is changed to schematic.




TBinverter is the root of the tree, which has a schematic view

- It has an instantiation of our inverter cell, which has a schematic view
- It has instantiations of cap, nmos4, pmos4, vdc, and vpulse cells with a spectre views.

View -> Tree is selected.

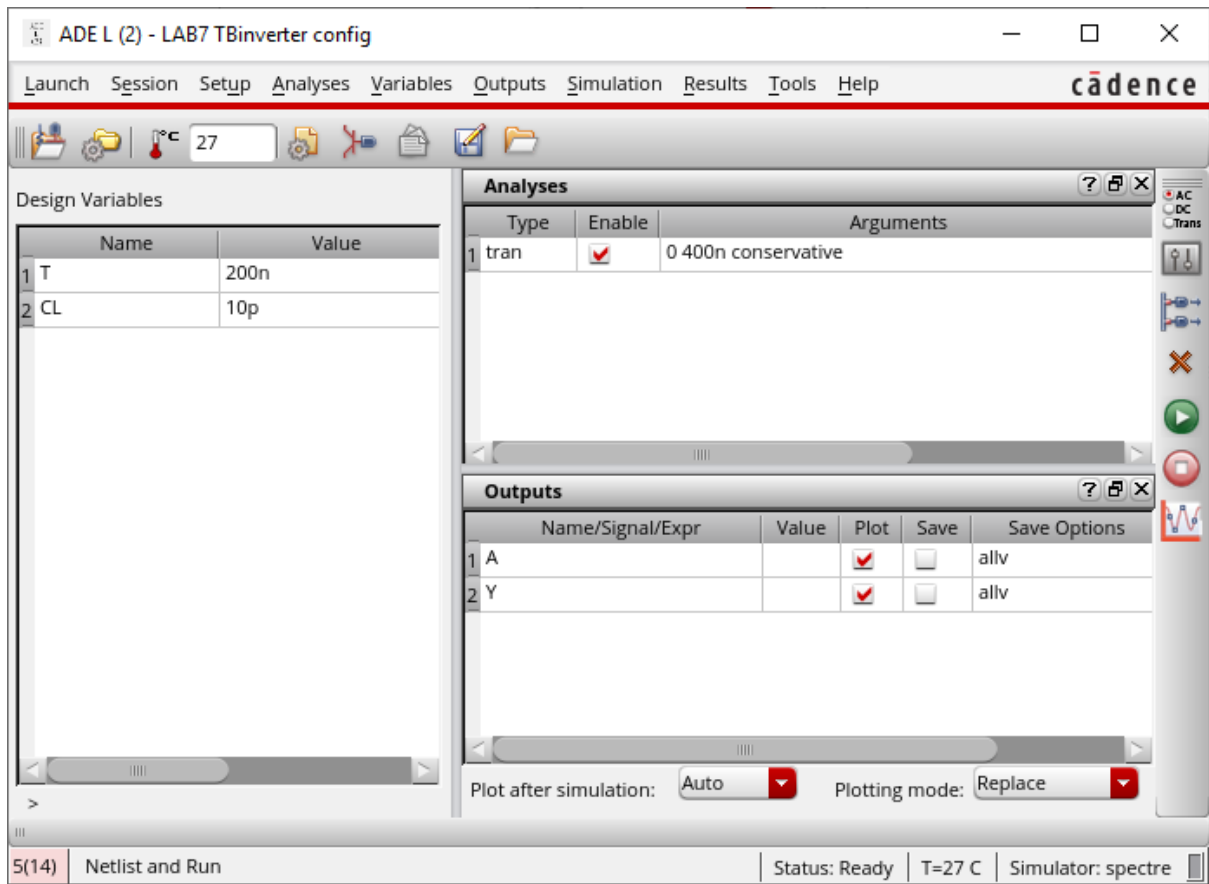In the Tree View, right clicking the inverter cell in the tree Instance View = analog_extracted is set.



The parasitic capacitances are very small and we notice no visible effect on the waveforms.

