


## ECE420/520: Lab3 Report – Symbol Editor

Name: Arijit Sengupta, ID: 001441742

In this lab, the goal is to achieve multiple milestones:


- 1) Learn how to work with the Symbol Editor.
- 2) Create symbols for an inverter and a nor gate.
- 3) Simulate a simple digital circuit with multiple gates in it and simulate it.

### Inverter Schematic:

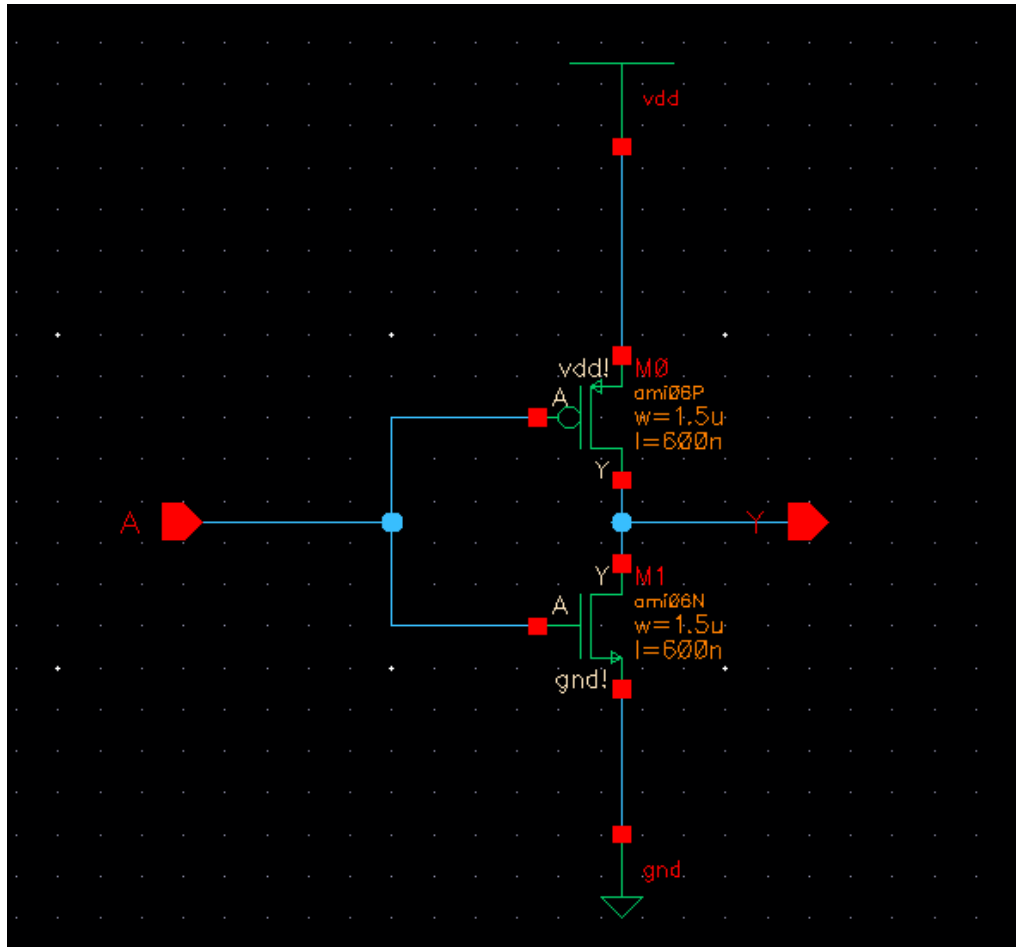

Now to create a symbol for the inverter, Create -> Cellview -> From Cellview. In the box named *To View Name*, **symbol** is chosen.


The final **inverter symbol**:

 

where red stuff is the electrical stuff and green stuff is the cosmetic stuff.

Now replacing the symbol in the **TBinverter** created in lab 2, the transient analysis is performed.

**Circuit diagram:**

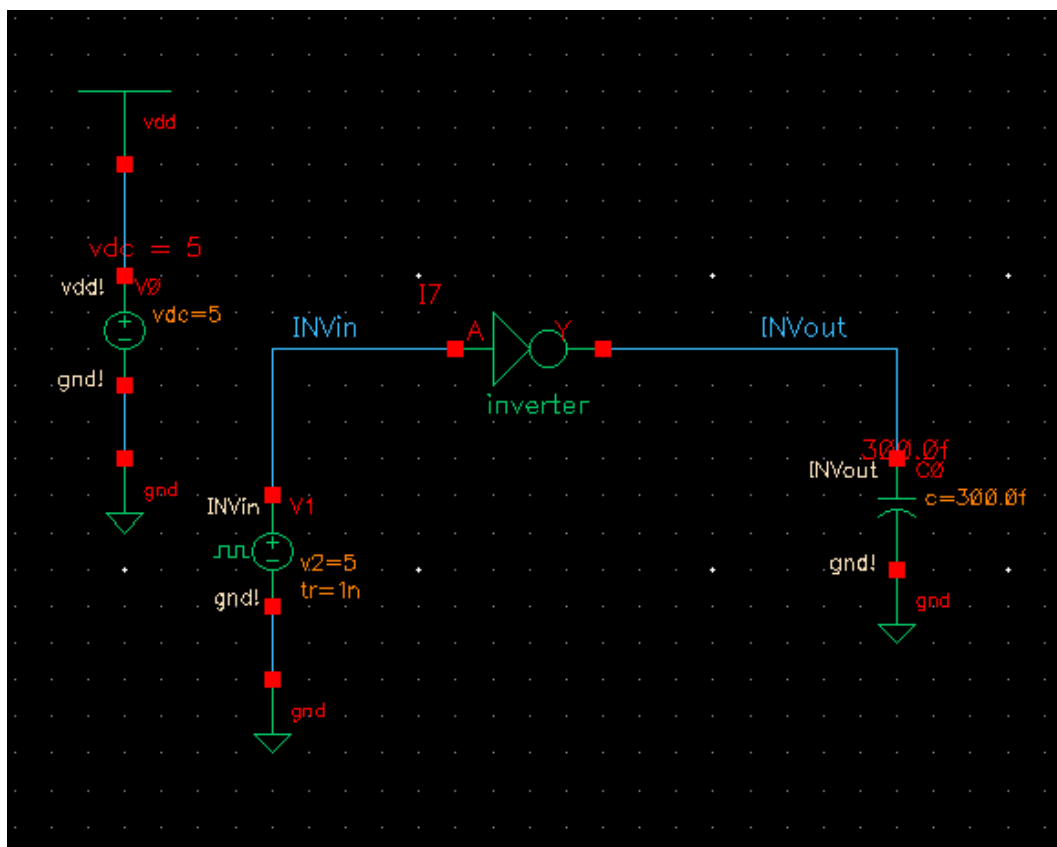

The **output results** are similar to the ones obtained in the previous lab and establishes that the inverter works correctly:

Output and IC/nodeset summary:

save 2 (current)  
save 6 (voltage)


tran: time = 26.17 ns	(2.62 %)	step = 6.545 ns	(655 m%)
tran: time = 78.63 ns	(7.86 %)	step = 4.472 ns	(447 m%)
tran: time = 127.7 ns	(12.8 %)	step = 7.299 ns	(730 m%)
tran: time = 178.7 ns	(17.9 %)	step = 4.514 ns	(451 m%)
tran: time = 227.8 ns	(22.8 %)	step = 7.337 ns	(734 m%)
tran: time = 278.7 ns	(27.9 %)	step = 4.508 ns	(451 m%)
tran: time = 327.8 ns	(32.8 %)	step = 7.344 ns	(734 m%)
tran: time = 378.7 ns	(37.9 %)	step = 4.507 ns	(451 m%)
tran: time = 427.8 ns	(42.8 %)	step = 7.354 ns	(735 m%)
tran: time = 478.7 ns	(47.9 %)	step = 4.506 ns	(451 m%)
tran: time = 527.8 ns	(52.8 %)	step = 7.364 ns	(736 m%)
tran: time = 578.7 ns	(57.9 %)	step = 4.505 ns	(450 m%)
tran: time = 627.9 ns	(62.8 %)	step = 7.375 ns	(737 m%)
tran: time = 678.7 ns	(67.9 %)	step = 4.503 ns	(450 m%)
tran: time = 727.9 ns	(72.8 %)	step = 7.381 ns	(738 m%)
tran: time = 778.7 ns	(77.9 %)	step = 4.503 ns	(450 m%)
tran: time = 827.9 ns	(82.8 %)	step = 7.387 ns	(739 m%)
tran: time = 878.7 ns	(87.9 %)	step = 4.502 ns	(450 m%)
tran: time = 927.9 ns	(92.8 %)	step = 7.393 ns	(739 m%)
tran: time = 978.7 ns	(97.9 %)	step = 4.502 ns	(450 m%)

Number of accepted tran steps = 946


Maximum value achieved for any signal of each quantity:

V: V(INVout) = 5.004 V


I: I(V0:p) = 305.2 uA

 


## NOR Gate Schematic:

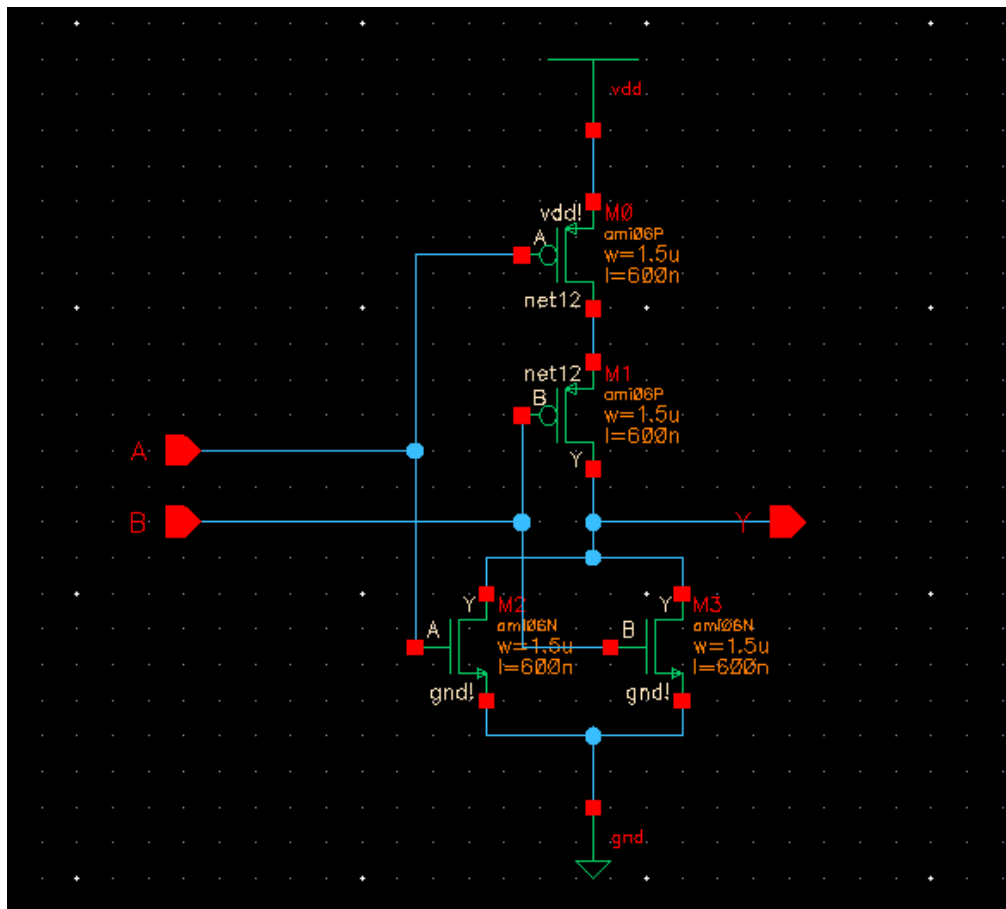

The final **nor** gate symbol:

 

The output results:

 


The output shows only when both the inputs are LOW (0), the output is HIGH (1). Hence, the NOR gate is verified.

**Implementing a simple Boolean Function:  $Y = AB'$**


Simplification:  $Y = AB' = (A' + B)' = \text{NOR}(\text{NOT}(A), B)$

Hence, the Boolean function Y can be achieved using a NOR gate and an inverter.

**The circuit schematic:**

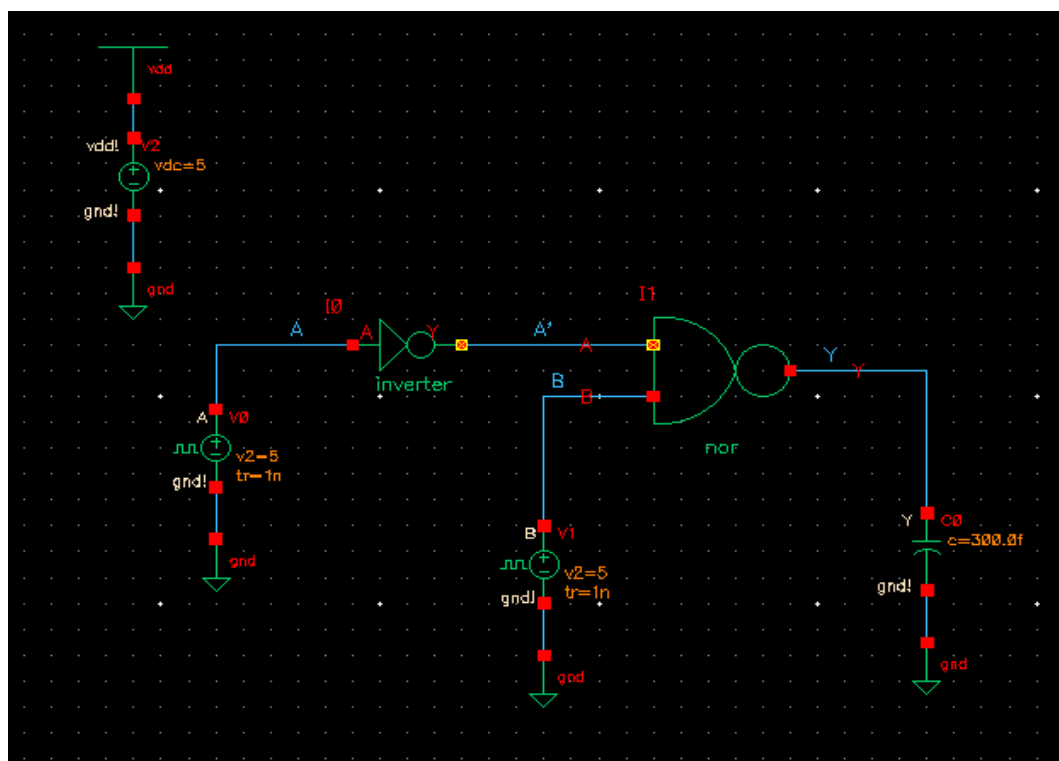

The output results:

 

The output shows only when the inputs A is HIGH (1) and B is LOW (0), the output is HIGH (1). Hence, the expression is verified from the truth table below.

**Truth Table:**

A	B	A'	Y
0	0	1	0
0	1	1	0
1	0	0	1
1	1	0	0