

ECE520 Introduction to VLSI, Project 2

Name: Arijit Sengupta, ID: 001441748

PART A

Truth Table of Full Adder:

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Therefore, the **Boolean expressions** for S and Cout are given by –

$$S = A'B'Cin + A'BCin' + AB'Cin' + ABCin = Cin(AB + A'B') + Cin'(AB' + A'B) = Cin(A'B + A'B')' + Cin'(AB' + A'B)$$

$$S = \text{XOR}(\text{Cin}, \text{XOR}(A, B))$$



$$\text{Cout} = A'BCin + AB'Cin + ABCin' + ABCin = Cin(A'B + AB') + AB(Cin + Cin') = Cin(A'B + AB') + AB$$

$$\text{Cout} = \text{NOT}(\text{NOR}(\text{NOT}(\text{NAND}(A, B)), \text{NOT}(\text{NAND}(\text{Cin}, \text{XOR}(A, B)))))$$



The above expressions represent the functions using the NOR, NAND, Inverter (NOT), XOR and XNOR gates only, as per the requirement.

Schematic and Symbols:



1. Inverter (NOT Gate) –

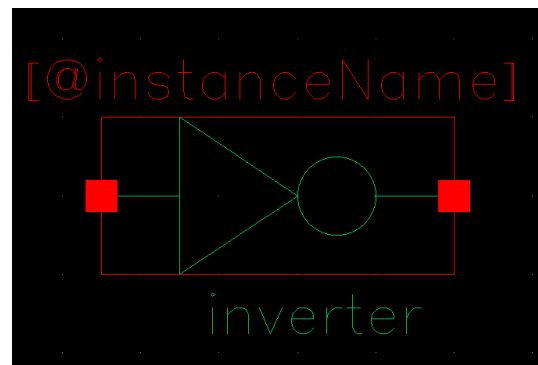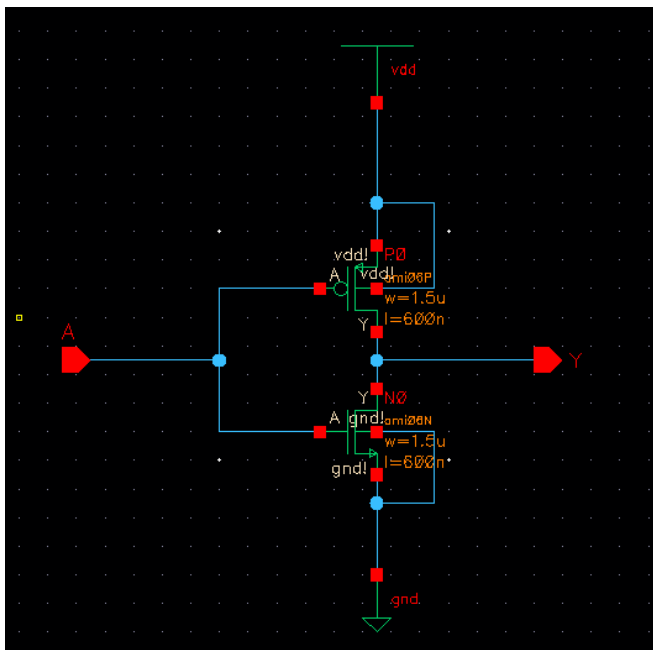



2. NOR Gate –

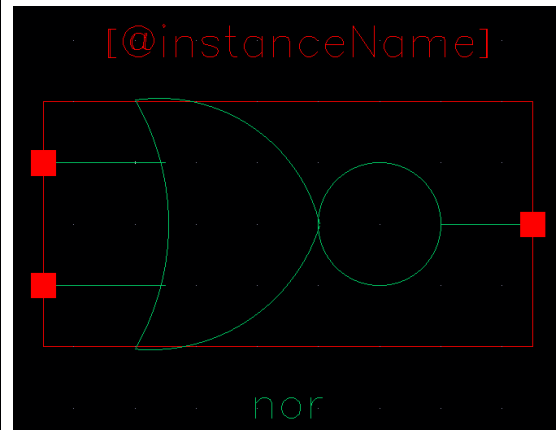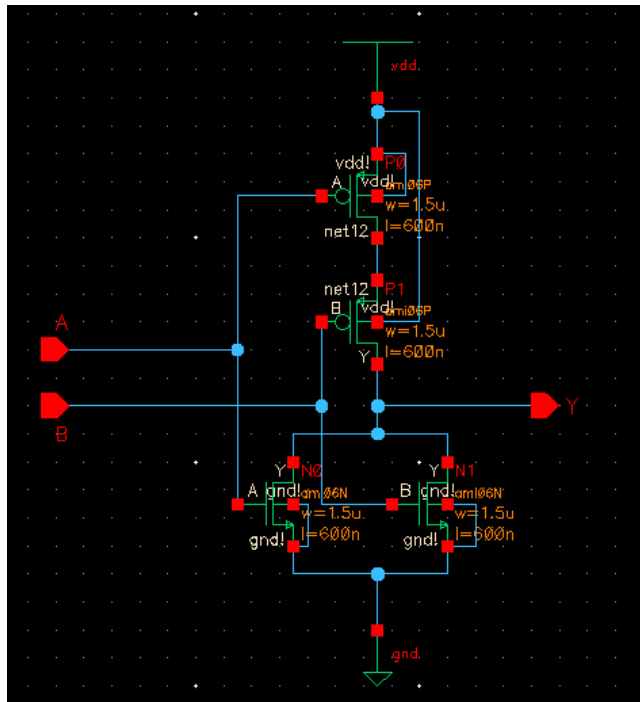



3. NAND Gate –

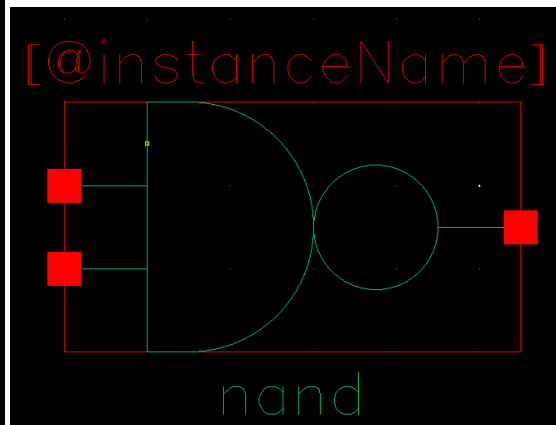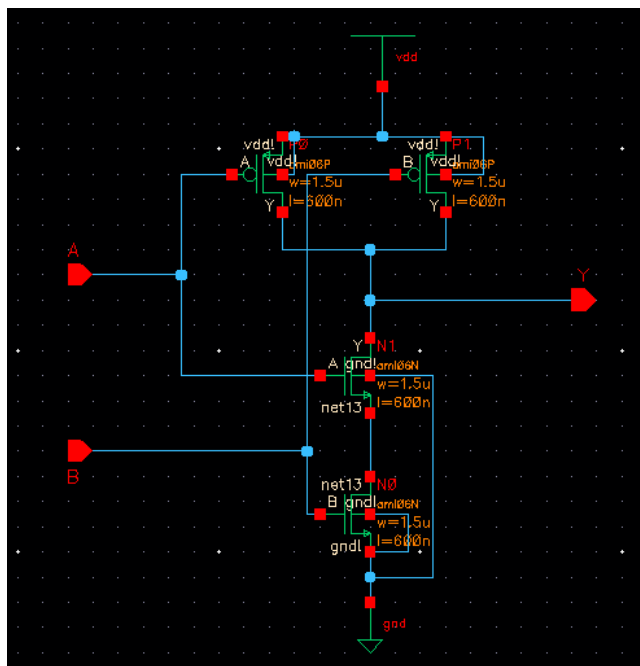



4. XOR Gate –

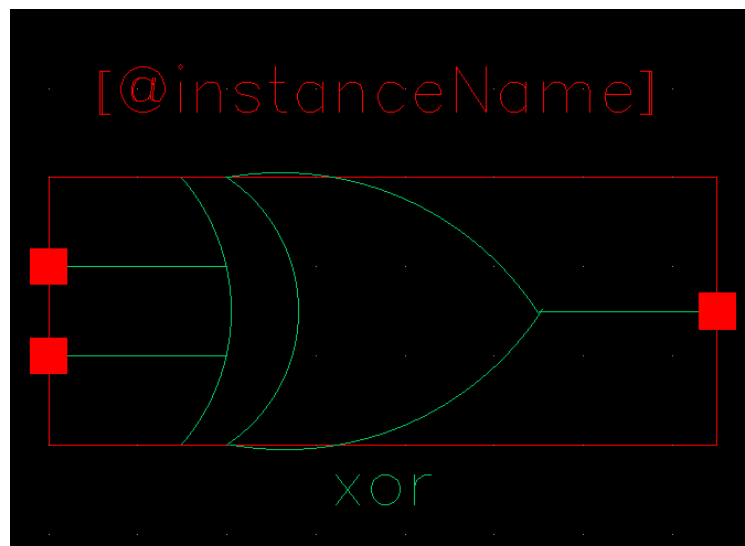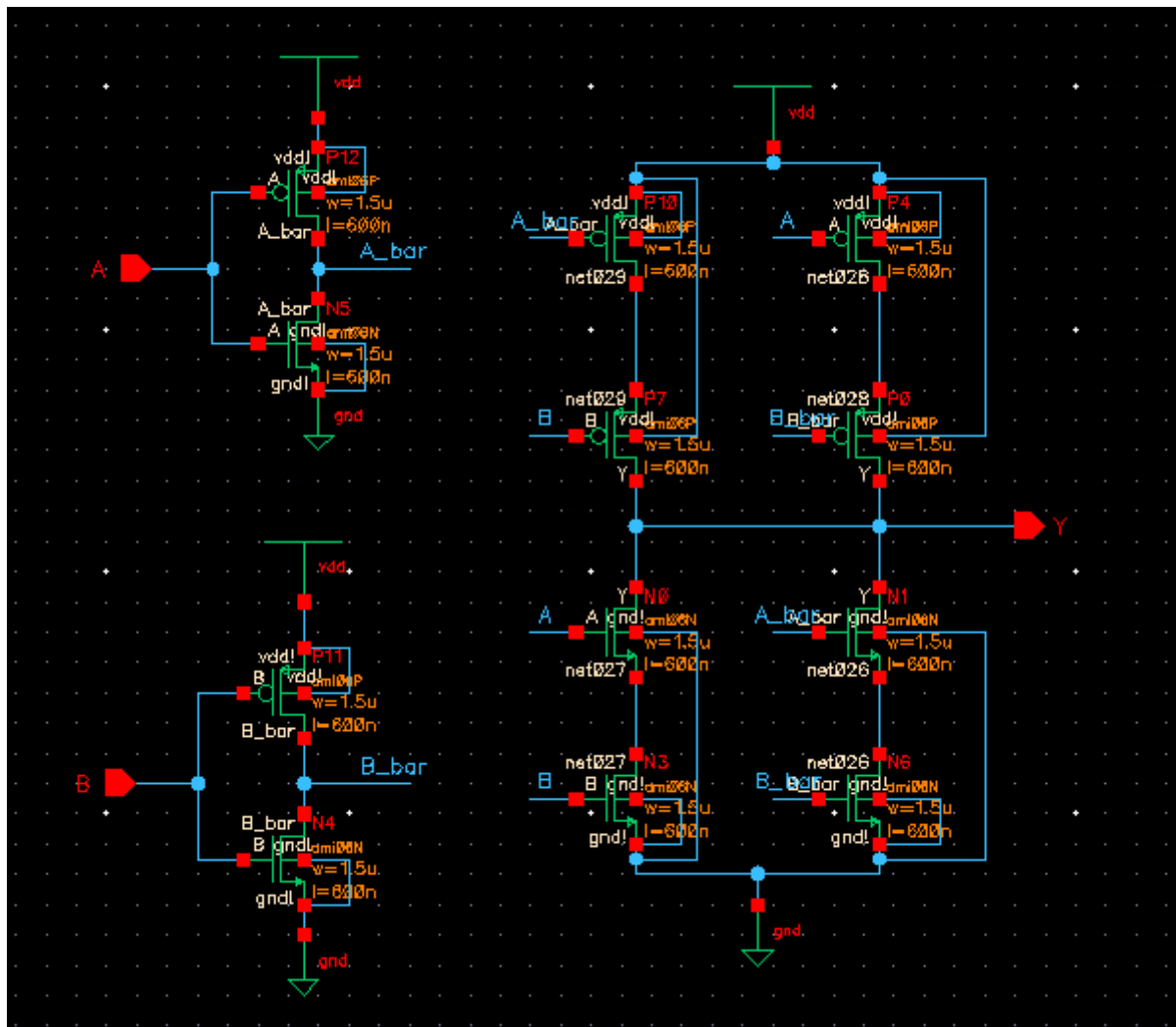

5. XNOR Gate –

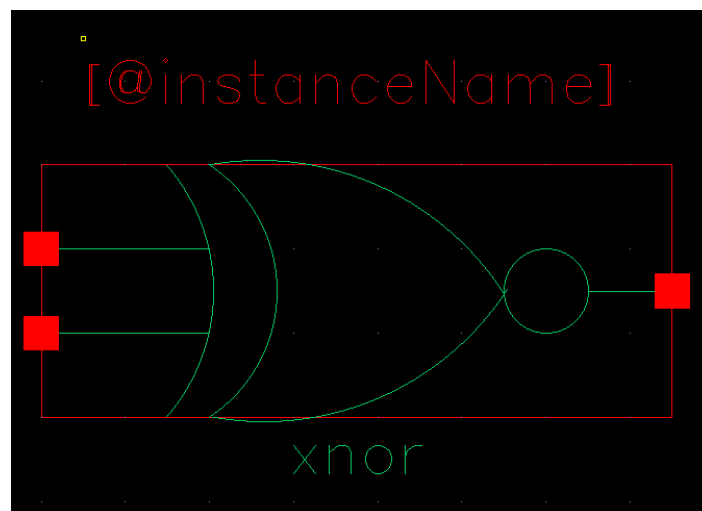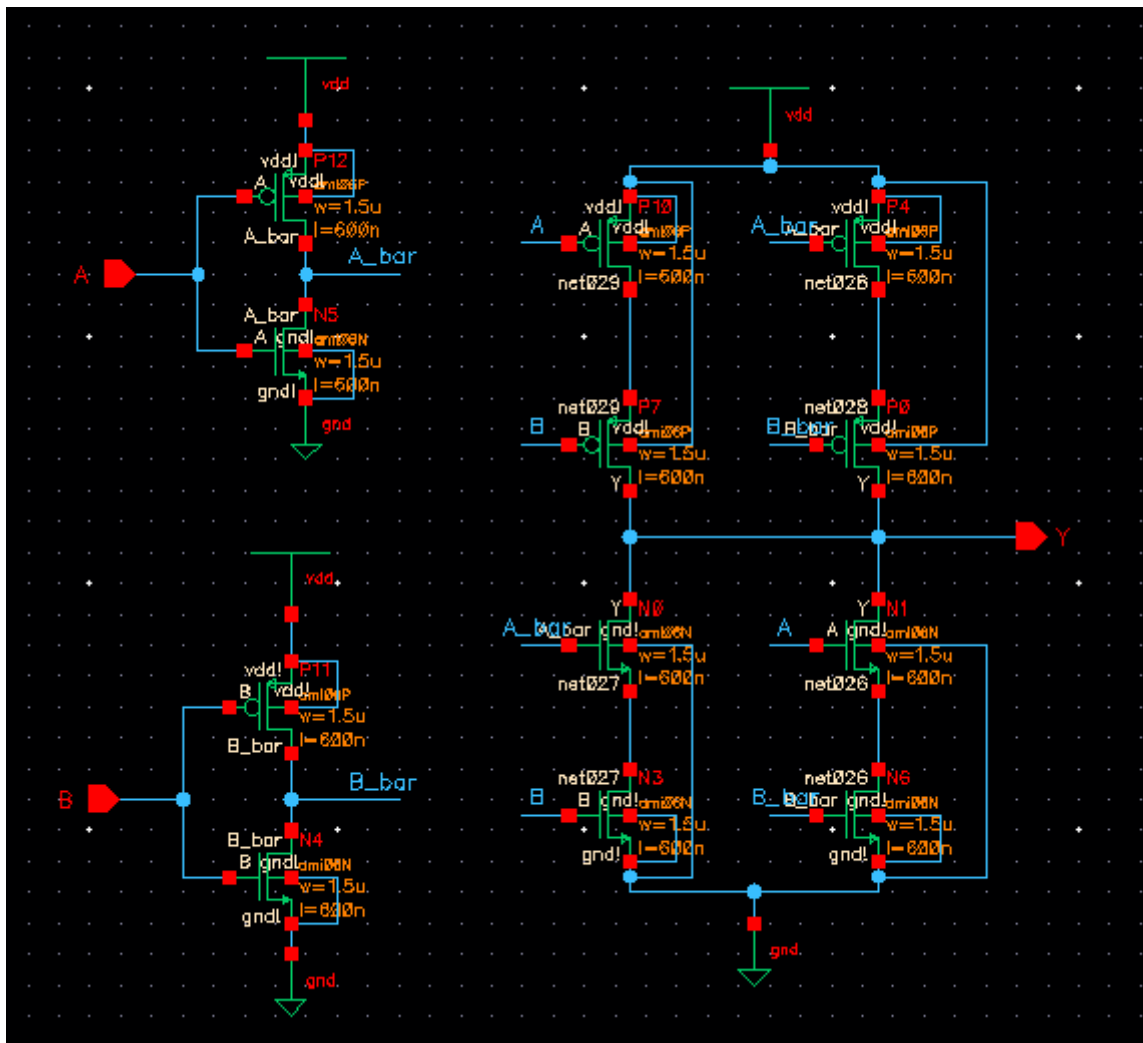

Full Adder Schematic and Symbol:

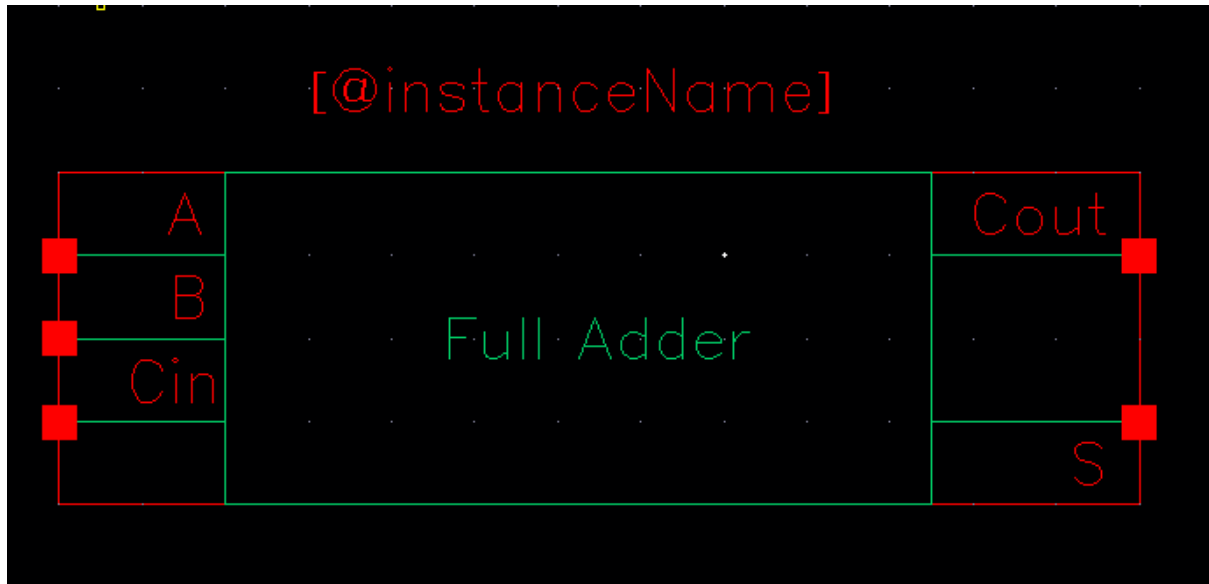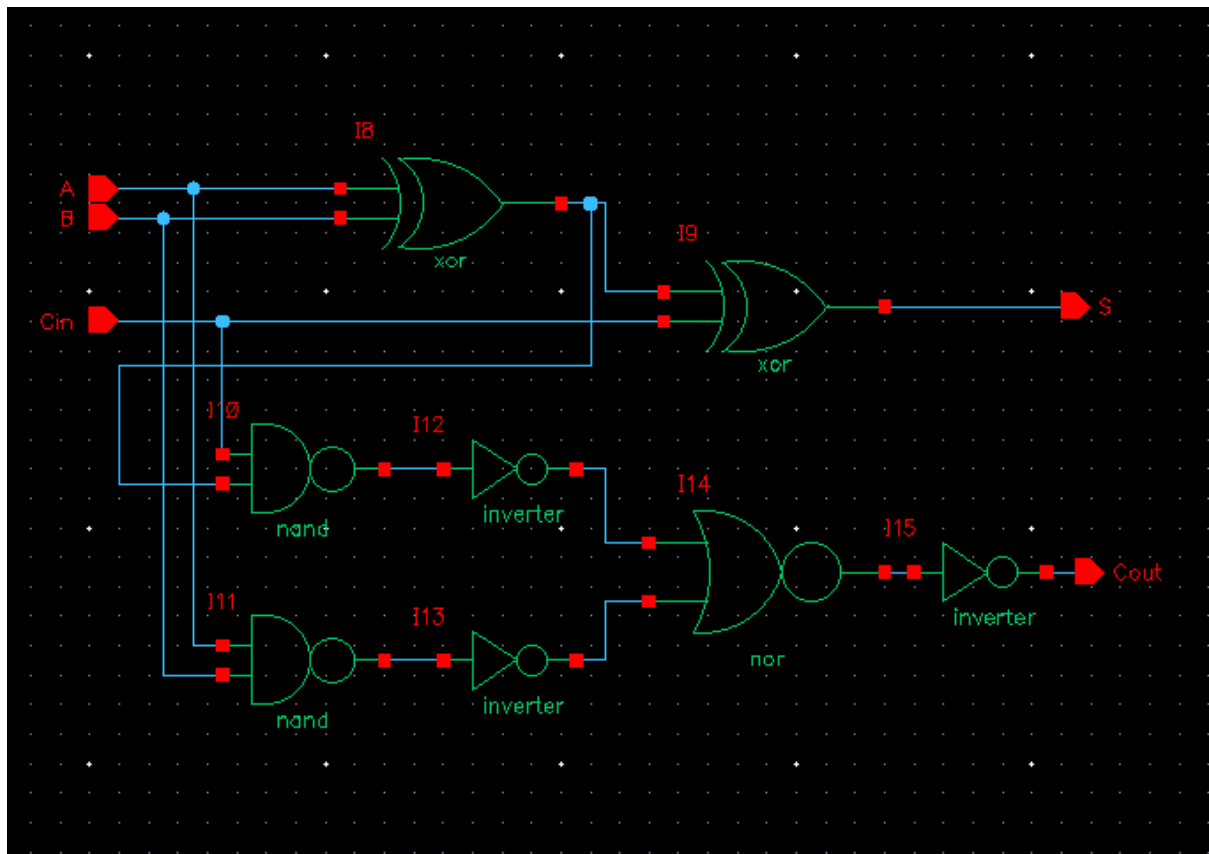


The FullAdder is run in a test bench named **TBFullAdder**.

Parameters for analysis:

Times for vpulse – **input A**: Delay=1ns, Rise time = r, Fall time = f, Pulse width = $(T-r-f)/2$, Period = T;
input B: Delay=1ns, Rise time = r, Fall time = f, Pulse width = $(2*T-r-f)/2$, Period = $2*T$.

CL=1E-12 (1 pF), **T**=100E-9 (100 ns), **r**=5E-9 (5ns), **t**=5E-9 (5ns).

TBFullAdder Schematic:

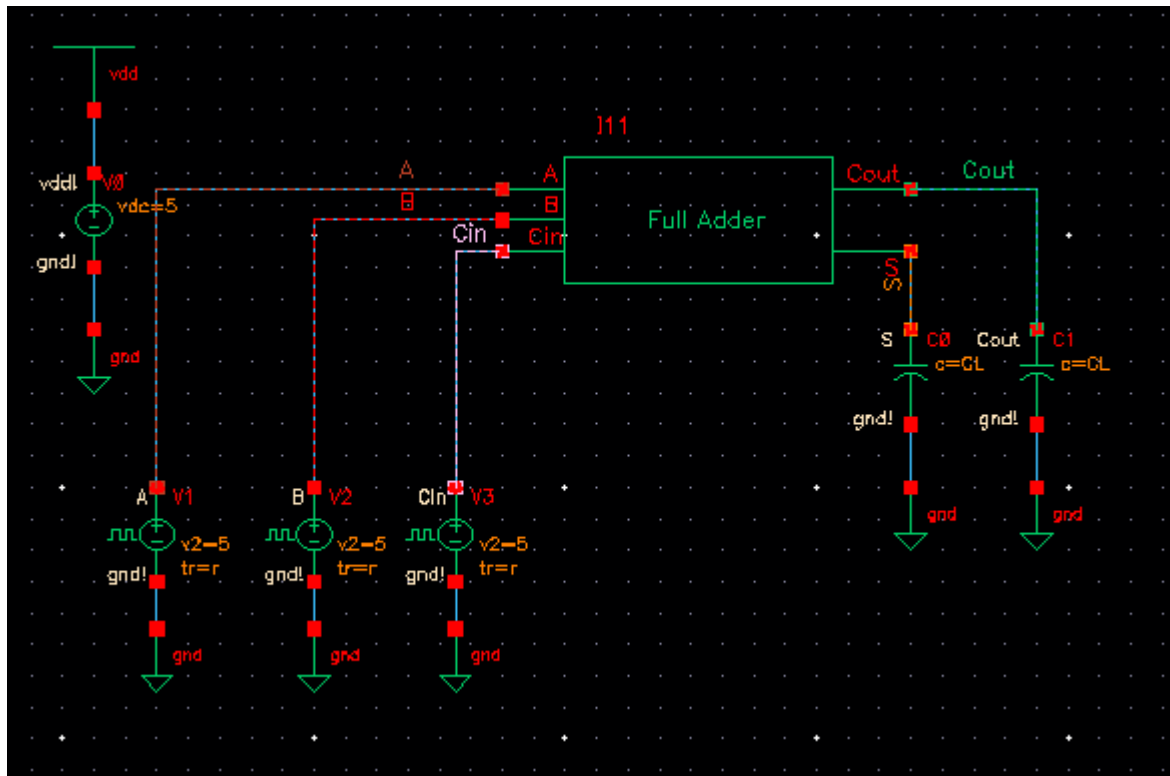

The circuit is run using the following values:

ADE L (2) - PROJ2 TBFullAdder schematic

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Help

Design Variables

Name	Value
1 CL	1p
2 f	5n
3 r	5n
4 T	100n

Analyses

Type	Enable	Arguments
1 tran	<input checked="" type="checkbox"/>	0.800n conservative

Outputs


Name/Signal/Expr	Value	Plot	Save	Save Options
1 A		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
2 B		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
3 Cin		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
4 S		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv
5 Cout		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	allv

Plot after simulation: Auto Plotting mode: Replace

> Results in ...as447343/cadence/simulation/TBFullAdder

4(29) Delete Status: Ready T=27 C Simulator: spectre

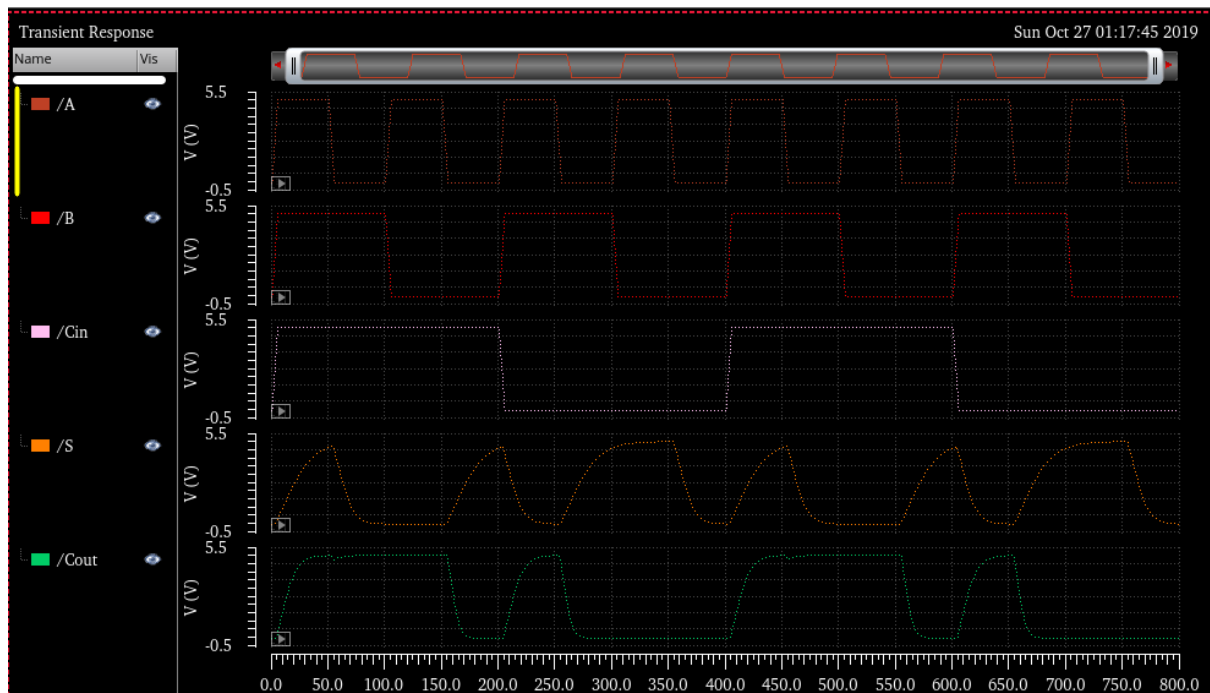
Waveform of A, B, Cin inputs and S, Cout outputs:




PART B

We modify the inputs A & B in order to get all the required transition delays for this part.

Waveform 1 - Time periods: $A = T$ s, $B = 2T$ s, $C_{in} = 4T$ s

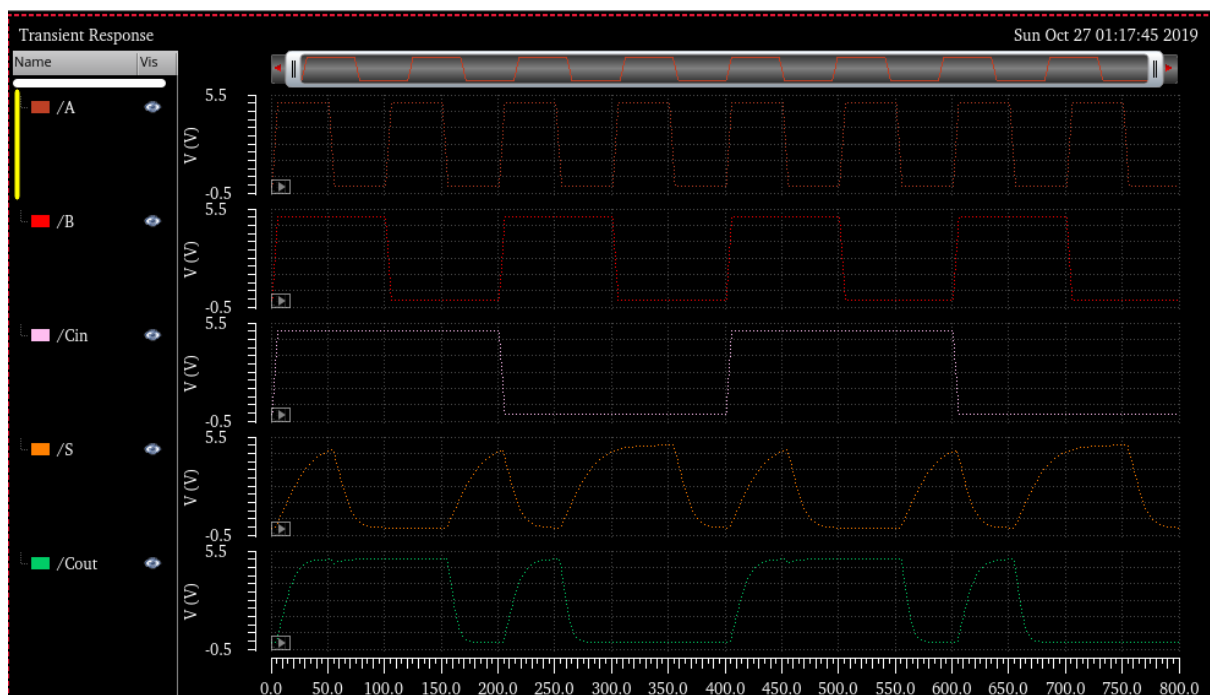

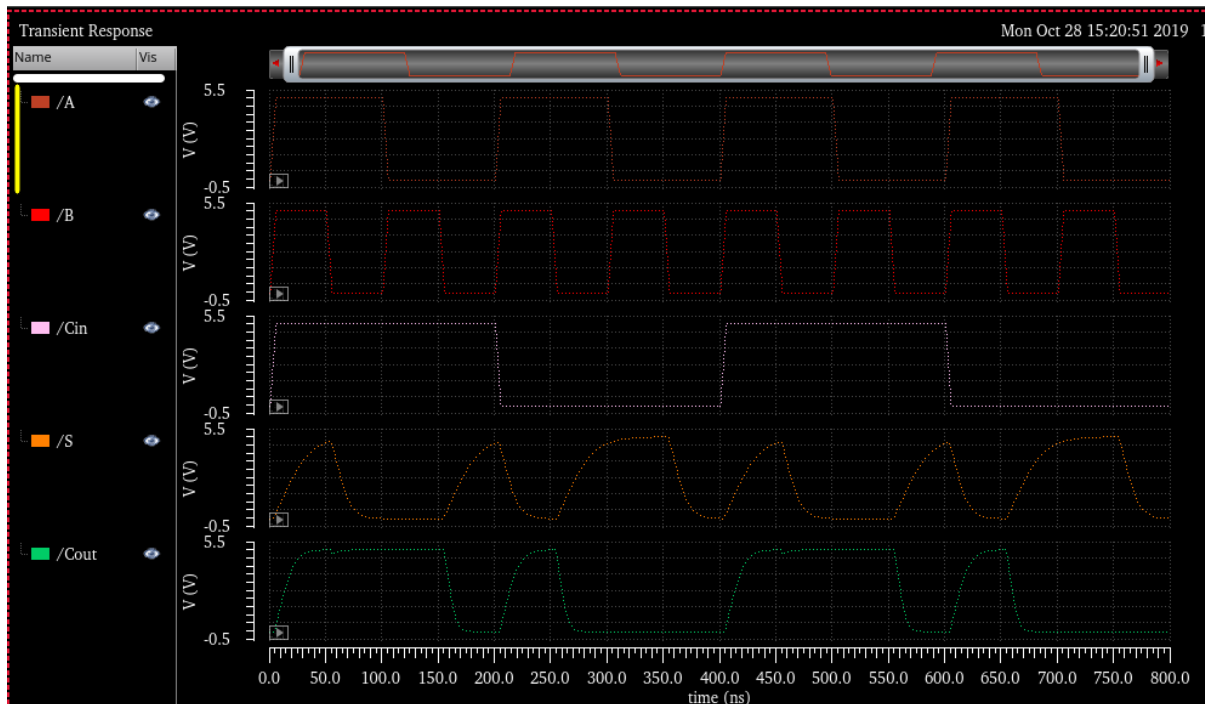Waveform 2 - Time periods: A= 2T s, B = T s, Cin = 4T s



These two waveforms are enough to give us the required 12 propagation delay values.

The measured propagation delays using Calculator are:

Delay	Expression	Value (ns)
tpdr (A --> S)	17.17E-9	17.17ns
tpdr (B --> S)	17.17E-9	17.17ns
tpdr (Cin --> S)	17.17E-9	17.17ns
tpdr (A --> Cout)	10.01E-9	10.01ns
tpdr (B --> Cout)	10.01E-9	10.01ns
tpdr (Cin --> Cout)	10.01E-9	10.01ns
tpdf (A --> S)	9.938E-9	9.938ns
tpdf (B --> S)	10.26E-9	10.26ns
tpdf (Cin --> S)	9.221E-9	9.221ns
tpdf (A --> Cout)	7.37E-9	7.37ns
tpdf (B --> Cout)	7.331E-9	7.331ns
tpdf (Cin --> Cout)	10.02E-9	10.02ns

The Calculator stack:

From Waveform 1 -

```
delay(?wf1 v("/Cin" ?result "tran"), ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/Cout" ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 2, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(?wf1 v("/A" ?result "tran"), ?value1 2.5, ?edge1 "falling", ?nth1 2, ?td1 0.0, ?tol1 nil, ?wf2 v("/Cout" ?result "tran"), ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(?wf1 v("/Cin" ?result "tran"), ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/S" ?result "tran"), ?value2 2.5, ?edge2 "falling", ?nth2 2, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(?wf1 v("/A" ?result "tran"), ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/S" ?result "tran"), ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(?wf1 v("/Cin" ?result "tran"), ?value1 2.5, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/Cout" ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(?wf1 v("/B" ?result "tran"), ?value1 2.5, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/Cout" ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(?wf1 v("/A" ?result "tran"), ?value1 2.5, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/Cout" ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(?wf1 v("/Cin" ?result "tran"), ?value1 2.5, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/S" ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(?wf1 v("/B" ?result "tran"), ?value1 2.5, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/S" ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(?wf1 v("/A" ?result "tran"), ?value1 2.5, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/S" ?result "tran"), ?value2 2.5, ?edge2 "rising", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
```


From Waveform 2 –

```
delay(?wf1 v("/B" ?result "tran"), ?value1 2.5, ?edge1 "falling", ?nth1 2, ?td1 0.0, ?tol1 nil, ?wf2 v("/Cout" ?result "tran"), ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
delay(?wf1 v("/B" ?result "tran"), ?value1 2.5, ?edge1 "falling", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/S" ?result "tran"), ?value2 2.5, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop 5, ?multiple nil)
v("/Cout" ?result "tran")
v("/S" ?result "tran")
v("/Cin" ?result "tran")
v("/B" ?result "tran")
v("/A" ?result "tran")
```

PART C

Average Power Consumption:

Expression = VAR("Vdd") * integ(IT("/V0/MINUS") 0 VAR("T") " ") / VAR("T")

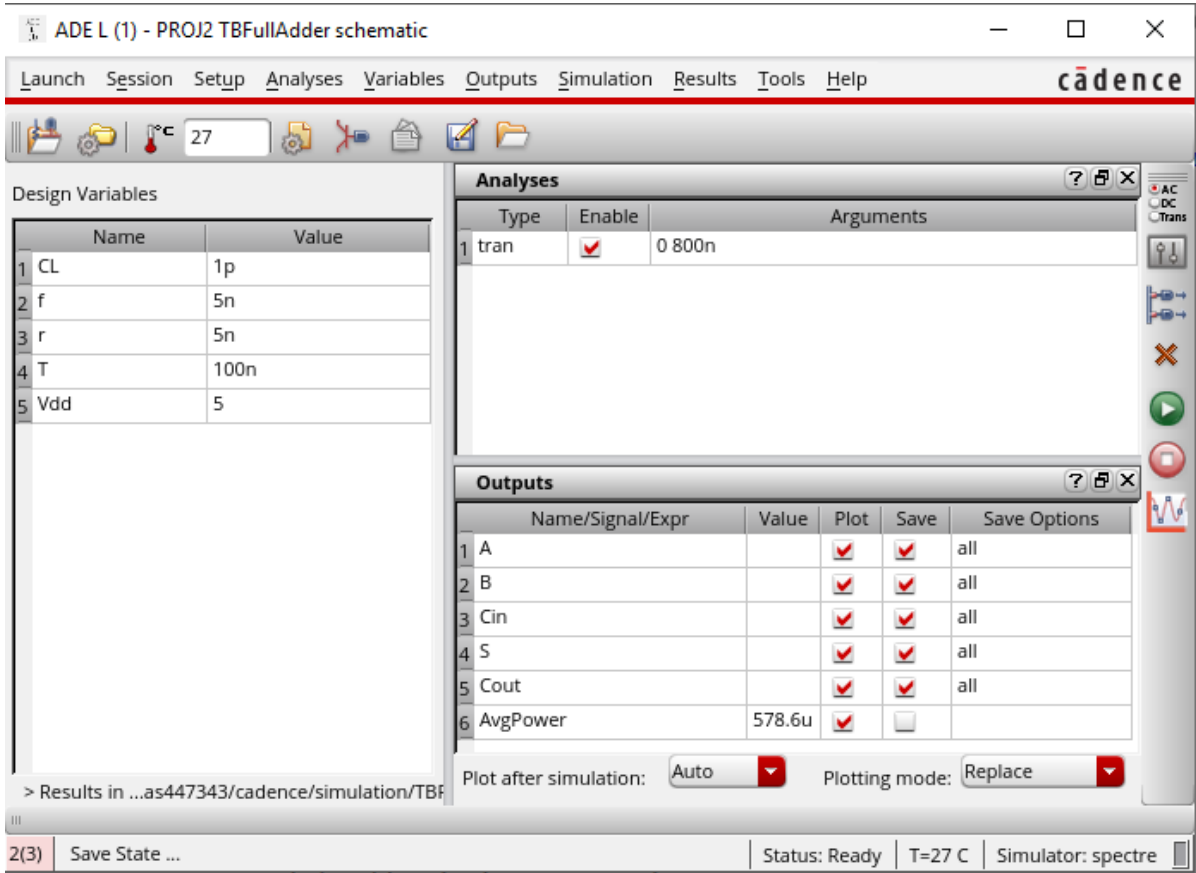

Analysis 1.1: Increasing T in 2x steps (keeping values of CL = 1pF, r = 5ns, f = 5ns)

T (ns)	AvgPower (μ W)
100ns	578.6 μ W
200ns	295.7 μ W
400ns	147.9 μ W
800ns	73.98 μ W
1600ns	33.6 μ W

Analysis 1.2: Increasing T in 2x steps (keeping values of CL = 1pF, r = 5% of T, f = 5% of T)

T (ns)	r (ns)	f (ns)	AvgPower (μ W)
100ns	5ns	5ns	578.6 μ W
200ns	10ns	10ns	328.4 μ W
400ns	20ns	20ns	200.2 μ W
800ns	40ns	40ns	134.4 μ W
1600ns	80ns	80ns	74.61 μ W

Hence it is observed that increasing the time period, i.e. **decreasing the frequency** keeping all the other parameters constant, the **average power consumption decreases**.

Analysis 2: Decreasing CL in 2x steps (keeping T = 100ns, r = 5ns, f = 5ns)

CL (pF)	AvgPower (μ W)
2pF	937.3 μ W
1pF	578.6 μ W
500fF	341.6 μ W
250fF	216.8 μ W
125fF	154.3 μ W

Hence it is observed that **decreasing the load capacitance** keeping all the other parameters constant, the **average power consumption decreases**.

Analysis 3: Increasing r, f in 5% of T steps (keeping T = 100ns, CL = 1pF)

r (ns)	f (ns)	AvgPower (μ W)
5ns	5ns	578.6 μ W
10ns	10ns	644.1 μ W
15ns	15ns	716.3 μ W
20ns	20ns	787.8 μ W
25ns	25ns	857.6 μ W
30ns	30ns	933.2 μ W

Hence it is observed that **increasing the rise/fall times** keeping all the other parameters constant, the **average power consumption increases**.